



# Combinational Logic Design

---

# Arithmetic Functions and Circuits



# Overview

---

- Binary Addition
  - Half Adder
  - Full Adder
  - Ripple Carry Adder
  - Carry Look-ahead Adder
- Binary Subtraction
  - Binary Subtractor
  - Binary Adder-Subtractor
- Subtraction with Complements
  - Complements (2's complement and 1's complement)
  - Binary Adder-Subtractor
- Signed Binary Numbers
  - Signed Numbers
  - Signed Addition/Subtraction
  - Overflow Problem
- Binary Multipliers
- Other Arithmetic Functions

# 1-bit Addition

- Performs the addition of two binary bits.
- Four possible operations:
  - $0+0=0$
  - $0+1=1$
  - $1+0=1$
  - $1+1=10$
- Circuit implementation requires 2 outputs; one to indicate the **sum** and another to indicate the **carry**.

# Half Adder

- Performs 1-bit addition.
- Inputs:  $A_0$ ,  $B_0$
- Outputs:  $S_0$ ,  $C_1$
- Index indicates significance, 0 is for LSB and 1 is for the next higher significant bit.
- Boolean equations:
  - $S_0 = A_0B_0' + A_0'B_0 = A_0 \oplus B_0$
  - $C_1 = A_0B_0$


Truth Table

$A_0$	$B_0$	$S_0$	$C_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


# Half Adder (cont.)

- $S_0 = A_0B_0' + A_0'B_0 = A_0 \oplus B_0$
- $C_1 = A_0B_0$

Block Diagram

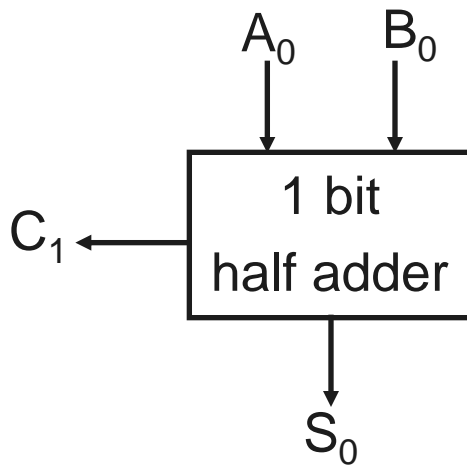

Logic Diagram

 

# n-bit Addition

- Design an n-bit binary adder which performs the addition of two n-bit binary numbers and generates a n-bit **sum** and a **carry out**.

- Example: Let n=4


<b>C<sub>out</sub></b>	<b>C<sub>3</sub></b>	<b>C<sub>2</sub></b>	<b>C<sub>1</sub></b>	<b>C<sub>0</sub></b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>
	<b>A<sub>3</sub></b>	<b>A<sub>2</sub></b>	<b>A<sub>1</sub></b>	<b>A<sub>0</sub></b>		<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
	<b>+B<sub>3</sub></b>	<b>B<sub>2</sub></b>	<b>B<sub>1</sub></b>	<b>B<sub>0</sub></b>	<b>+1</b>	<b>1</b>	<b>0</b>	<b>1</b>	
	-----				-----				
	<b>S<sub>3</sub></b>	<b>S<sub>2</sub></b>	<b>S<sub>1</sub></b>	<b>S<sub>0</sub></b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	

- **Notice that in each column we add 3 bits!**

# Full Adder

- Combinational circuit that performs the additions of 3 bits (two bits and a carry-in bit).
- Full Adder is used for addition of n-bit binary numbers (for higher-order bit addition).

Block Diagram

 

Truth Table

$A_i$	$B_i$	$C_i$		$S_i$	$C_{i+1}$
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1

# Full Adder (cont.)

- K-maps:

**K-map for  $S_i$**

		$B_i C_i$		$B_i$	
		00	01	11	10
$A_i$	0		1		1
$A_i$	1	1		1	
		$C_i$			

**K-map for  $C_{i+1}$**

		$B_i C_i$		$B_i$	
		00	01	11	10
$A_i$	0			1	
$A_i$	1		1	1	1
		$C_i$			

- Boolean equations:

- $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$

- $S_i = A_i B_i' C_i' + A_i' B_i' C_i + A_i' B_i C_i' + A_i B_i C_i$   
 $= A_i \oplus B_i \oplus C_i$

- You can design full adder circuit **directly** from the above equations (requires 3 ANDs and 2 OR for  $C_{i+1}$  and 2 XORs for  $S_i$ )

- Can we do better?




# Full Adder using 2 Half Adders

- A full adder can also be realized with **two half adders** and an OR gate, since  $C_{i+1}$  can also be expressed as:

- $$\begin{aligned} C_{i+1} &= A_i B_i + A_i C_i + B_i C_i \\ &= A_i B_i + A_i (B_i + B_i') C_i + (A_i + A_i') B_i C_i \\ &= A_i B_i + A_i B_i C_i + A_i B_i' C_i + A_i B_i C_i + A_i' B_i C_i \\ &= A_i B_i (1 + C_i + C_i) + C_i (A_i B_i' + A_i' B_i) \\ &= A_i B_i + C_i (A_i \oplus B_i) \end{aligned}$$

- $$S_i = A_i \oplus B_i \oplus C_i$$

 





# n-bit Combinational Adders

---

- Perform *parallel* addition of n-bit binary numbers.
- Ripple Carry Adder
  - Simple design.
  - Slow circuit. Why? (you'll see ...)
- Carry Lookahead Adder
  - More complex than ripple-carry adder.
  - Reduces circuit delay.

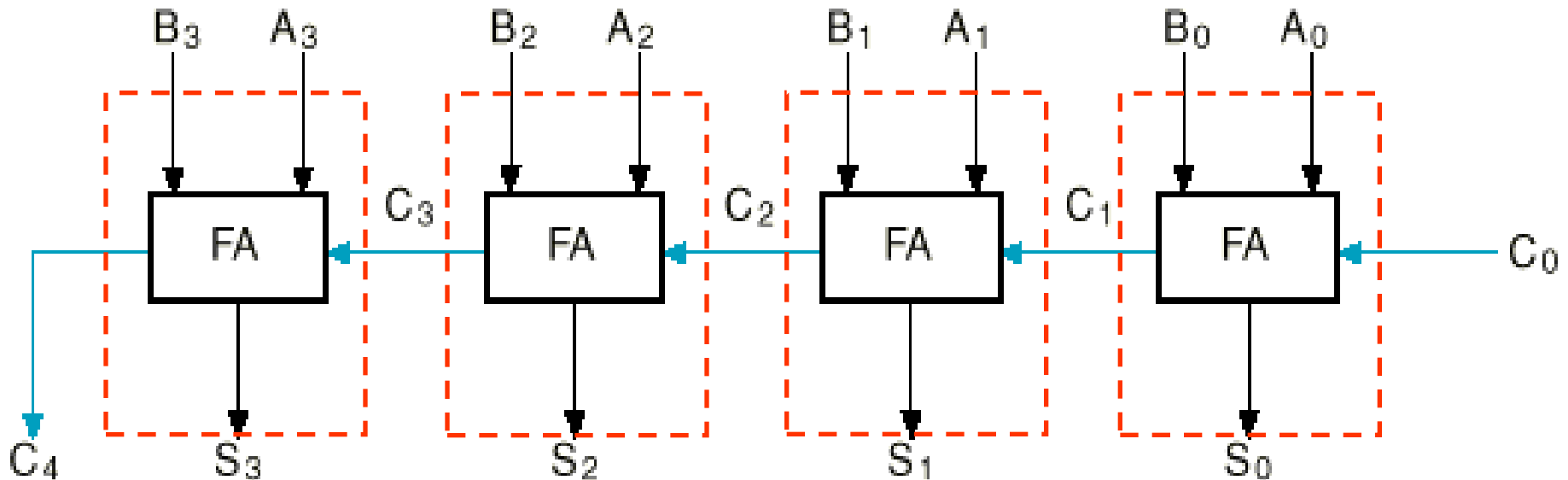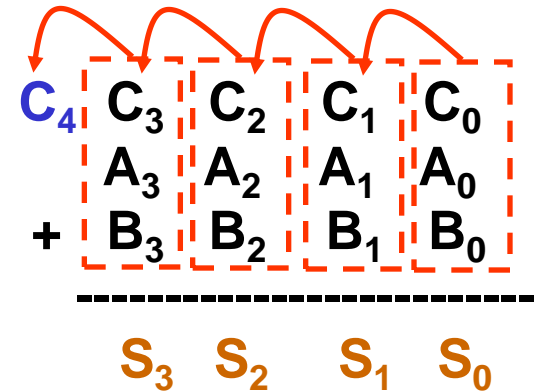
# n-bit Ripple Carry Adder

- Constructed using  $n$  1-bit full adder blocks in parallel.
- Cascade the full adders so that the carry out from one becomes the carry in to the next higher bit position.
- Example: 4-bit Ripple Carry Adder




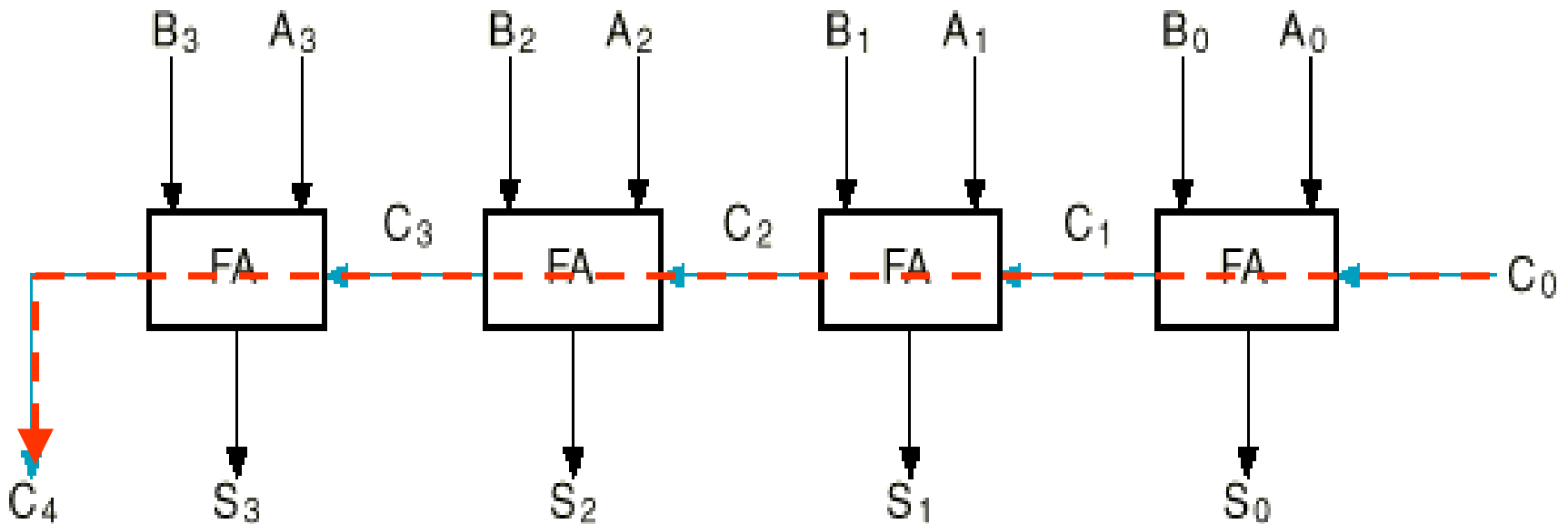
# Ripple Carry Adder Delay

- Circuit delay in an n-bit ripple carry adder is determined by the **delay on the carry path** from the LSB ( $C_0$ ) to the MSB ( $C_n$ ).
- Let the delay in a 1-bit FA be  $\Delta$ . Then, the delay of an n-bit ripple carry adder is  $n\Delta$ .


 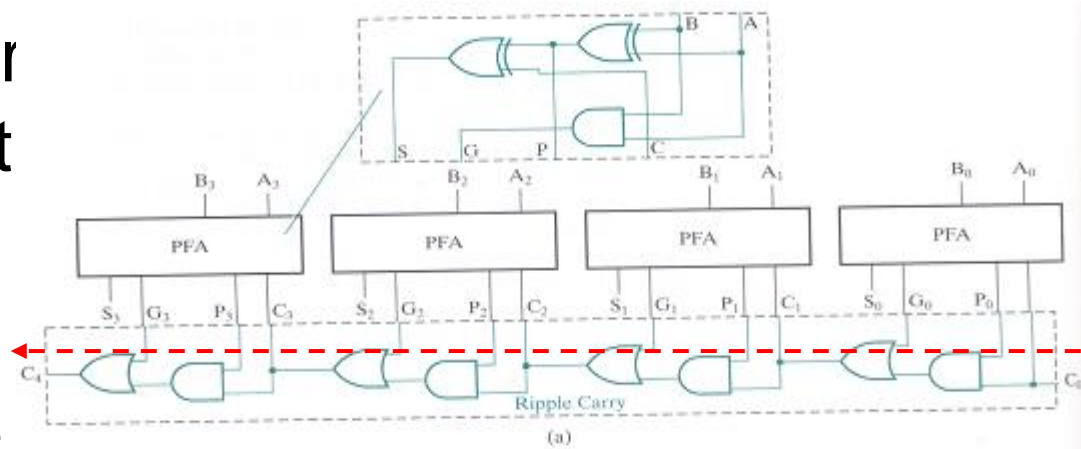
# Carry Look-ahead Addder

- Alternative design for a combinational n-bit adder.
- Reduced delay at the expense of more complex hardware.
- ← - Ripple Carry Delay (RD)
- ← - Carry Look-ahead Delay (LD)
- LD < RD**
- Study this circuit in detail using the textbook.



# Binary Subtraction

- **Unsigned numbers:** minus sign is not explicitly represented.
- Given 2 binary numbers M and N, find M-N:

- Case I:  $M \geq N$ , thus, MSB of Borrow is 0

B	0	0	0	1	1	0	
M		1	1	1	1	0	30
N		1	0	0	1	1	19
Dif		0	1	0	1	1	11

Result is Correct

- Case II:  $N > M$ , thus MSB of Borrow is 1

B	1	1	1	0	0	0	
M		1	0	0	1	1	19
N		1	1	1	1	0	30
Dif		1	0	1	0	1	21

Result requires correction!

# Binary Subtraction (cont.)

- In Case II of the previous example,  $Dif = 19 - 30 = 21 = 19 - 30 + 2^5$  (not correct).
- In general, if  $N > M$ ,  $Dif = M - N + 2^n$ , where  $n = \# \text{ bits}$ .
- To correct the magnitude of Dif, which should be  $N - M$ , calculate  $2^n - (M - N + 2^n) = N - M$  (**correct**).
- This is known as the 2's complement of Dif.
- To subtract two  $n$ -bit numbers,  $M - N$ , in base 2:
  - Find  $M - N$ .
  - If MSB of Borrow is 0, then  $M \geq N$ . Result is positive and correct.
  - If MSB of Borrow is 1, then  $N > M$ . Result is negative and its magnitude must be corrected by subtracting it from  $2^n$  (find its 2's complement).

# Another Subtraction Example

- Given  $M = 01100100$  and  $N = 10010110$ , find  $M-N$ .

B	1	0	0	1	1	1	1	0	0	
M	-	0	1	1	0	0	1	0	0	100
N	-	1	0	0	1	0	1	1	0	150
Dif		1	1	0	0	1	1	1	0	206


(the result is negative)

$2^n$	1	0	0	0	0	0	0	0	0	256
Dif	-	1	1	0	0	1	1	1	0	206
		0	0	0	1	1	0	0	1	50

(corrected result, should be read as -50)




# Block Diagram for Subtractor

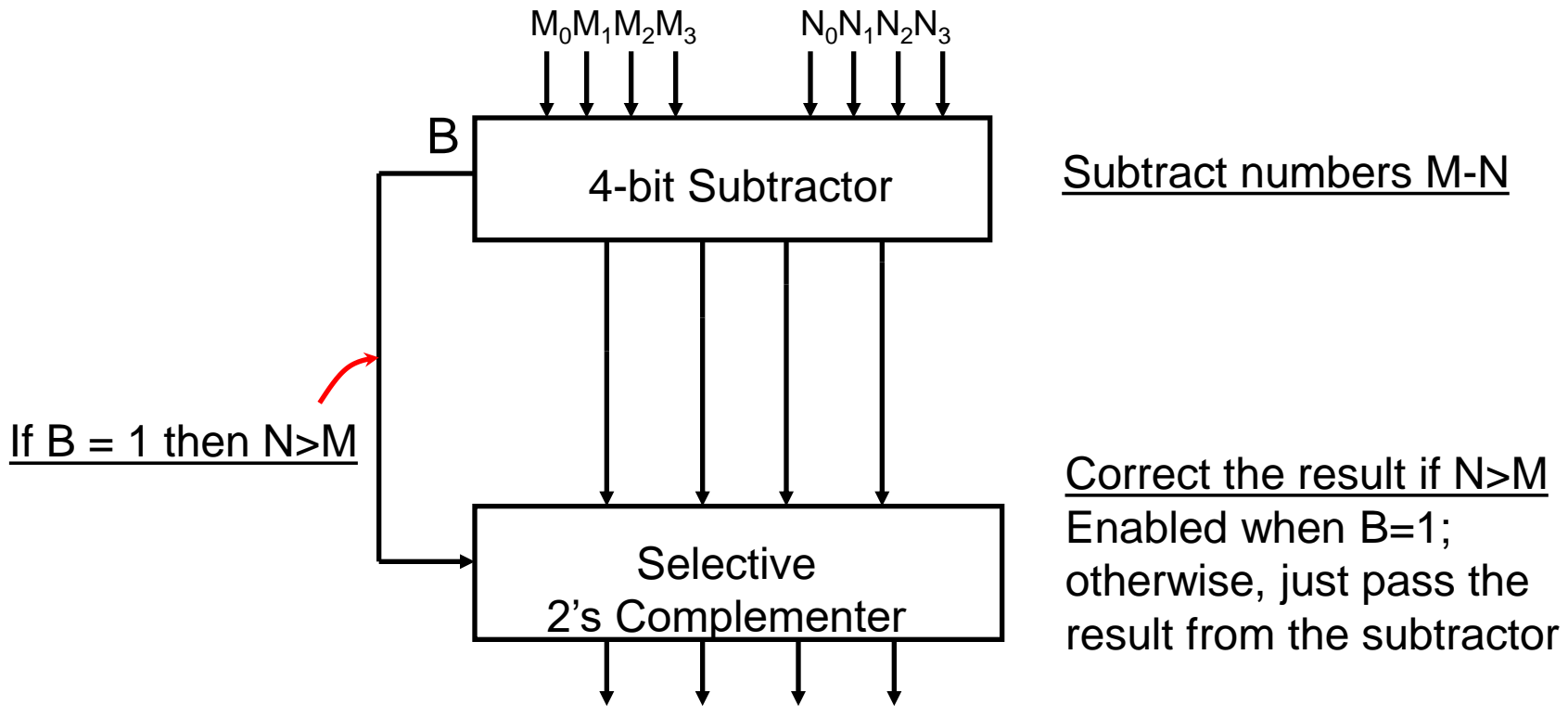

Not the best way to implement a subtractor circuit!
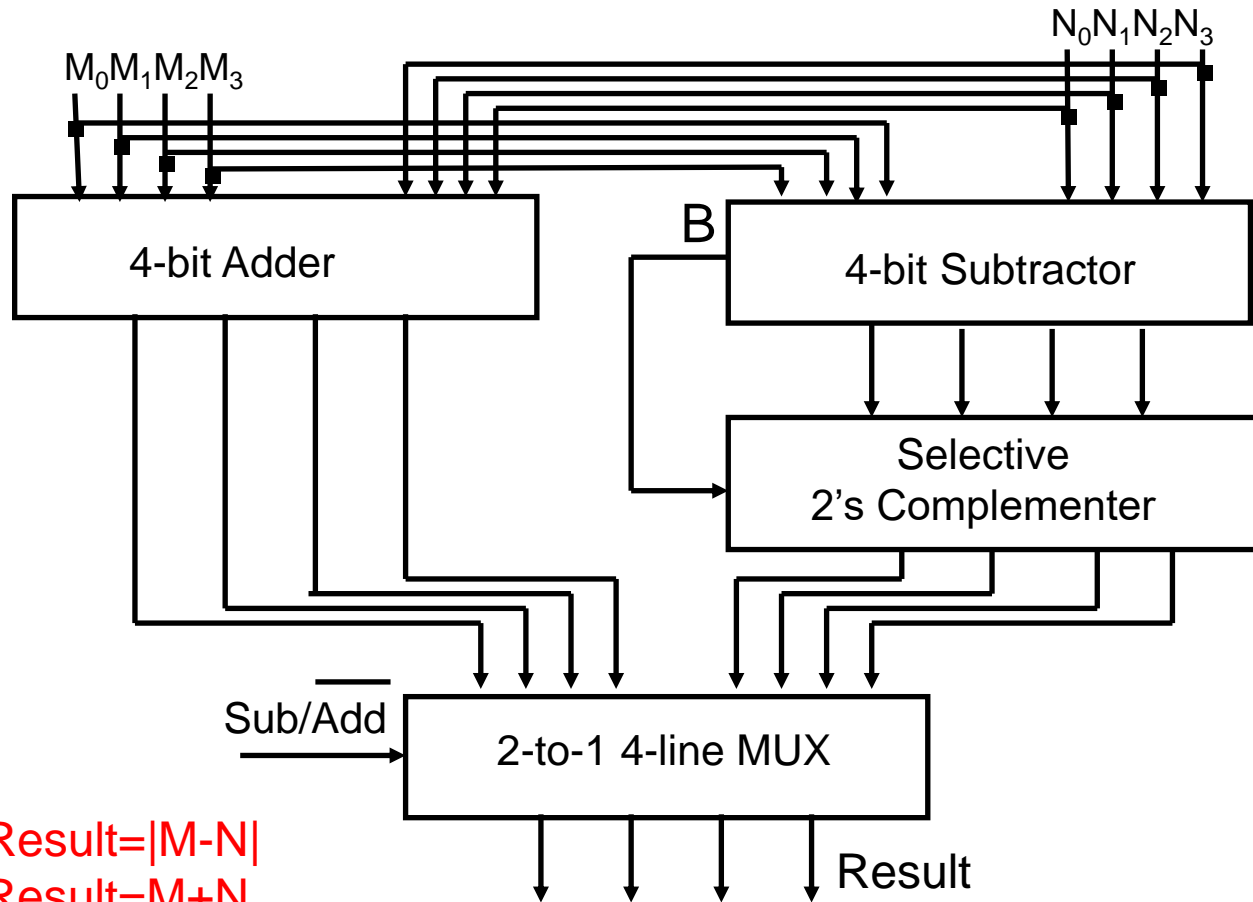
# Block Diagram for Binary Adder-Subtractor



$\overline{\text{Sub/Add}}=1 \rightarrow \text{Result}=|M-N|$   
 $\text{Sub/Add}=0 \rightarrow \text{Result}=M+N$

Again, not the best way to implement a Sub/Add circuit!



# Complement Representations

---

- There are 2 types of complement representation of a number in base-**2** (*binary*) system:
  - 2's complement
  - 1's complement
- We have discussed this briefly at the beginning of the course (see Lecture 1).

# 2's Complement

- For a positive  $n$ -bit number  $N$ , the 2's complement,  $2C(N)$ , is given by:
  - $2C(N) = 2^n - N$
- Example:  $N = 1010$ 
  - $2C(N) = 2^4 - N = 10000 - 1010_2 = \mathbf{0110}$
- Example:  $N = 11111$ 
  - $2C(N) = 2^5 - N = 100000 - 11111 = 00001$
- Here's an easier way to compute the 2's complement:
  1. Leave all least significant 0's and first 1 unchanged
  2. Replace 0 with 1 and 1 with 0 in all remaining higher significant bits.
- Examples:

complement | unchanged

■  $N = 1010$

└─→ **0110**

2's complement on N

complement | unchanged

$N = 01011000$

└─→ **10101000**

2's complement of N

# 1's Complement

- For a positive  $n$ -bit number  $N$ , the 1's complement,  $1C(N_2)$ , is given by:
  - $1C(N) = (2^n - 1) - N$
- Example:  $N = 011$ 
  - $1C(N) = (2^3 - 1) - N = 111 - 011 = 100$
- Example:  $N = 1010$ 
  - $1C(N) = (2^4 - 1) - N = 1111 - 1010 = 0101$
- Observation1: 1's complement can be derived by just **inverting** all the bits in the number.
- Observation2: Compare **1's complement** with **2's complement**
  - $2^n - N = [(2^n - 1) - N] + 1$
- Thus, the 2's complement can be obtained by deriving the 1's complement and adding 1 to it.
  - Example:
    - $N = 1001$
    - $2C(N) = 1C(N) + 1 = 0110 + 0001 = 0111$



# Subtraction with Complements

---

- To perform the subtraction  $M - N$  do:
  - Take the complement of  $N$ , i.e.,  $C(N)$
  - Perform **addition**  $M + C(N)$
  - May need to **correct** the result
- We have discussed this briefly at the beginning of the course (see Lecture 1).

# Subtraction with 2's complement

- If we use 2's complements to represent negative numbers:
  1. Form  $R_1 = M + 2C(N) = M + (2^n - N) = M - N + 2^n$ .
  2. If there is a nonzero carry out of the addition,  $M \geq N$ , so discard that carry and the remaining digits are the result  $R = M - N$ .
  3. Otherwise,  $M < N$ , so take the 2's complement of  $R_1$  ( $= 2^n - R_1 = 2^n - (M - N + 2^n) = N - M$ ), and attach a minus sign in front, *i.e.*, the result  $R$  is  $-2C([R_1]_2) = -(N - M)$ .
- $A = 1010100$  ( $84_{10}$ ),  $B = 1000011$  ( $67_{10}$ )
- Find  $R = A - B$ :
  - $2C(B) = 0111101$  ( $61_{10}$ )
  - $A + 2C(B) = 1010100 + 0111101 = 10010001$
  - Discard **carry**,  $R = 0010001$  ( $17_{10}$ ) ✓
- Find  $R = B - A$ :
  - $2C(A) = 0101100$  ( $44_{10}$ )
  - $B + 2C(A) = 1000011 + 0101100 = 1101111$  (**no carry, correction req.**)
  - $R = -2C(B + 2C(A)) = -0010001$  ( $-17_{10}$ ) ✓

# Subtraction with 1's complement

- If we use 1's complements to represent negative numbers:
  1. Form  $R_1 = M + 1C(N) = M + (2^n - 1 - N) = M - N + 2^n - 1$ .
  2. If there is a nonzero carry out of the addition,  $M \geq N$ , so discard that carry and add 1 to the remaining digits. The result  $R = M - N$ .
  3. Otherwise,  $M < N$ , so take the 1's complement of  $R_1 (= 2^n - 1 - R_1 = 2^n - 1 - (M - N + 2^n - 1) = N - M)$ , and attach a minus sign in front, *i.e.*, the result  $R$  is  $-1C([R_1]_2) = -(N - M)$ .
- $A = 1010100$  ( $84_{10}$ ),  $B = 1000011$  ( $67_{10}$ )
- Find  $R = A - B$ :
  - $1C(B) = 0111100$  ( $60_{10}$ )
  - $A + 1C(B) = 1010100 + 0111100 = 10010000$
  - Discard **carry** and add 1,  
 $R = 0010000 + 1 = 0010001$  ( $17_{10}$ ) ✓
- Find  $R = B - A$ :
  - $1C(A) = 0101011$
  - $B + 1C(A) = 1000011 + 0101011 = 1101110$  (**no carry, correction needed**)
  - $R = -1C(B + 1C(A)) = -0010001$  ( $-17$ ) ✓




# Binary Adder/Subtractors

- If we perform subtraction using complements
  - we do addition instead of subtraction operation
  - we can use an adder with appropriate complements for subtraction
- Actually, we can use an adder for both addition and subtraction:
  - Complement subtrahend for subtraction
  - Do not complement subtrahend for addition
- Thus, to form an adder-subtractor circuit, we only need a **selective complementer** and an **adder**.
- The subtraction  $A-B$  can be performed as follows:

$$\begin{aligned}A-B &= A + 2C(B) \\ &= A + 1C(B) + 1 \\ &= A + B' + 1\end{aligned}$$

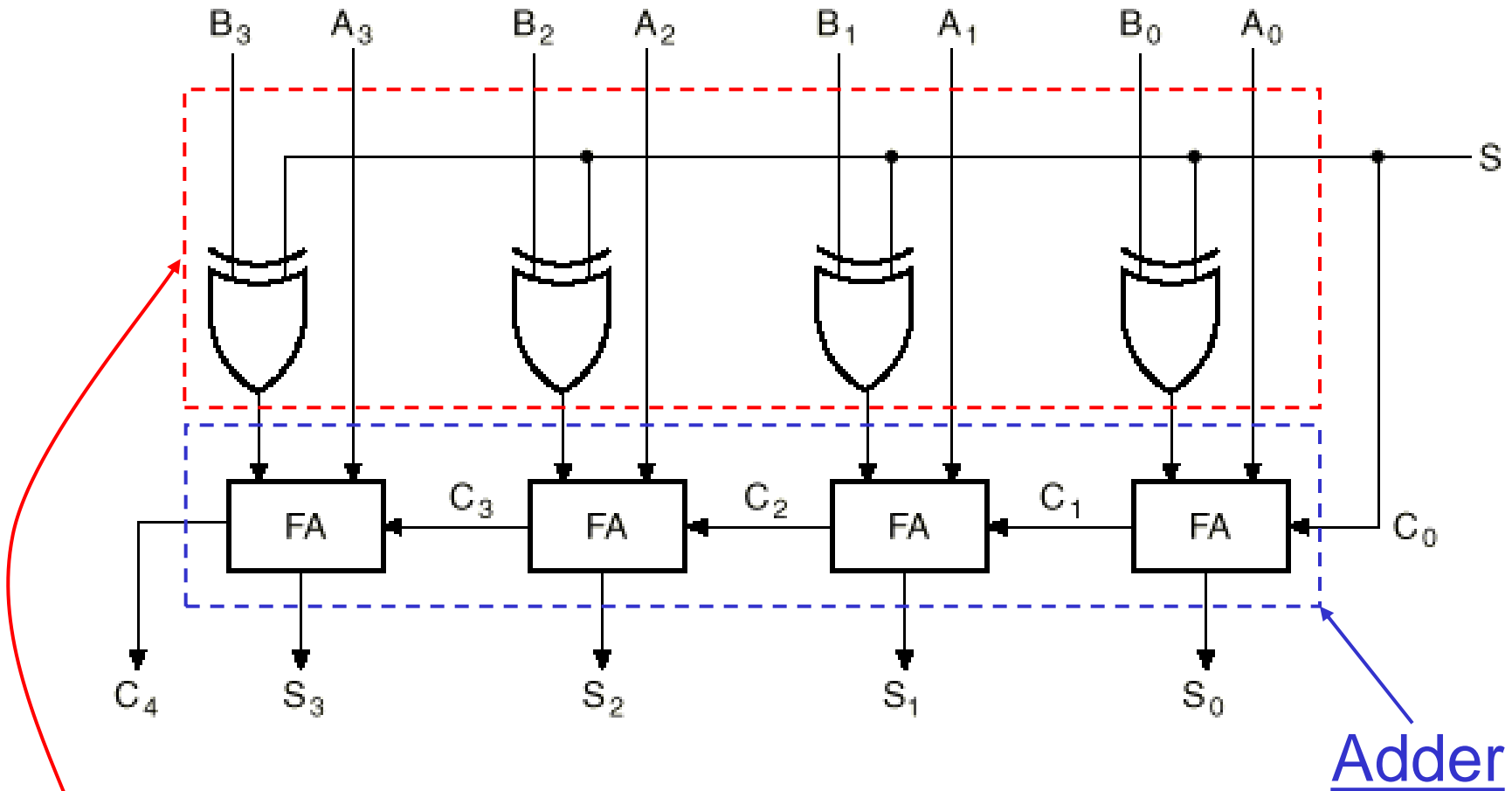
# 4-bit Binary Adder-Subtractor using 2's Complement



Selective complementer:


XOR gates act as programmable inverters

# 4-bit Binary Adder-Subtractor (cont.)

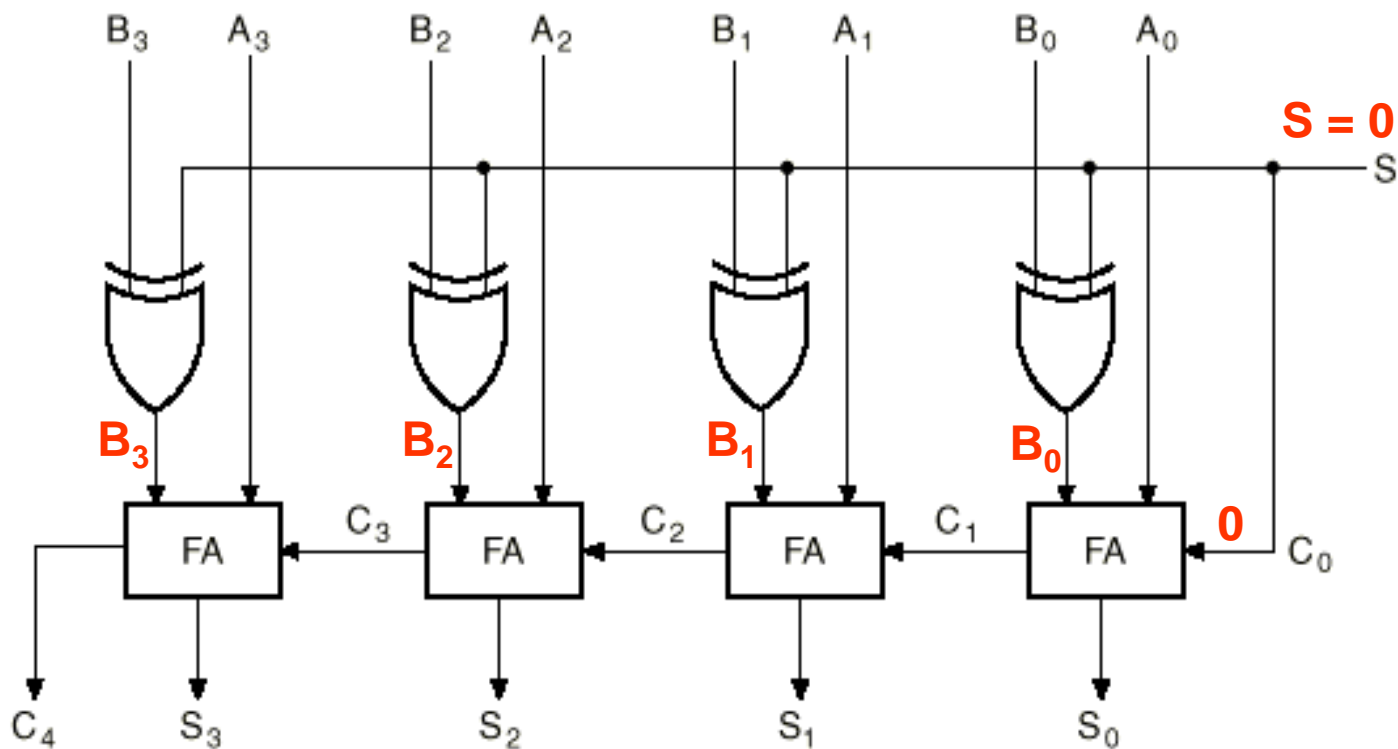

- When  $S = 0$ , the circuit performs  $A + B$ . The carry in is 0, and the XOR gates simply pass  $B$  untouched.

# 4-bit Binary Adder-Subtractor (cont.)

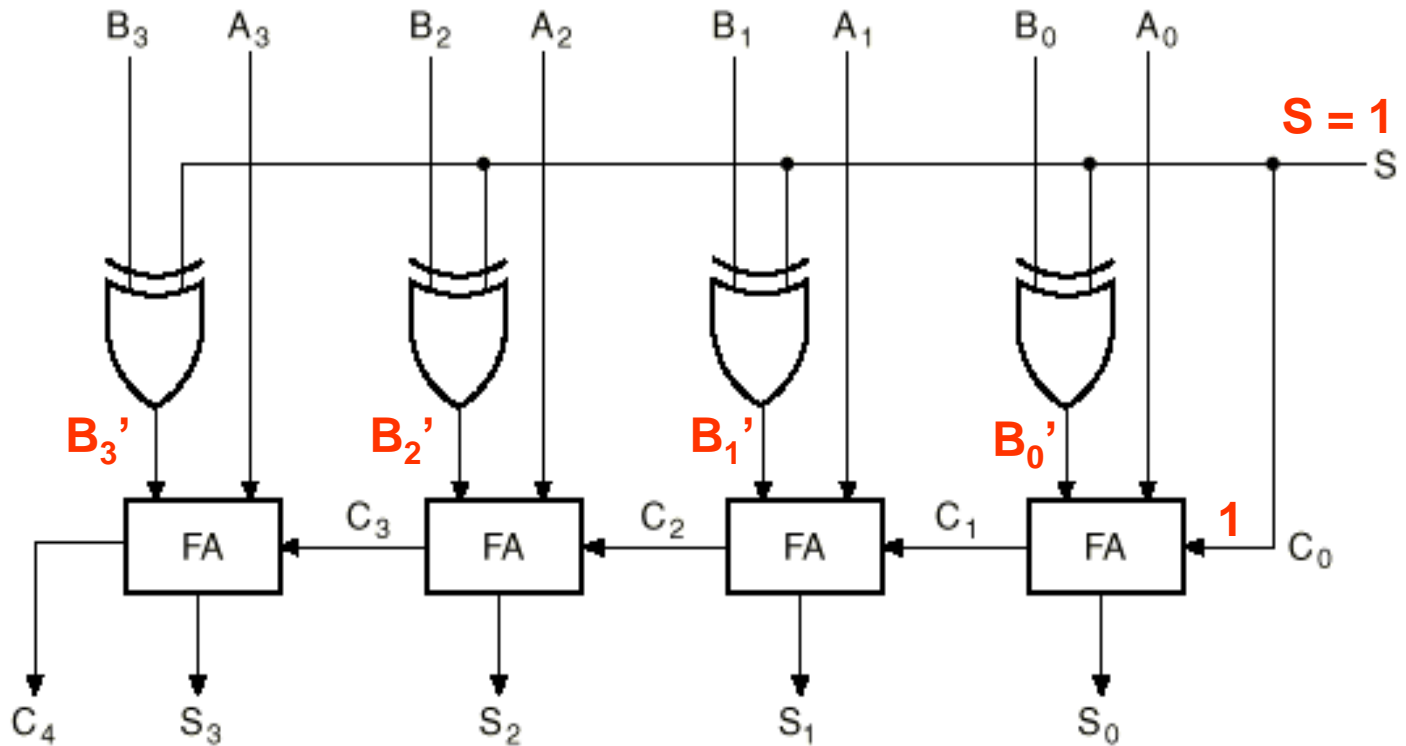


- When  $S = 1$ , the circuit performs  $A - B$ , i.e.,  
 $A - B = A + 2C(B) = A + 1C(B) + 1 = A + B' + 1$
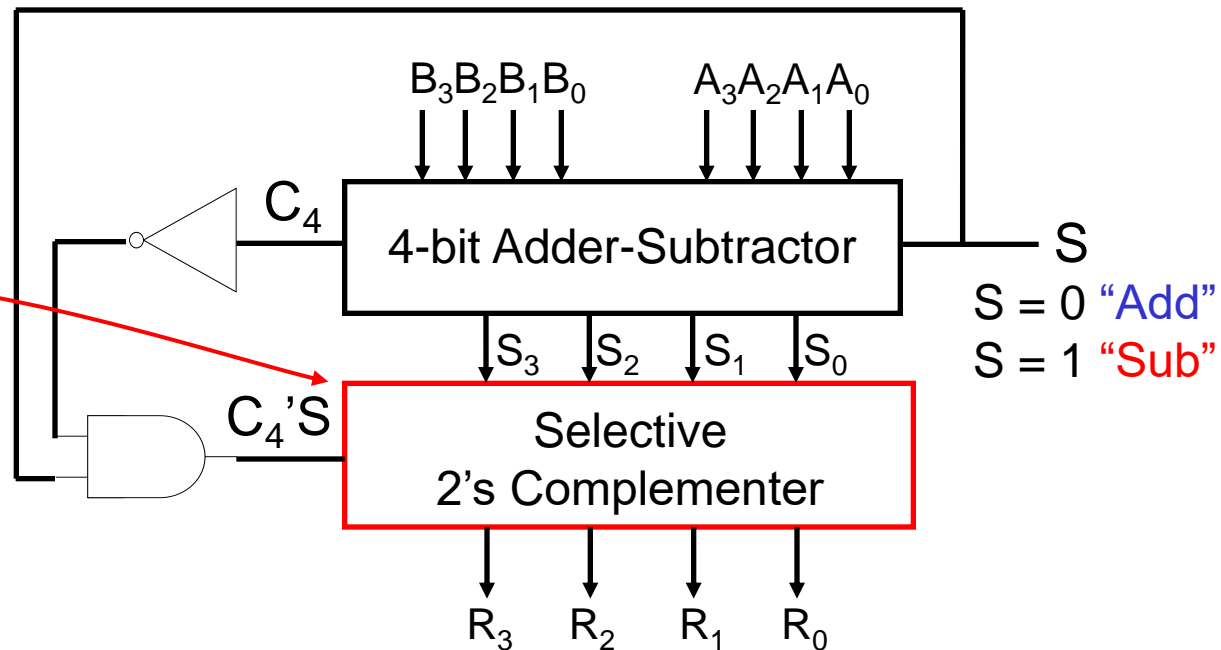
# 4-bit Binary Adder-Subtractor (cont.)

- When we do subtraction, result may need to be corrected
  - If  $C_4 = 0$  and  $S = 1$ , we must correct the result  $S_3 \dots S_0$ .
- Thus, we must compute 2's complement of  $S_3 \dots S_0$ :
  - Use a specialized 2's complement circuit or
  - Use the 4-bit Adder-Subtractor again, with  $A_3 \dots A_0 = 0000$ ,  $B_3 \dots B_0 = S_3 \dots S_0$ , and  $S = 1$ .

Correct the result if  $B > A$   
Enabled when  $C_4'S = 1$ ;  
otherwise, just pass the  
result from Adder-Subtractor





# Signed Binary Numbers

---

- **Signed-magnitude representation**: Signed numbers are represented using the MSB of the binary number to indicate the number's sign:
  - If MSB is 0 → number is positive
  - If MSB is 1 → number is negative
- Do **not** confuse with unsigned numbers!
- For example:
  - $-10_{10}$  is
    - $11010_2$  in signed (“-” sign is indicated in MSB = 1)
- Another example:
  - $1011_2$  is
    - $11_{10}$  in unsigned
    - $-3_{10}$  in signed

# Signed-Magnitude Addition-Subtraction

- To implement signed-magnitude addition and subtraction
  - separate the **sign bit** from the **magnitude bits**
  - treat the magnitude bits as an unsigned number
  - do ordinary arithmetic
  - **do correction if needed**
- Example: M:00011001, N:10100101; find M+N
  - N is negative
  - so do  $M-N = 0011001-0100101 = 1110100$ , with end borrow 1. This implies that M-N is a negative number,
  - so to correct find its 2's complement 0001100. Result is 10001100.



# Signed-Complement System

---

- To avoid correction of the result, use the singed-complement representation of numbers
  - Signed-1's complement
  - Signed-2's complement
- Ex.: Use 8-bits to represent  $-9_{10}$  and  $9_{10}$ 
  - $9_{10}$  is  $00001001_2$  in any of the above representations
  - $-9_{10}$  is:
    - $10001001_2$  in singed-magnitude
    - $11110110_2$  in singed-1's complement
    - $11110111_2$  in singed-2's complement



# Signed-Complement Addition

- Addition of two signed numbers in signed-2's complement form is obtained
  - by adding the two numbers **including the sign bits**.
  - **carry out is discarded**".
- Examples: (Assume 5-bit representations)

$$\begin{array}{r} 0|1010 \ (+10) \\ + 0|0101 \ (+5) \\ \hline 0|1111 \ (+15) \end{array}$$

$$\begin{array}{r} 0|1010 \ (+10) \\ + 1|1011 \ (-5) \\ \hline 10|0101 \ (+5) \end{array}$$

$$\begin{array}{r} 1|0110 \ (-10) \\ + 0|0101 \ (+5) \\ \hline 1|1011 \ (-5) \end{array}$$

$$\begin{array}{r} 1|0110 \ (-10) \\ + 1|1011 \ (-5) \\ \hline 11|0001 \ (-15) \end{array}$$

# Signed-Complement Subtraction

- Subtraction of two signed numbers in signed-2's complement form is obtained by
  - taking the **2's complement** of the subtrahend **including sign bit**
  - add it to the minuend
  - **Discard carry out**


- Examples: (Assume 5-bit representations)

$$\begin{array}{r}
 0|1010 \quad (+10) \\
 \hline
 -0|0101 \quad -(+5)
 \end{array}
 \quad
 \begin{array}{r}
 0|1010 \quad (+10) \\
 \hline
 -1|1011 \quad -(-5)
 \end{array}
 \quad
 \begin{array}{r}
 1|0110 \quad (-10) \\
 \hline
 -0|0101 \quad -(+5)
 \end{array}
 \quad
 \begin{array}{r}
 1|0110 \quad (-10) \\
 \hline
 -1|1011 \quad -(-5)
 \end{array}$$

$$\begin{array}{r}
 0|1010 \quad (+10) \\
 +1|1011 \quad +(-5) \\
 \hline
 10|0101 \quad (+5)
 \end{array}
 \quad
 \begin{array}{r}
 0|1010 \quad (+10) \\
 +0|0101 \quad +(+5) \\
 \hline
 0|1111 \quad (+15)
 \end{array}
 \quad
 \begin{array}{r}
 1|0110 \quad (-10) \\
 +1|1011 \quad +(-5) \\
 \hline
 11|0001 \quad (-15)
 \end{array}
 \quad
 \begin{array}{r}
 1|0110 \quad (-10) \\
 +0|0101 \quad +(+5) \\
 \hline
 1|1011 \quad (-5)
 \end{array}$$

 
# Binary Adder-Subtractor using 2's Complement Signed Numbers

- The circuit is simpler (**correction is not needed**):



Adder-Subtractor of 4-bit **unsigned** numbers.

Remove the correction circuit

 

Adder-Subtractor of **4-bit signed 2's complement numbers**

The **4-th bit** in the numbers is interpreted as the sign bit.




# The Overflow problem

---

- If the sum of two  $n$ -bit numbers results in an  $n+1$  bit number, then an **overflow** conditions is said to occur.
- Detection of overflow can be implemented using either hardware or software.
- Detection depends on number system used: signed or unsigned.
 
# The Overflow problem in Unsigned System

- Addition:
  - When Carry out is 1 we have overflow.
- Subtraction:
  - Can never occur. Magnitude of the result is always equal or smaller than the larger of the two numbers.
- → **Not REALLY a problem!**



- $V = 1$  indicates overflow condition when adding unsigned numbers.


# The Overflow problem in Signed-2's Complement

- Remember that the MSB is the sign. But, the sign is also added! Thus, a carry out equal to 1 does not necessarily indicate overflow.
- Overflow can occur ONLY when both numbers have the same sign. This condition can be detected when the carry out ( $C_n$ ) is different than the carry at the previous position ( $C_{n-1}$ ).
- Example 1: Let  $M=65_{10}$  and  $N=65_{10}$  in an 8-bit signed-2's complement system.
  - $M = N = 01000001_2$
  - $M+N = 10000010$  with  $C_n=0$ . This is clearly wrong! Bring  $C_n$  as the MSB to get  $010000010_2$  ( $130_{10}$ ) which is correct, but requires 9-bits → **overflow occurs**.
- Example 2: Let  $M=-65_{10}$  and  $N=-65_{10}$  in an 8-bit signed-2's complement system.
  - $M = N = 10111111_2$
  - $M+N = 01111110$  with  $C_n=1$ . This is wrong again! Bring  $C_n$  as the MSB to get  $101111110_2$  ( $-130_{10}$ ) which is correct, but also requires 9-bits → **overflow occurs**.

# Overflow Detection in Signed-2's Complement

- Overflow condition is detected by comparing the carry values into and out of the sign bit ( $C_n$  and  $C_{n-1}$ ).
 
## n-bit Adder/Subtractor with Overflow Detection Logic



- $V = 1$  indicates overflow condition when adding/subtracting signed-2's complement numbers.

# Binary Multiplier

- Binary multiplication resembles decimal multiplication:
  - $n$ -bit multiplicand is multiplied by each bit of the  $m$ -bit multiplier, starting from LSB, to form  $m$  partial products.
  - Each successive partial product is shifted 1 bit to the left.
  - Derive result by addition the  $m$  rows of partial products.
  - The resultant product is a binary number that consists of  $n + m$  bits.
- Example:

- Multiplicand  $\mathbf{B} = (1011)_2$
- Multiplier  $\mathbf{A} = (101)_2$
- Find Product  $\mathbf{C} = \mathbf{B} \times \mathbf{A}$ :


$$\begin{array}{r} \text{Multiplicand: } 1011 \\ \text{Multiplier: } \quad \times \quad 101 \\ \hline \quad \quad \quad 1011 \\ \quad \quad + \quad 0000 \\ \quad \underline{1011} \\ \text{Product: } 110111 \end{array}$$




# 2-bit by 2-bit Binary Multiplier

		$B_1$	$B_0$	
	$A_1$	$A_0$		
	<hr/>			
	$A_0B_1$	$A_0B_0$		
$A_1B_1$	$A_1B_0$			
<hr/>				
$C_3$	$C_2$	$C_1$	$C_0$	

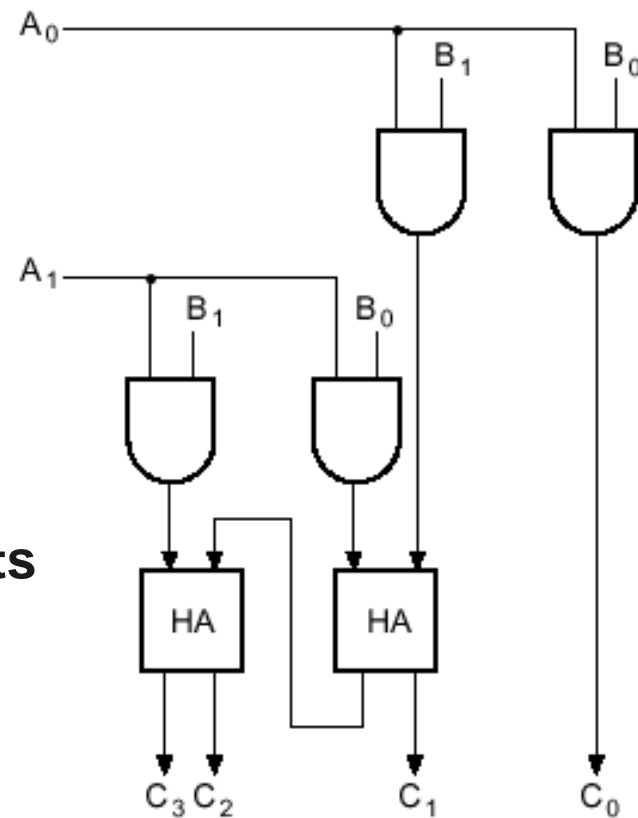**Half Adders are Sufficient**  
since there is no Carry-in  
in addition to the two inputs  
to sum



# 4-bit by 3-bit Binary Multiplier

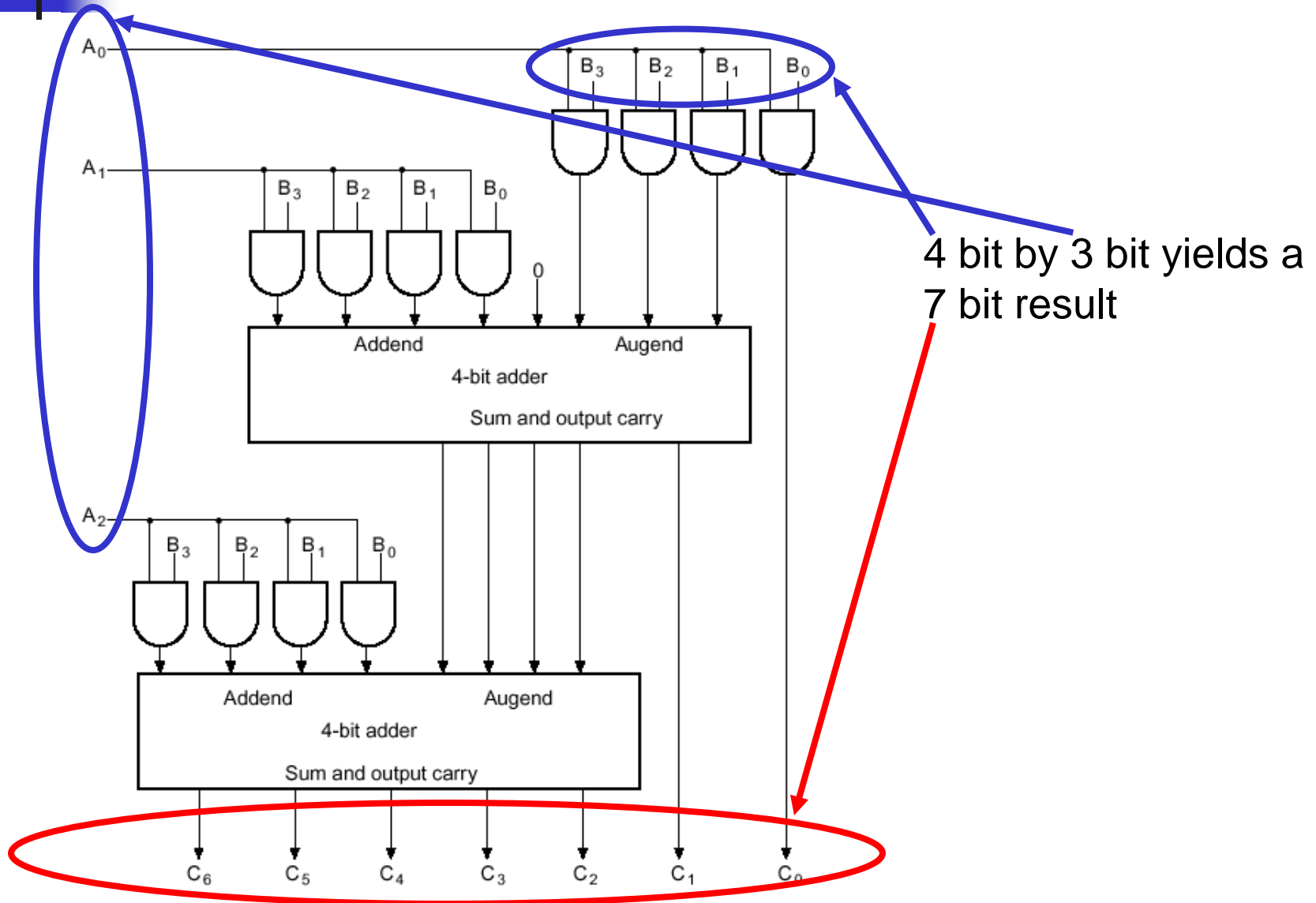




# Other Arithmetic Functions


---

- Incrementing
- Decrementing
- Multiplication by Constant
- Division by Constant

# Increment by 1

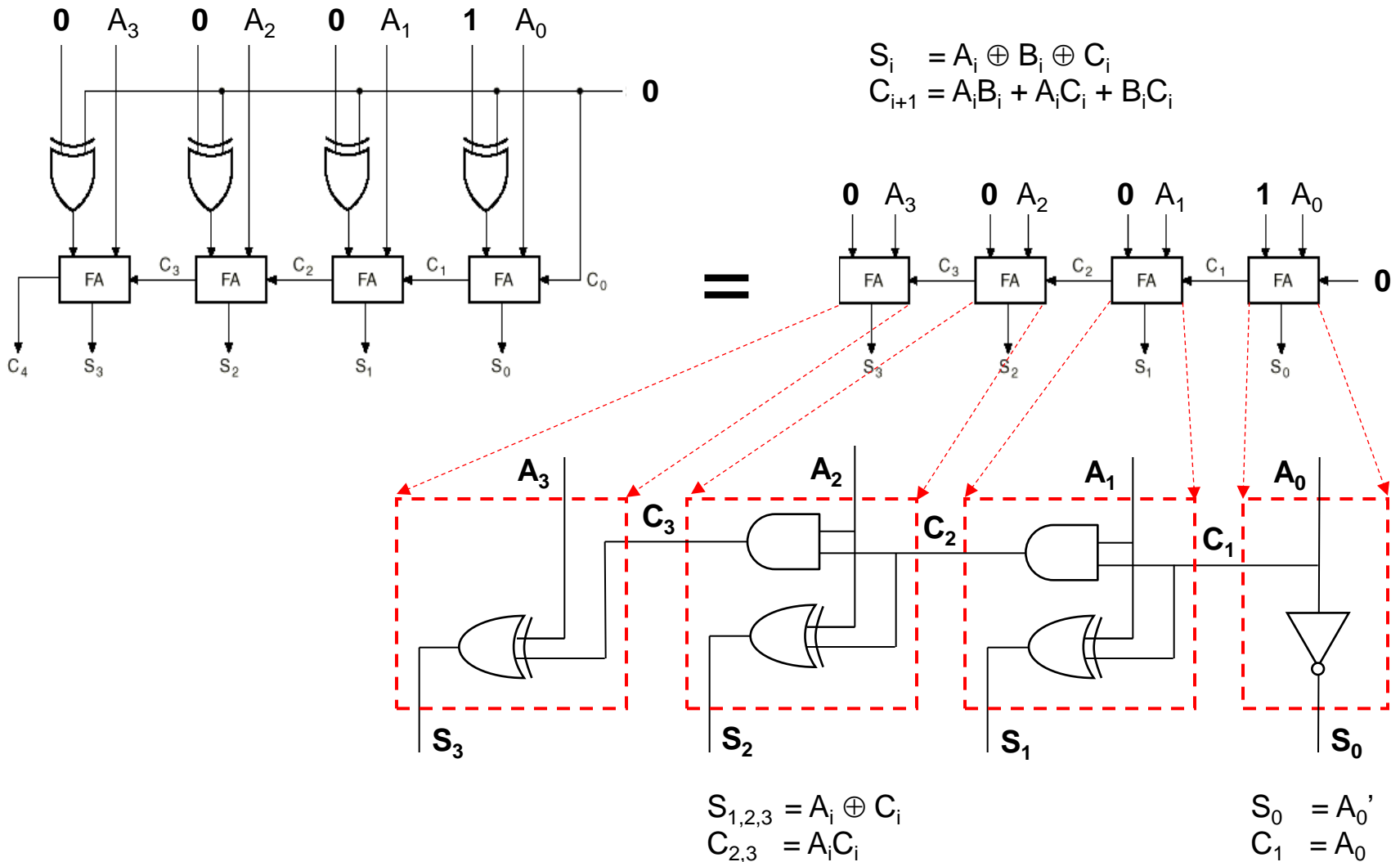


# Decrement by 1

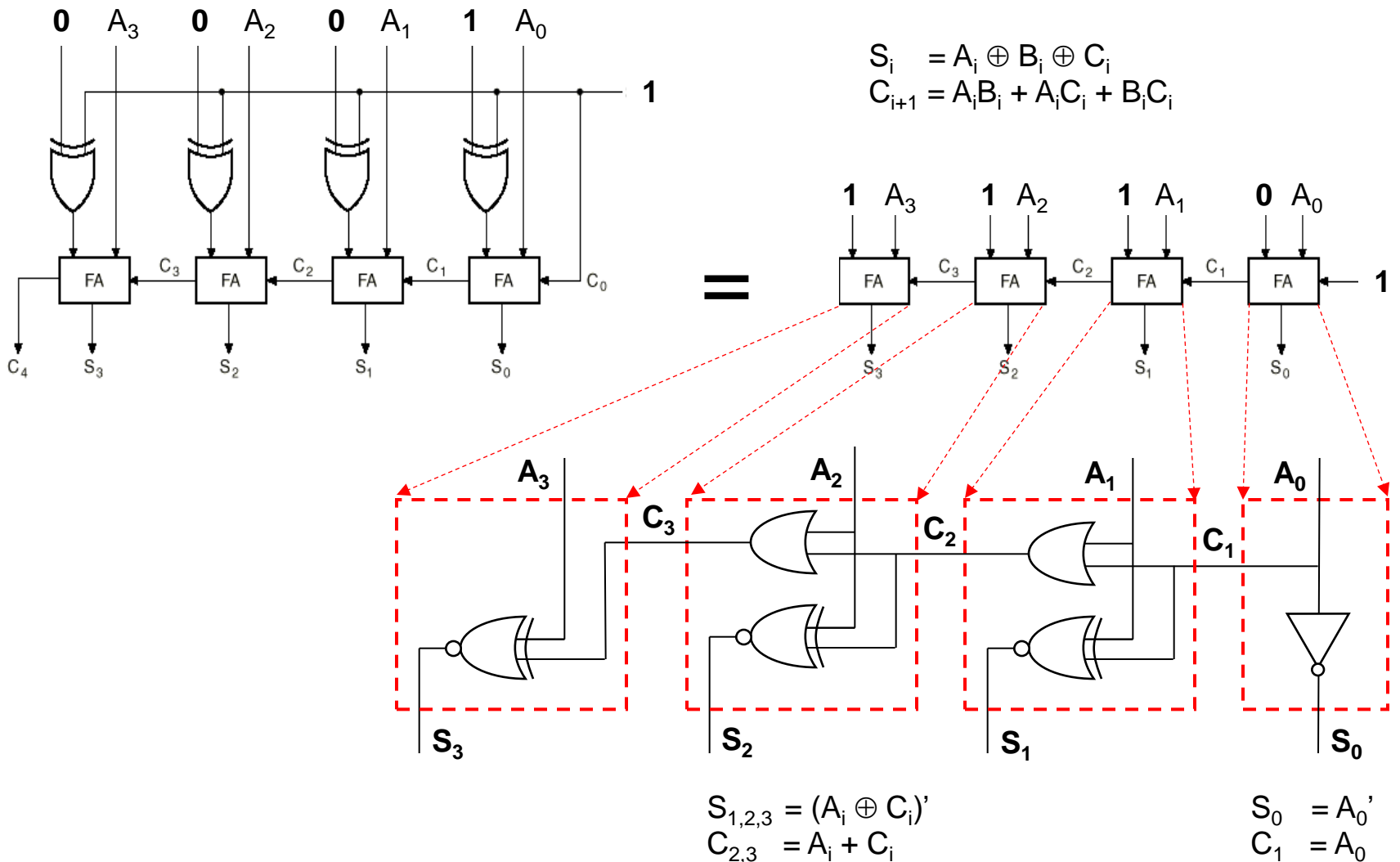


# Multiplication/Division by constant


Multiplication by 2 (shift left)

 


Division by 2 (shift right)

 

Multiplication by  $2^n$

 

Division by  $2^n$

 

$n$  'zeros'