



Sequential Circuits: Basic Concept




Overview

- Sequential Circuits
 - Sequential vs. Combinational Circuits
- Types of Sequential Circuits
 - Synchronous vs. Asynchronous Circuits
- Sequential Circuit Representations
 - Boolean Equations
 - Characteristic (Flip-Flop Input) Equations
 - Primary Output Equations
 - State Table
 - State Diagram
- Finite State Machines
 - Mealy vs. Moore Machines

Combinational vs. Sequential Circuits

 
- Combinational circuits are **memory-less** and **do not have feed-back loops**. Thus, the output values depend **ONLY** on the current input values.



- Able to perform useful operations (add, subtract, multiply, encode, decode, multiplex, demultiplex, etc...).
- However, the performance of useful sequences of operations using only combinational circuits requires cascading many structures together.
- Thus, the hardware to do this is **very costly** and **inflexible**.
- To perform useful or flexible sequences of operations, we need to construct circuits that can **store** information between the operations.
- Such circuits are called **Sequential Circuits**.

Sequential Circuits

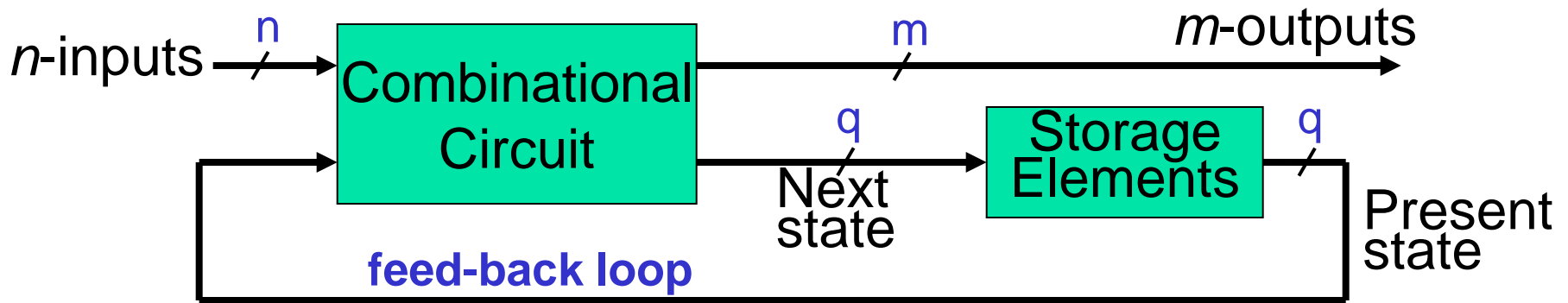- Sequential circuits consist of **combinational logic** as well as **memory elements** (used to store certain circuit states). Outputs depend on **BOTH** current input values and previous input values (kept in the storage elements).



- There is a **feed-back loop** in the sequential circuits.
- The storage elements are circuits that are capable of storing binary information.
- One storage element can store one bit of information.


Storage Elements

- Two types of storage elements are used in Sequential Circuits: **Latches** and **Flip-Flops**.

- Latches (D, SR, JK, T)**

- General description of a latch:

 
- 1-bit storage device with several inputs (\mathbf{X}) and an output (\mathbf{Q}).
- Output is changed $\mathbf{Q} = f(\mathbf{X})$ only when **specific combinations** occur at the inputs \mathbf{X} ; otherwise the output remains unchanged (storage mode).



- Flip-Flops (D, SR, JK, T)**

- General description of a Flip-Flop:

 - 1-bit storage device with several inputs (\mathbf{X}), an output (\mathbf{Q}), and a specific **trigger** input (\mathbf{CLK}).
- Output is changed $\mathbf{Q} = f(\mathbf{X})$ on **response of a pulse at the trigger input \mathbf{CLK}** (on the **rising** or **falling** edge of the pulse). When a pulse is absent at input \mathbf{CLK} the output remains unchanged (storage mode).




- More details about Latches and Flip-Flops later!**



Types of Sequential Circuits


- Sequential circuits are divided into two main types depending on the storage elements that are used in the feed-back loop.
- **Synchronous** Sequential Circuits
 - Circuits with Flip-Flops in the feedback loop
- **Asynchronous** Sequential Circuits
 - Circuits without storage elements in the feed-back loop
OR
 - Circuits with Latches in the feed-back loop
- We will not study asynchronous circuits
 - Only brief description and comparison will follow.

Asynchronous Sequential Circuits

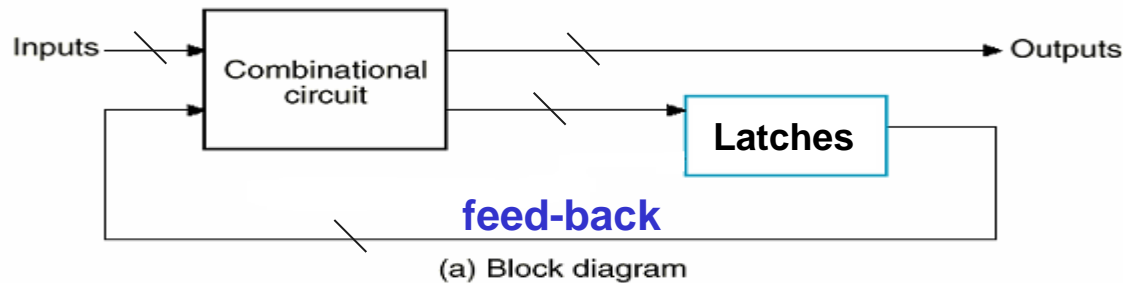

- The behavior is dependent on the order of input signal changes over continuous time, and output can change at **any** time (**clockless**).
- The Latches receive their inputs from the combinational circuit.
- The Latches can change state **as soon as their inputs are changed**.
 - Thus, a transition from one state to the other may occur at **any** time.
 - This makes the design and analysis of the circuit **very difficult**.
- If a circuit is not designed properly its behavior may become unpredictable:
 - The new state may change the Latches again through the **feed-back loop**.
 - This may lead to a **succession of changes of state** instead of a single change even if we do not change the inputs of the circuit:
 - The circuit comes to a stable state after several state transitions.
 - The transition from one state to another may never stop.

Synchronous Sequential Circuits

 

T – clock period

$1/T$ – clock frequency

W/T – duty cycle

(a) Block diagram



rising edge
falling edge

(b) Timing diagram of clock pulses

- The behavior can be defined from knowledge of its signals at discrete instants of time.
 - Circuit achieves synchronization by using a timing signal called the **clock**
- The Flip-Flops receive their inputs from the combinational circuit.
- The Flip-Flops can change state only in response to a **clock pulse** on **rising** or **falling** edge.
- When a clock pulse is absent the Flip-Flop outputs cannot change even if the combinational circuit driving the flip-flop inputs changes in value.
- Thus, a transition from one state to the other occurs **only at fixed time intervals** dictated by the clock pulse, giving synchronous operation.

Synchronous vs. Asynchronous Sequential Circuits

■ Storage Elements:

- In synchronous sequential circuits - **FLIP-FLOPs**.
- In asynchronous sequential circuits - either **Latches** or **gate circuits** with feedback producing the effect of latch operation.

■ State Changes:

- In a synchronous sequential circuit a change of state occurs **only in response to a synchronizing clock pulse**. All the FLIP-FLOPs are clocked **simultaneously** by a common clock pulse.
- In an asynchronous sequential circuit, the state of the circuit can change **immediately when an input change occurs**. It does not use a clock.

■ Circuit Speed:

- In synchronous sequential circuits, the speed of operation depends on the **maximum allowed clock frequency**
 - because states are changed only on response of a clock pulse.
- Asynchronous sequential circuits do not require clock pulses and they can change state with the input change.
 - Therefore, in general the asynchronous sequential circuits are **faster** than the synchronous sequential circuits.

Synchronous vs. Asynchronous Sequential Circuits (cont.)

■ Input Changes:

- In synchronous sequential circuits input changes are assumed to **occur between clock pulses**. The circuit must be in the stable state before next clock pulse arrives.
- In asynchronous sequential circuits input changes should occur **only when the circuit is in a stable state**.

■ Number of Inputs that can Change:

- In synchronous sequential circuits, **any number** of inputs can change **simultaneously** (during the absence of the clock).
- In asynchronous sequential circuits **only one** input is allowed to change at a time. If more than one inputs change simultaneously, the circuit makes erroneous state transitions due to different delay paths for each input variable.

■ Output Changes


- In synchronous sequential circuits outputs change at **any time** when inputs change or **on response to a clock pulse**.
- In asynchronous sequential circuits outputs change at **any time** when inputs are changed.

Synchronous vs. Asynchronous Sequential Circuits (cont.)

- Nowadays, most of the sequential circuits are **synchronous** due to
 - their **predictability** and
 - relatively **easy design and analysis**.
- An **asynchronous circuit** is preferred over synchronous circuit when **high speed of operations are required**
 - asynchronous circuits respond immediately without having to wait for a clock pulse.
- **Asynchronous** sequential circuits **cost less** in terms of number of gates than the synchronous circuits
 - therefore, for economical reasons, they find useful applications.


Synchronous Sequential Circuits: Definitions and Notations

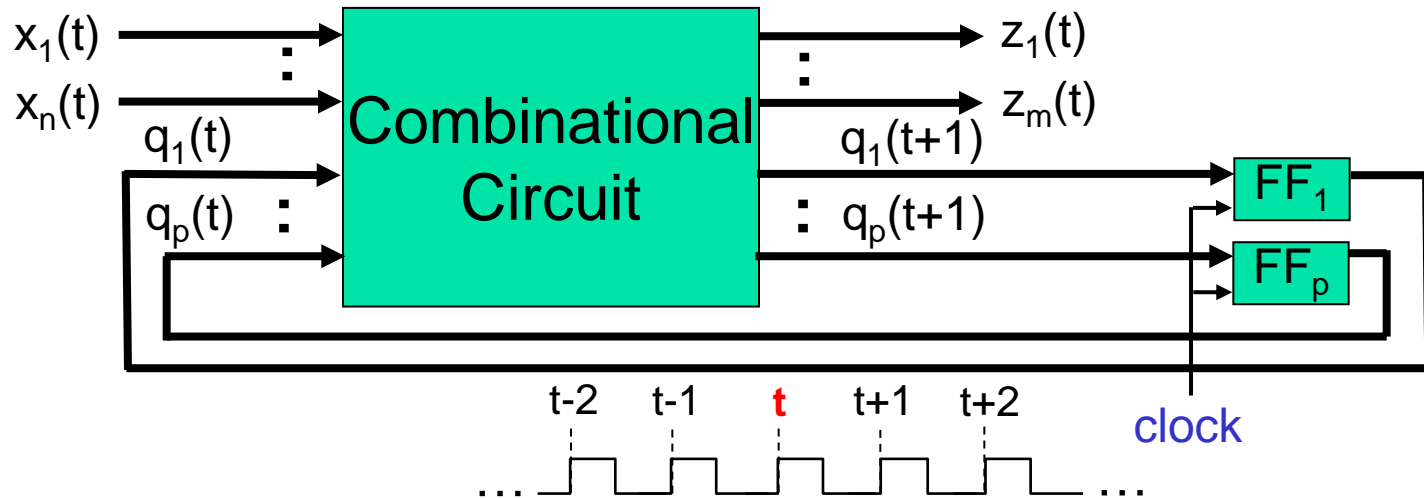- Consider the sequential circuit below which has n inputs, m outputs, and p Flip-Flops (storage elements):



- $x_j(t)$ – the **present value** of input x_j , i.e., the value prior to the application of a clock pulse at time t .
- $z_j(t)$ – the **present value** of output z_j , i.e., the value prior to the application of a clock pulse at time t .
- $q_j(t)$ – the **present value** stored by FF_j , i.e., the value prior to the application of a clock pulse at time t .
- $q_j(t+1)$ – the **next value** to be stored by FF_j , i.e., the value stored after the application of a clock pulse at time t .

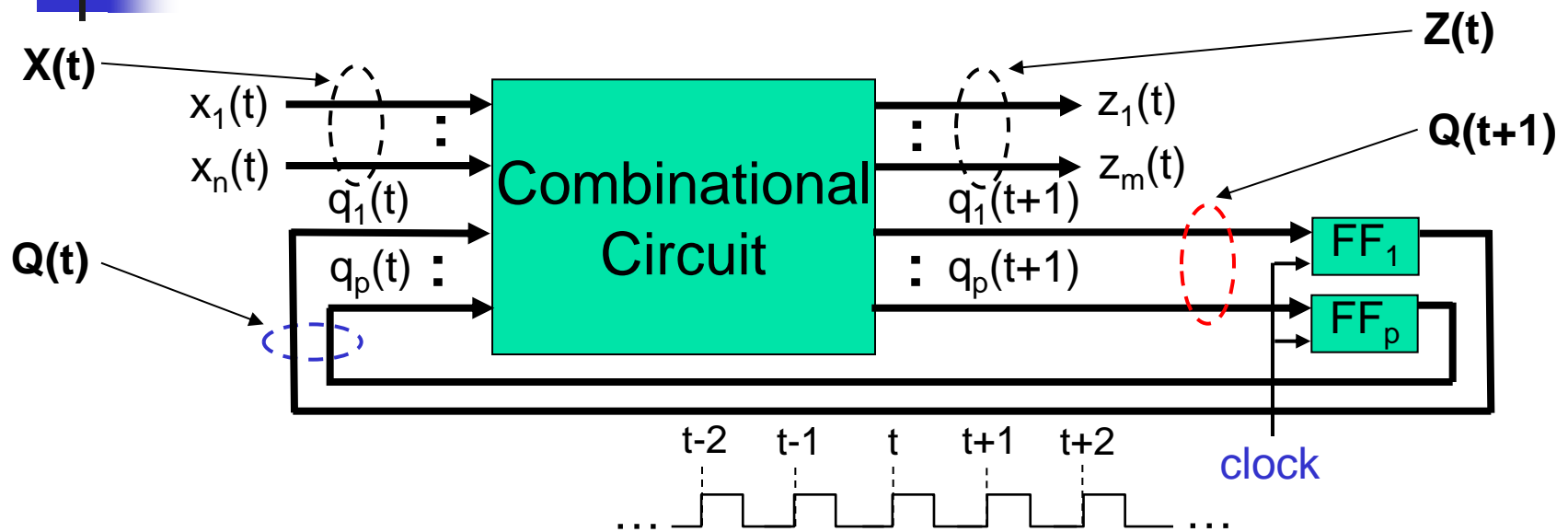Synchronous Sequential Circuits: Definitions and Notations (cont.)




- **Input Vector** $X(t) = (x_1(t), \dots, x_n(t))$ – the values at the inputs prior to the application of a clock pulse at time t .
- **Output Vector** $Z(t) = (z_1(t), \dots, z_m(t))$ – the values at the outputs prior to the application of a clock pulse at time t .
- **Present State** $Q(t) = (q_1(t), \dots, q_p(t))$ – the values stored by the Flip-Flops prior to the application of a clock pulse at time t .
- **Next State** $Q(t+1) = (q_1(t+1), \dots, q_p(t+1))$ – the values stored by the Flip-Flops after the application of a clock pulse at time t . In other words, **the state one clock period later**.



Sequential Circuit Representations

- Boolean Equations
 - Characteristic (Flip-Flop Input) Equations
 - Primary Output Equations
- State Table
- State Diagram

Characteristic (FF Input) Equations

 


- An algebraic representation used to fully specify the combinational logic that drives the inputs of the FFs.
- Set of Boolean Equations:

$$q_1(t+1) = f_1(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$

$$\vdots$$

$$q_p(t+1) = f_p(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$
- Short Notation: $Q(t+1) = F(X(t), Q(t))$
- The next state $Q(t+1)$ depends on the present state $Q(t)$ and the input vector $X(t)$.

Primary Output Equations

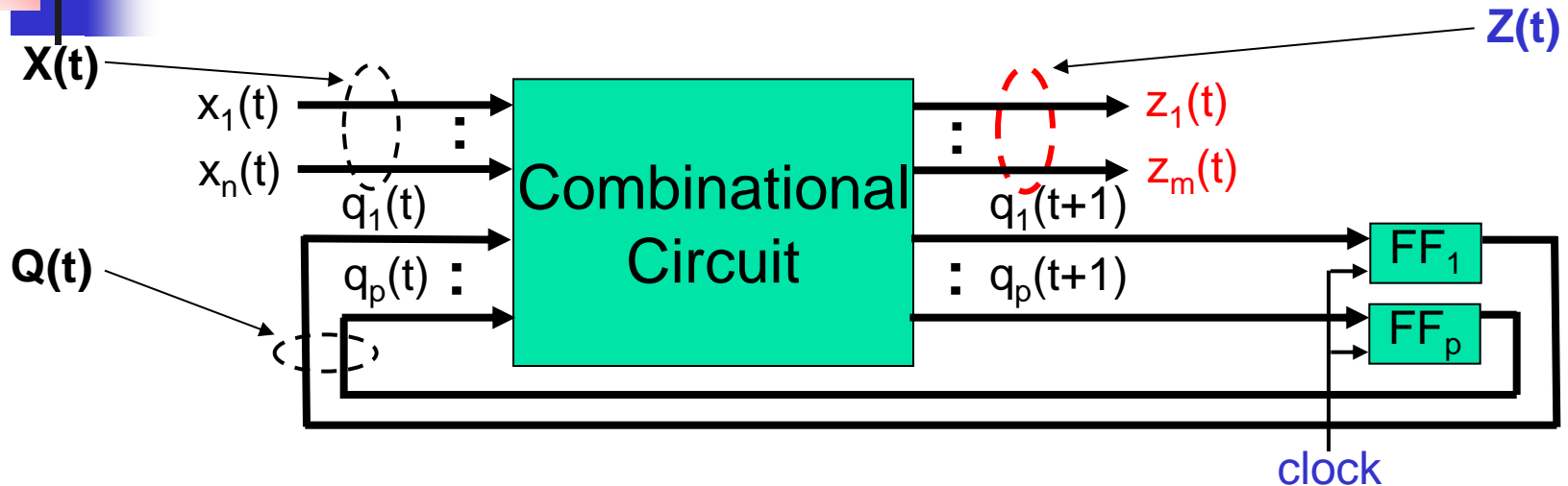

- An algebraic representation used to fully specify the combinational logic that defines the outputs of the circuit.
- Set of Boolean Equations:



$$z_1(t) = g_1(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$

$$\vdots$$

$$z_m(t) = g_m(x_1(t), \dots, x_n(t), q_1(t), \dots, q_p(t))$$
- Short Notation: $Z(t) = G(X(t), Q(t))$
- The output vector $Z(t)$ depends on the present state $Q(t)$ and the input vector $X(t)$.

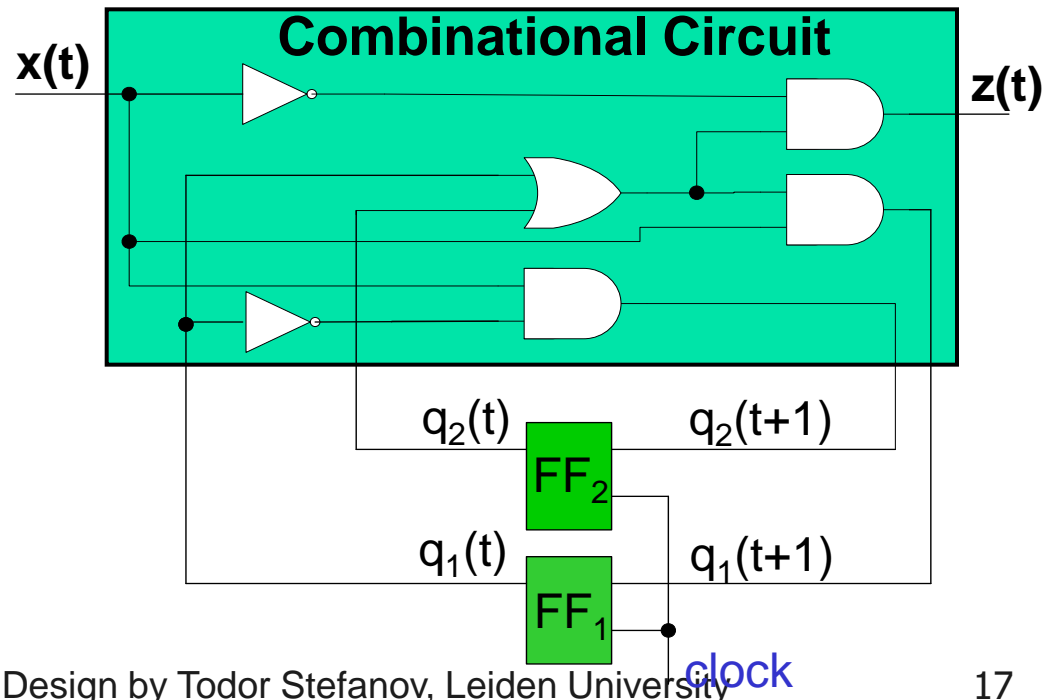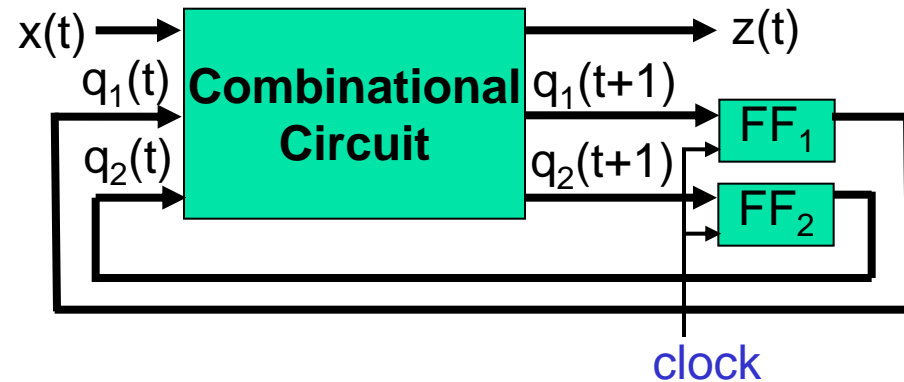
Example: Equations

- Consider simple sequential circuit:
 - 1 input , 1 output , 2 Flip-Flops
- Characteristic (FF input) equations:
 - $q_1(t+1) = f_1(x(t), q_1(t), q_2(t))$
 $= q_1(t) \cdot x(t) + q_2(t) \cdot x(t)$
 $= (q_1(t) + q_2(t)) \cdot x(t)$
 - $q_2(t+1) = f_2(x(t), q_1(t), q_2(t))$
 $= q_1(t)' \cdot x(t)$
- Primary output equations:
 - $z(t) = g(x(t), q_1(t), q_2(t))$
 $= q_1(t) \cdot x(t)' + q_2(t) \cdot x(t)$
 $= (q_1(t) + q_2(t)) \cdot x(t)'$



State Table

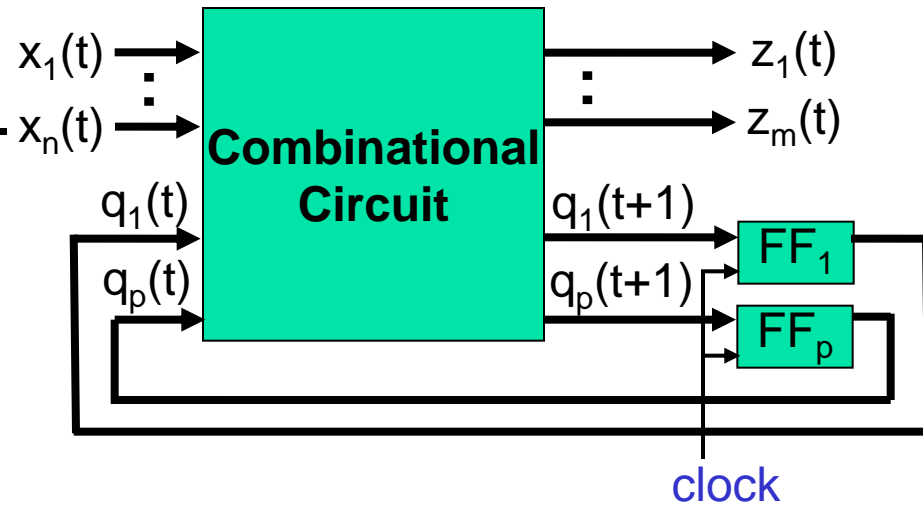- Enumerates the relationship between inputs, outputs, and states of the sequential circuit.
- Given a circuit with n inputs, m outputs, and p Flip-Flops:
 - The corresponding state table contains 2^{n+p} rows.
 - The corresponding state table contains $n+2p+m$ columns.



Inputs			Present State			Next State			Outputs		
$x_1(t)$...	$x_n(t)$	$q_1(t)$...	$q_p(t)$	$q_1(t+1)$...	$q_p(t+1)$	$z_1(t)$...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
...											
1	...	1	1	...	0						
1	...	1	1	...	1						

$n+p+p+m$


Example: State Table

- Consider previous example:
 - 1 input , 1 output , 2 Flip-Flops
- Equations:

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$

$$q_2(t+1) = x(t) \cdot q_1(t)'$$
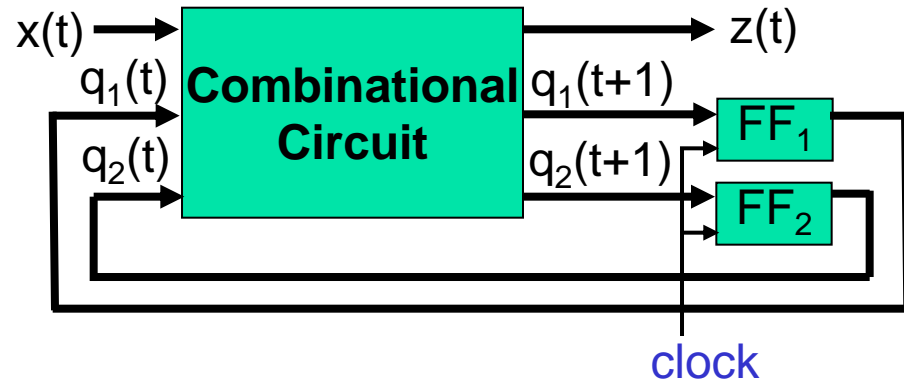
$$z(t) = x(t)' \cdot q_2(t) + x(t) \cdot q_1(t)$$



State Table

- $2^2 = 4$ states
 - Q1 = 00
 - Q2 = 01
 - Q3 = 10
 - Q4 = 11
- How do you read this table?

Inputs	Present State		Next State		Outputs
	x(t)	q ₁ (t)	q ₂ (t)	q ₁ (t+1)	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

State Table to/from Equations

■ State Table to Equations

- Treat the State Table as a Truth Table of Boolean functions to get the Characteristic and Primary Output Equations.
- You can derive the CSOP or CPOS form of the Equations directly using the **right part** of the State Table.
- You can simplify the Equations using algebraic manipulations or K-maps.

Inputs			Present State			Next State			Outputs		
$x_1(t)$...	$x_n(t)$	$q_1(t)$...	$q_p(t)$	$q_1(t+1)$...	$q_p(t+1)$	$z_1(t)$...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
...											
1	...	1	1	...	0						
1	...	1	1	...	1						

right part of the table

■ State Table from Equations

- The Characteristic and Primary Output Equations are Boolean functions.
- Represent the Equations in a common Truth Table. This is actually the State Table.

Example: State Table to Equations

Inputs $x(t)$	Present State		Next State		Outputs $z(t)$
	$q_1(t)$	$q_2(t)$	$q_1(t+1)$	$q_2(t+1)$	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

Equations in CSOP form

$$q_1(t+1) = x(t) \cdot q_1(t)' \cdot q_2(t) + x(t) \cdot q_1(t) \cdot q_2(t)' + x(t) \cdot q_1(t) \cdot q_2(t)$$

$$q_2(t+1) = x(t) \cdot q_1(t)' \cdot q_2(t)' + x(t) \cdot q_1(t)' \cdot q_2(t)$$

$$z(t) = x(t)' \cdot q_1(t)' \cdot q_2(t) + x(t)' \cdot q_1(t) \cdot q_2(t)' + x(t) \cdot q_1(t) \cdot q_2(t)$$

Simplified Equations



		q_1			
		q_1q_0	00	01	11
x	0				
	1		1	1	1
		q_2			

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$

		q_1			
		q_1q_0	00	01	11
x	0				
	1	1	1		
		q_2			


$$q_2(t+1) = x(t) \cdot q_1(t)'$$

		q_1			
		q_1q_0	00	01	11
x	0				
	1		1	1	1
		q_2			

$$z(t) = x(t)' \cdot q_2(t) + x(t)' \cdot q_1(t)$$

 Example: State Table from Equations

$$q_1(t+1) = x(t) \cdot q_2(t) + x(t) \cdot q_1(t)$$
$$q_2(t+1) = x(t) \cdot q_1(t)'$$
$$z(t) = x(t)' \cdot q_2(t) + x(t)' \cdot q_1(t)$$



Follow the procedure described below


Inputs		Present State		Next State		Outputs
x(t)		q ₁ (t)	q ₂ (t)	q ₁ (t+1)	q ₂ (t+1)	z(t)
0		0	0	0	0	0
0		0	1	0	0	1
0		1	0	0	0	1
0		1	1	0	0	1
1		0	0	0	1	0
1		0	1	1	1	0
1		1	0	1	0	0
1		1	1	1	0	0

- Identify the variables that are used on the right-hand side of the equations
 - x(t), q₁(t), and q₂(t) → 3 variables
- List all possible combinations of the above variables:
 - 2³ = 8 combinations
- For each combination evaluate the Equations:
 - Find the value of q₁(t+1), q₂(t+1), and z(t)

State Diagram

- Graph representation of a state table.



Inputs			Present State			Next State			Outputs		
$x_1(t)$...	$x_n(t)$	$q_1(t)$...	$q_p(t)$	$q_1(t+1)$...	$q_p(t+1)$	$z_1(t)$...	$x_m(t)$
0	...	0	0	...	0						
0	...	0	0	...	1						
1	...	1	1	...	0						
1	...	1	1	...	1						

 


- Graph **node** with label **Q** denotes state **Q**.
- Graph **edge** with label **X** denotes transition between two states when input **X** is applied.
- The graph has **2^p nodes** and **2^{n+p} edges**. Why?

  Example: State Diagram

- Possible states = { 00, 01, 10, 11 }
→ 4 nodes in the diagram
- Possible Transitions = #rows in table
→ 8 edges in the diagram



Inputs x(t)	Present State		Next State		Outputs z(t)
	q ₁ (t)	q ₂ (t)	q ₁ (t+1)	q ₂ (t+1)	
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	0

 

Reads as:


When at state **Q1** and apply vector **X**, we get output **Z** and proceed to state **Q2**.



Finite State Machines

- The synchronous sequential circuits also can be called **Finite State Machines (FSM)**. Why?
- A sequential circuit with p Flip-Flops
 - can have 2^p distinct states.
 - can have $2^p \times 2^p = 2^{2p}$ distinct transitions.
- So, it has **finite** number of distinct states and transitions, hence the name.
- FSM is also one of the so called **Models of Computation**.
- There are two types of FSM:
 - **Mealy** model FSM
 - **Moore** model FSM

Mealy Finite State Machine

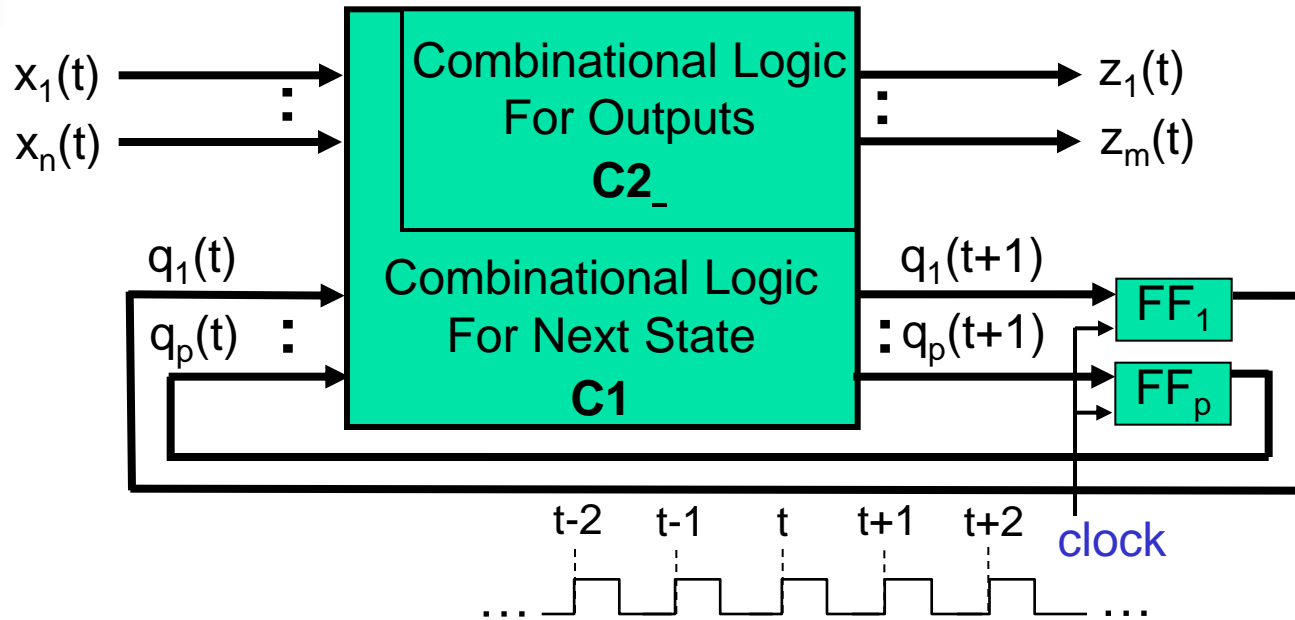



- Both outputs and next state depend directly on both primary inputs **AND** present state.

$$\begin{aligned}
 Q(t+1) &= C1(X(t), Q(t)) \\
 Z(t) &= C2(X(t), Q(t))
 \end{aligned}$$

- Outputs are **asynchronous**, i.e., they can change in response to any changes in the inputs, **independent** of the clock.

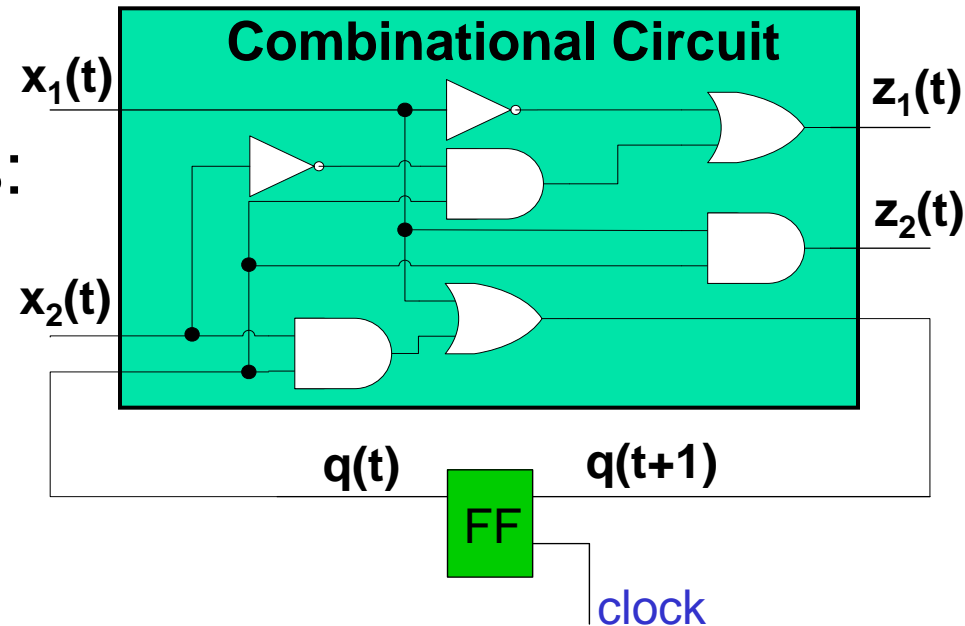 
Example: Mealy Machine

- Consider simple sequential circuit:
 - 2 input , 2 output , 1 Flip-Flop
- Characteristic (FF input) equations:
 - $q(t+1) = x_1(t) + x_2(t) \cdot q(t)$
- Primary output equations:
 - $z_1(t) = x_1(t)' + x_2(t)' \cdot q(t)$
 - $z_2(t) = x_1(t) \cdot q(t)$





 Example: Mealy Machine (cont.)

- Possible states = $\{0,1\}$, thus 2 nodes in state diagram
- Possible Transitions = #rows in the table, thus 8 edges in state diagram




Inputs		PS		NS	Outputs	
$x_1(t)$	$x_2(t)$	$q(t)$		$q(t+1)$	$z_1(t)$	$z_2(t)$
0	0	0		0	1	0
0	0	1		0	1	0
0	1	0		0	1	0
0	1	1		1	1	0
1	0	0		1	0	0
1	0	1		1	1	1
1	1	0		1	0	0
1	1	1		1	0	1

  

Reads as:
 When at state **Q1** and apply vector **X**,
 we get output **Z** and proceed to state **Q2**.

Moore Finite State Machine

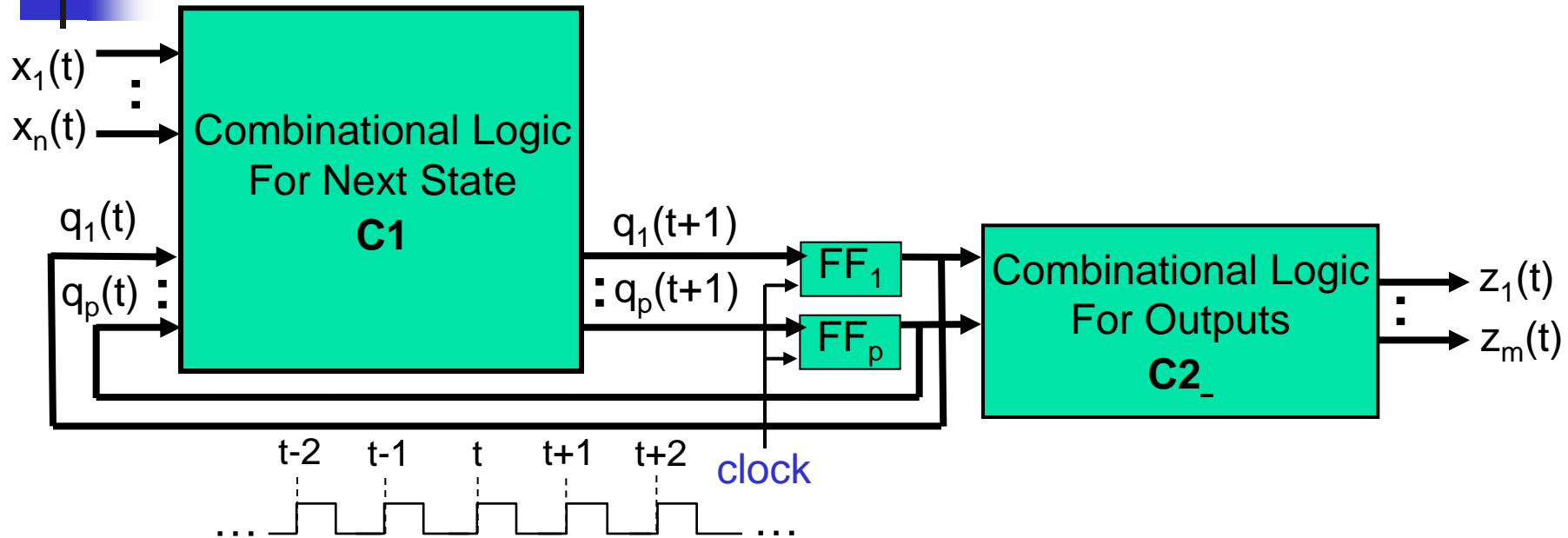



- Next state depends directly on both primary inputs **AND** present state. Outputs depend directly **only** on present state.

$$\begin{aligned} Q(t+1) &= C1(X(t), Q(t)) \\ Z(t) &= C2(Q(t)) = C2(C1(X(t-1), Q(t-1))) \end{aligned}$$

- Moore outputs are **synchronous** with the clock, only changing with state transitions.

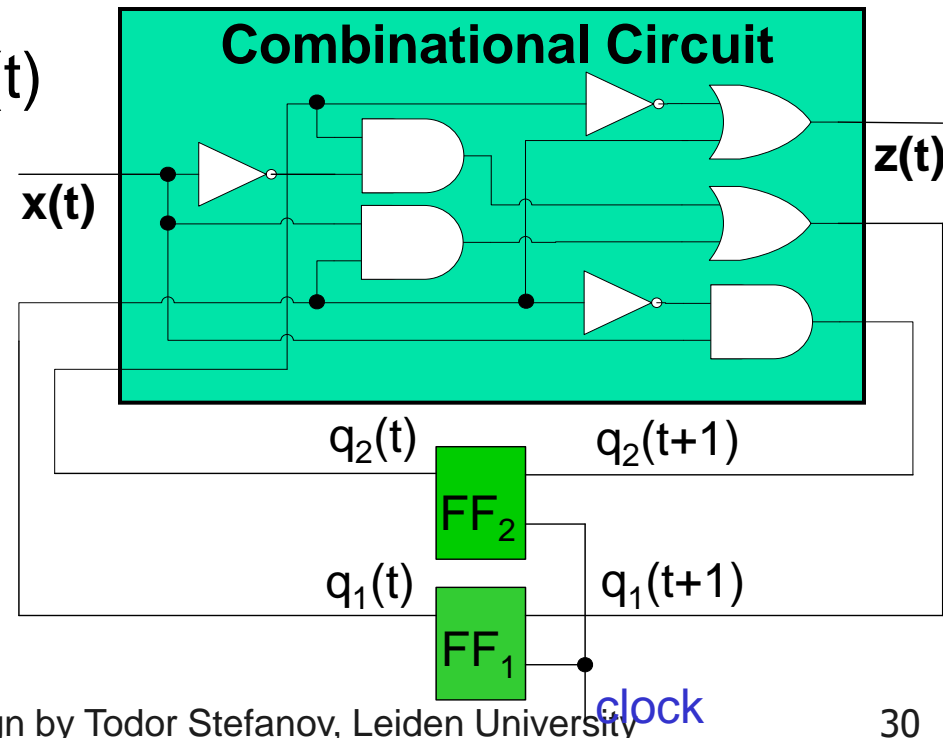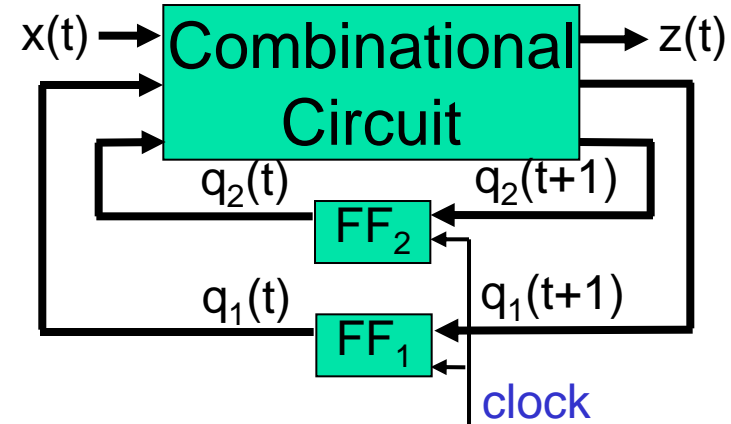Example: Moore Machine



- Consider simple sequential circuit:
 - 1 input , 1 output , 2 Flip-Flops
- Characteristic (FF input) equations:
 - $q_1(t+1) = x(t) \cdot q_1(t) + x(t)' \cdot q_2(t)$
 - $q_2(t+1) = x(t) \cdot q_1(t)'$
- Primary output equations:
 - $z(t) = q_1(t) + q_2(t)'$



Example: Moore Machine (cont.)

Inputs x(t)	Present State		Next State		Outputs z(t)
	q ₁ (t)	q ₂ (t)	q ₁ (t+1)	q ₂ (t+1)	
0	0	0	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	1	0	1
1	1	1	1	0	1

  - Possible states = { 00, 01, 10, 11 }
→ 4 nodes in the diagram
- Possible Transitions = #rows in table
→ 8 edges in the diagram





Reads as:


When at state **Q1** with output **Z1** and apply input **X**, we proceed to state **Q2** with output **Z2**.

Comparison of *Mealy* and *Moore* Machines

- Mealy Machines tend to have less states
 - Different outputs on arcs rather than on states
- Mealy Machines react faster to inputs
 - React in same cycle – don't need to wait for clock.
 - In Moore machines, more logic may be necessary to decode state into outputs – more gate delays after.
- Moore Machines are safer to use
 - Outputs change at clock edge (always one cycle later).
 - In Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur.

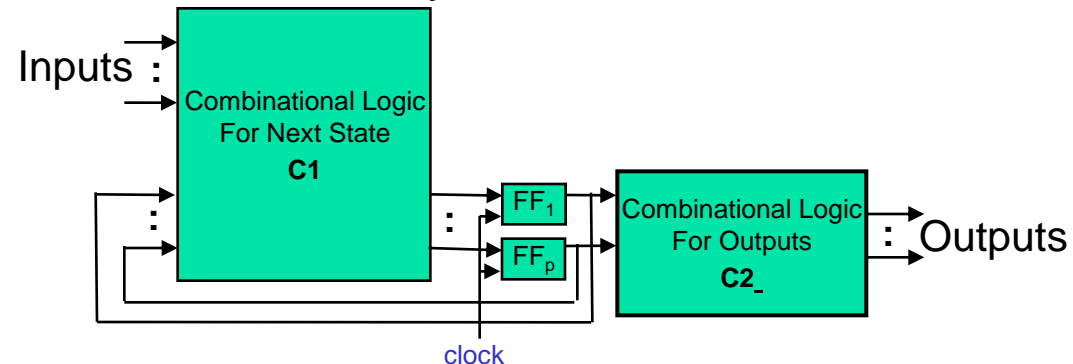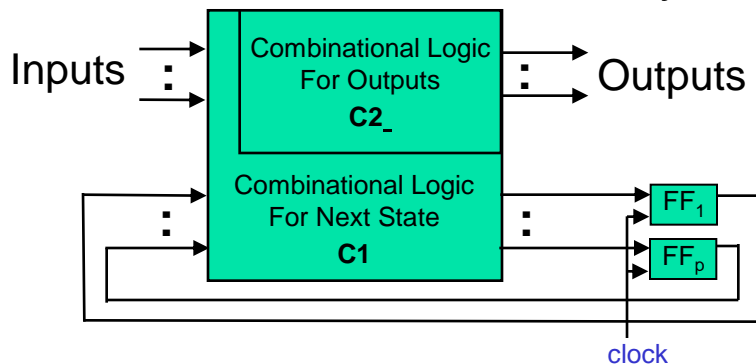

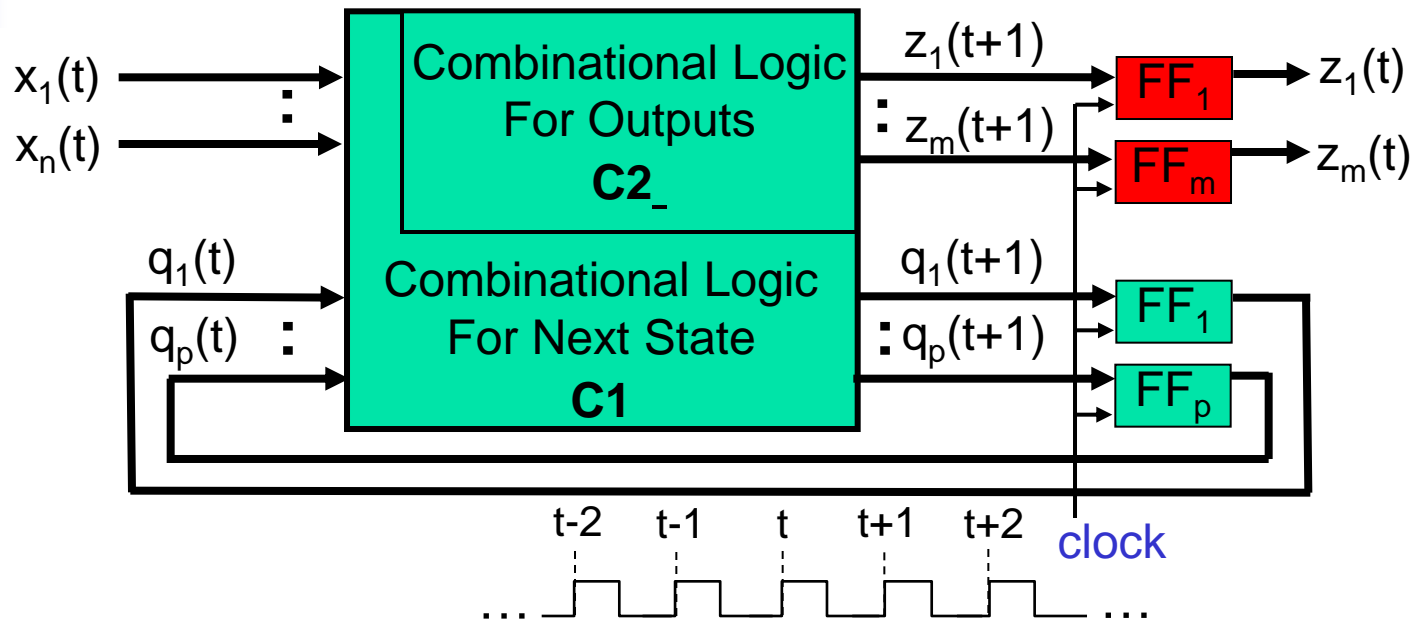Registered *Mealy* Machine (Really Moore)



- Synchronous (or registered) Mealy Machine
 - Registered outputs
 - Avoids “glitchy” outputs
- Registered Mealy Machine is actually Moore Machine. Why?
 - View outputs as expanded state vector
- So, we get Moore Machine with no output decoding