



# Sequential Circuits: Latches & Flip-Flops




# Overview

---

- Storage Elements
- Latches
  - SR, JK, D, and T
  - Characteristic Tables, Characteristic Equations, Execution Tables, and State Diagrams
  - Standard Symbols
- Flip-Flops
  - SR, JK, D, and T
  - Characteristic Tables, Characteristic Equations, Execution Tables, and State Diagrams
  - Standard Symbols
- Design of Latches/Flip-Flops using a given Latch/Flip-Flop
- Implementing Latches using Logic Gates
  - SR Latch Design using Logic Gates
  - D Latch Design using Logic Gates
- Implementing Flip-Flops using Latches
  - D Flip-Flop Design based on SR Latch and D Latch
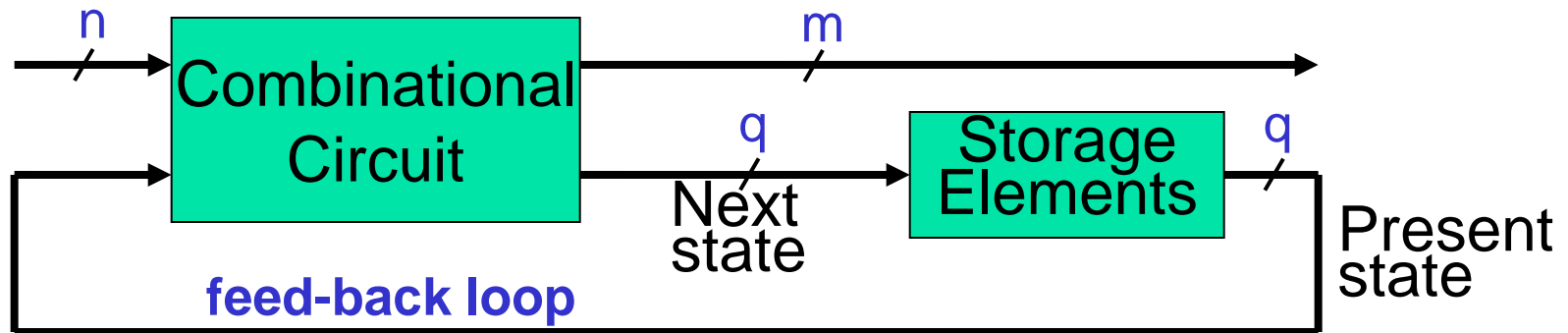
# Storage Elements

- Sequential Circuits contain **Storage Elements** that keep the state of the circuit.



- One storage element can store one bit of information.
- A one-bit storage element should have at least three properties:
  - It should be able to **hold** a single bit, 0 or 1 (**storage mode**).
  - You should be able to **read** the bit that was stored.
  - You should be able to **change** the value. Since there's only a single bit, there are only two choices:
    - Set** the bit to 1
    - Reset**, or **clear**, the bit to 0.


# Storage Elements (cont.)

- Two types of storage elements are used in Sequential Circuits: **Latches** and **Flip-Flops**.

- Latches (SR, JK, D, T)**

- General description of a latch:

 
- 1-bit storage device with several inputs ( $\mathbf{X}$ ) and an output ( $\mathbf{Q}$ ).
- Output is changed  $\mathbf{Q} = f(\mathbf{X})$  only when **specific combinations** occur at the inputs  $\mathbf{X}$ ; otherwise the output remains unchanged (storage mode).



- Flip-Flops (SR, JK, D, T)**


- General description of a Flip-Flop:

 - 1-bit storage device with several inputs ( $\mathbf{X}$ ), an output ( $\mathbf{Q}$ ), and a specific **trigger** input ( $\mathbf{CLK}$ ).
- Output is changed  $\mathbf{Q} = f(\mathbf{X})$  on **response of a pulse at the trigger input  $\mathbf{CLK}$  (on the rising or falling edge of the pulse)**. When a pulse is absent at input  $\mathbf{CLK}$  the output remains unchanged (storage mode).



# SR Latch

## Symbol

 

## Function Table

C	S(t)	R(t)	Q(t)	Q(t+1)	Operation
1	0	0	0	0	No change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	?	Undefined
1	1	1	1	?	
0	x	x	x	Q(t)	No change


## Characteristic Table

S(t)	R(t)	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x


## Execution Table

Q(t)	Q(t+1)	S(t)	R(t)
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

## State Diagram

 


## Characteristic Equation

 

# JK Latch

## Symbol

 

## Function Table

C	J(t)	K(t)	Q(t)	Q(t+1)	Operation
1	0	0	0	0	No change
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	1	Complement
1	1	1	1	0	
0	x	x	x	Q(t)	No change


## Characteristic Table

J(t)	K(t)	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


## Execution Table

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

## State Diagram

 


## Characteristic Equation

 

$$Q(t+1) = J(t) \cdot Q(t)' + K(t)' \cdot Q(t)$$

# D Latch

## Symbol

 

Function Table			
C	D(t)	Q(t)	Q(t+1)
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1
0	x	x	Q(t)

Operation

Propagate input D

No change


## Characteristic Table

D(t)	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1


## Execution Table

Q(t)	Q(t+1)	D(t)
0	0	0
0	1	1
1	0	0
1	1	1

## State Diagram

 


## Characteristic Equation

 

# T Latch

## Symbol

 


Function Table			
C	T(t)	Q(t)	Q(t+1)
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0
0	x	x	Q(t)

Characteristic Table		
T(t)	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

## Execution Table

Q(t)	Q(t+1)	T(t)
0	0	0
0	1	1
1	0	1
1	1	0

## State Diagram

 

## Characteristic Equation


		Q(t)
		1
T(t)	1	
	0	

$$Q(t+1) = T(t) \oplus Q(t)$$



 
# Standard Symbols for Latches

- We have seen that a Latch can change state if there is an active level on the control input **C**.
- Logic-1 active level Latches:
  - Latch can change state if **C** = Logic-1
  - Standard symbols for Logic-1 active level Latches:




 - Logic-0 active level Latches:
  - Latch can change state if **C** = Logic-0
  - Standard symbols for Logic-0 active level Latches:



# SR Flip-Flop

## Symbol

 

↑ - rising edge

↘ - 1 or 0 or falling edge

## Function Table

CLK	S(t)	R(t)	Q(t)	Q(t+1)	Operation
↑	0	0	0	0	No change
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	?	Undefined
↑	1	1	1	?	
↘	x	x	x	Q(t)	No change


## Characteristic Table

S(t)	R(t)	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x


## Execution Table

Q(t)	Q(t+1)	S(t)	R(t)
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

## State Diagram

 


## Characteristic Equation

 

# JK Flip-Flop

## Symbol

 

↑ - rising edge

↘ - 1 or 0 or falling edge

## Function Table

CLK	J(t)	K(t)	Q(t)	Q(t+1)	Operation
↑	0	0	0	0	No change
↑	0	0	1	1	
↑	0	1	0	0	Reset
↑	0	1	1	0	
↑	1	0	0	1	Set
↑	1	0	1	1	
↑	1	1	0	1	Complement
↑	1	1	1	0	
↘	x	x	x	Q(t)	No change


## Characteristic Table

J(t)	K(t)	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


## Execution Table

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

## State Diagram

 


## Characteristic Equation

 

$$Q(t+1) = J(t) \cdot Q(t)' + K(t)' \cdot Q(t)$$

# D Flip-Flop

## Symbol

 

↑ - rising edge

↘ - 1 or 0 or falling edge

Function Table			
CLK	D(t)	Q(t)	Q(t+1)
↑	0	0	0
↑	0	1	0
↑	1	0	1
↑	1	1	1
↘	x	x	Q(t)

Characteristic Table		
D(t)	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

Operation


Propagate input D

No change


## Execution Table

Q(t)	Q(t+1)	D(t)
0	0	0
0	1	1
1	0	0
1	1	1

## State Diagram

 


## Characteristic Equation

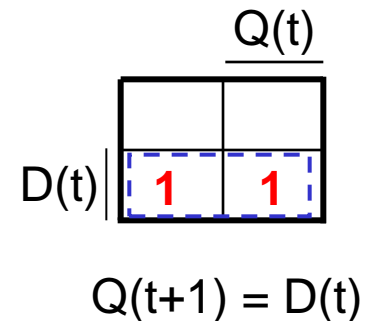

# T Flip-Flop

## Symbol

 

↑ - rising edge

↘ - 1 or 0 or falling edge


Function Table			
CLK	T(t)	Q(t)	Q(t+1)
↑	0	0	0
↑	0	1	1
↑	1	0	1
↑	1	1	0
↘	x	x	Q(t)

Characteristic Table		
T(t)	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

## Execution Table

Q(t)	Q(t+1)	T(t)
0	0	0
0	1	1
1	0	1
1	1	0

## State Diagram

 


## Characteristic Equation

		Q(t)	
		0	1
T(t)	0	0	1
	1	1	0


$$Q(t+1) = T(t) \oplus Q(t)$$
 
# Standard Symbols for Flip-Flops

- We have seen that a Flip-Flop can change state, **only** during a **transition** of the trigger input **CLK (Edge-Triggered)**.
- Rising-Edge Triggered Flip-Flops:
  - Flip-Flop can change state only during **0-to-1 transition** on **CLK**
  - Standard symbols for **Rising-Edge** triggered Flip-Flops:




 - Falling-Edge Triggered Flip-Flops:
  - Flip-Flop can change state only during **1-to-0 transition** on **CLK**
  - Standard symbols for **Falling-Edge** triggered Flip-Flops :


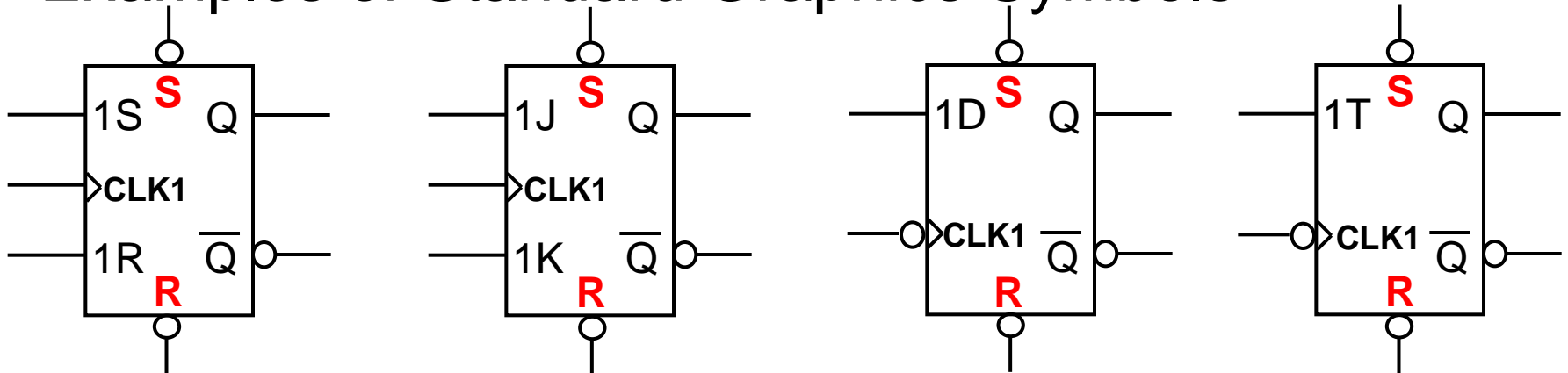
# Asynchronous Set/Reset of Flip-Flops


- Many times it is desirable to **asynchronously** (i.e., independent of the clock) **set** or **reset** FFs.
  - Asynchronous set is called **direct set** or **Preset**
  - Asynchronous reset is called **direct reset** or **Clear**
- Example: At power-up so that we can start from a known state.
- Examples of Standard Graphics Symbols



NOTE: CLK<sub>n</sub> indicates that CLK<sub>n</sub> controls all inputs whose label starts with n. Hence, CLK<sub>n</sub> does **NOT** control **S** and **R** (**S** and **R** have Logic-0 active level).
 
# Asynchronous Set/Reset: Example

- JK Flip-Flop with asynchronous set & reset.



IEEE standard graphics symbol for JK-FF with direct set & reset

Function Table							
S	R	CLK	J(t)	K(t)	Q(t)	Q(t+1)	Operation
1	1	↑	0	0	0	0	No change
1	1	↑	0	0	1	1	
1	1	↑	0	1	0	0	Reset
1	1	↑	0	1	1	0	Set
1	1	↑	1	0	0	1	
1	1	↑	1	0	1	1	Complement
1	1	↑	1	1	0	1	
1	1	↑	1	1	1	0	No change
1	1	↓	x	x	x	Q(t)	
0	1	x	x	x	x	1	Asynch. Preset
1	0	x	x	x	x	0	Asynch. Clear
0	0	x	x	x	x	?	Undefined

Independent of CLK

**NOTE:** Characteristic Table, Characteristic Equation, Execution Table, and State Diagram are **the same as** for the normal JK Flip-Flop (without direct set & reset).





# Latches & Flip-Flops

---

- The Latches are **Level-triggered** whereas the Flip-Flops are **Edge-triggered**.
- **SR** Latch and **SR** Flip-Flop **have the same** Characteristic Table, Characteristic Equation, Execution Table, and State Diagram.
- The above is valid for the other pairs: ***JK Latch – JK Flip-Flop, D Latch – D Flip-Flop, T Latch – T Flip-Flop.***
- Given a Latch of type **X** (**X** is SR or JK or D or T), **any other type of Latch can be designed using X.**
- Given a Flip-Flop of type **X** (**X** is SR or JK or D or T), **any other type of Flip-Flop can be designed using X.**




# Design Procedure

---

- The procedure to design Latches with a given Latch of type  $X$  **is the same as** the procedure to design Flip-Flops with a given Flip-Flop of type  $X$ .
- So, I will **illustrate** the design procedure for Flip-Flops.
- Given  $D$  Flip-Flop, design:
  - $SR$  Flip-Flop,  $JK$  Flip-Flop, and  $T$  Flip-Flop (see this lecture)
- Given  $SR$  Flip-Flop, design:
  - $D$  Flip-Flop (see this lecture)
  - $JK$  Flip-Flop, and  $T$  Flip-Flop (see homework 7)
- Given  $JK$  Flip-Flop, design:
  - $SR$  Flip-Flop,  $D$  Flip-Flop (see homework 7)
  - $T$  Flip-Flop (try at home)
- Given  $T$  Flip-Flop, design:
  - $SR$  Flip-Flop,  $JK$  Flip-Flop, and  $D$  Flip-Flop (try at home)


# SR Flip-Flop with D Flip-Flop

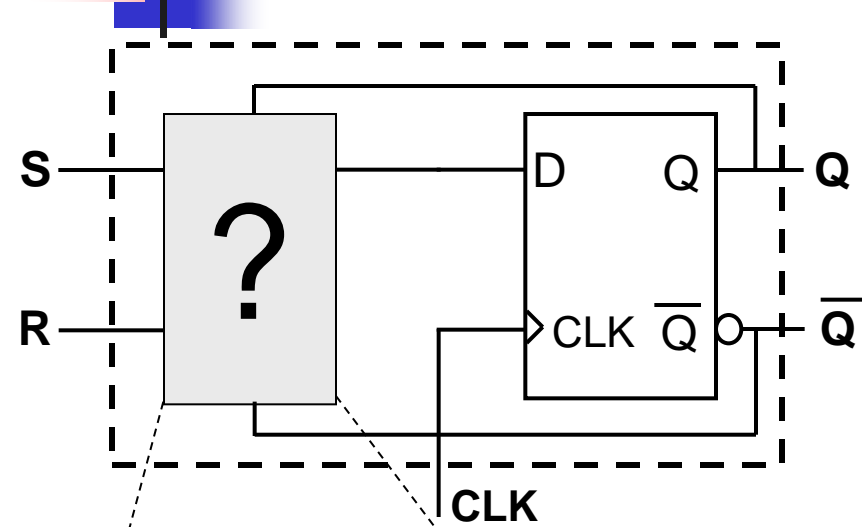

Determine D using the Execution Table for D

Characteristic Table SR



S(t)	R(t)	Q(t)	Q(t+1)	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	?	X
1	1	1	?	X

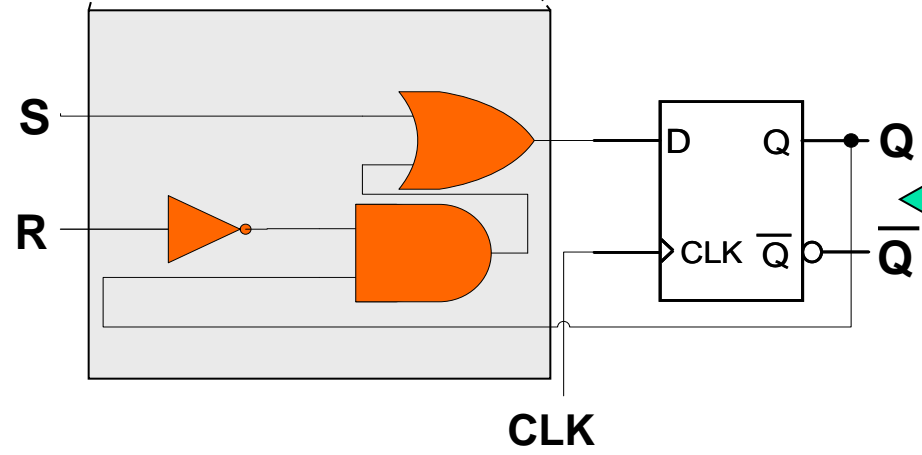

	R(t)			
	0	1	0	1
S(t)	1	1	X	X
	Q(t)			
	0	1	0	1

$$D = S(t) + R(t)' \cdot Q(t)$$


# JK Flip-Flop with D Flip-Flop

 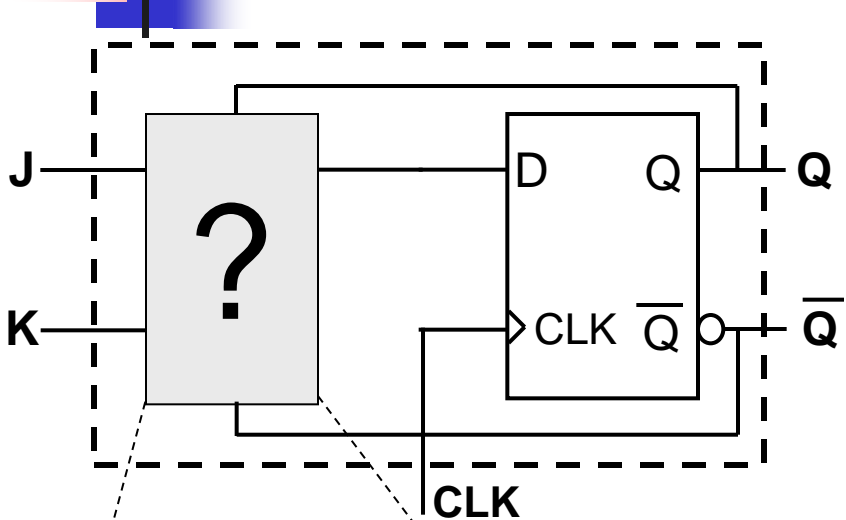

Determine D using the Execution Table for D


Characteristic Table JK

J(t)	K(t)	Q(t)	Q(t+1)	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

 

$$D = J(t) \cdot Q(t)' + K(t)' \cdot Q(t)$$


# T Flip-Flop with D Flip-Flop

 

Determine D using the Execution Table for D

Characteristic Table T


T	Q(t)	Q(t+1)	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

 

	Q(t)	
		1
T(t)	1	

**$D = T(t) \oplus Q(t)$**


# D Flip-Flop with SR Flip-Flop

 

Determine S and R using the Execution Table for SR

Characteristic Table D

D	Q(t)	Q(t+1)	S	R
0	0	0	0	x
0	1	0	0	1
1	0	1	1	0
1	1	1	x	0

 


D(t)	Q(t)
	0
	1

**S = D(t)**

D(t)	Q(t)
	0
	1

**R = D'(t)**




# T Flip-Flop with JK Flip-Flop

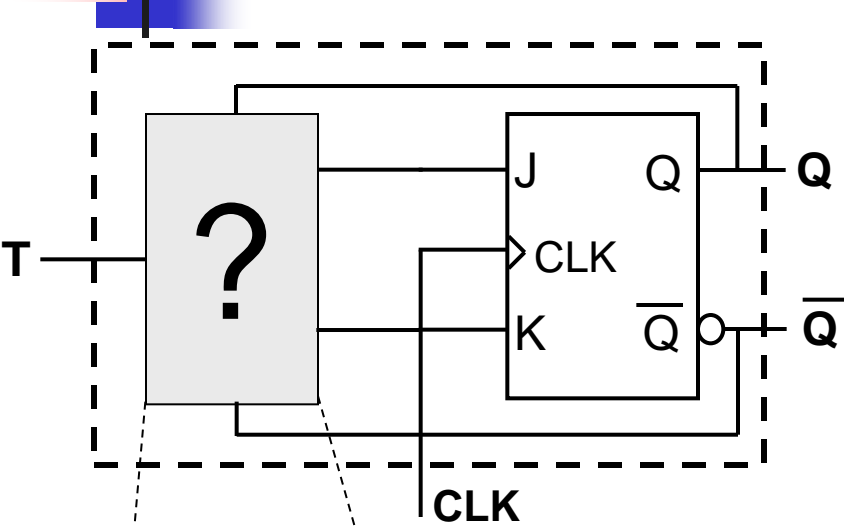


Determine J and K using the Execution Table for JK

Characteristic Table T

T	Q(t)	Q(t+1)	J	K
0	0	0	0	x
0	1	1	x	0
1	0	1	1	x
1	1	0	x	1

   



# SR Flip-Flop with T Flip-Flop

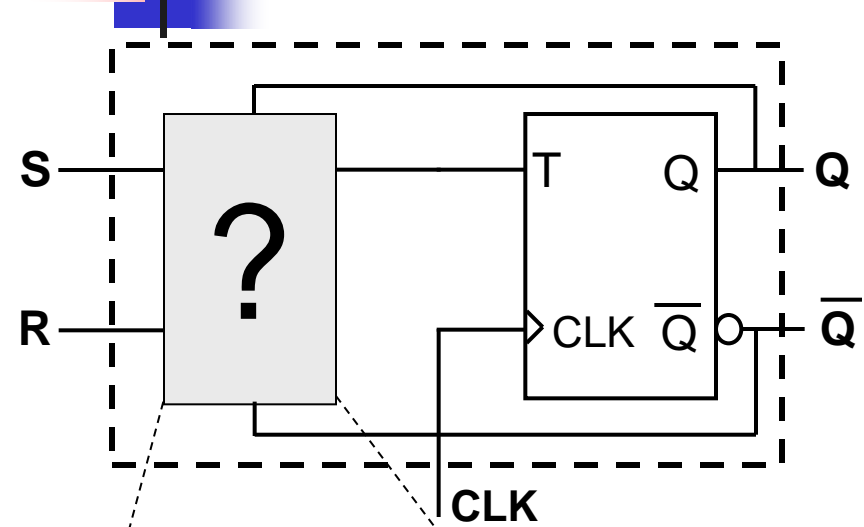

Determine T using the Execution Table for T

Characteristic Table SR



S(t)	R(t)	Q(t)	Q(t+1)	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	?	x
1	1	1	?	x

 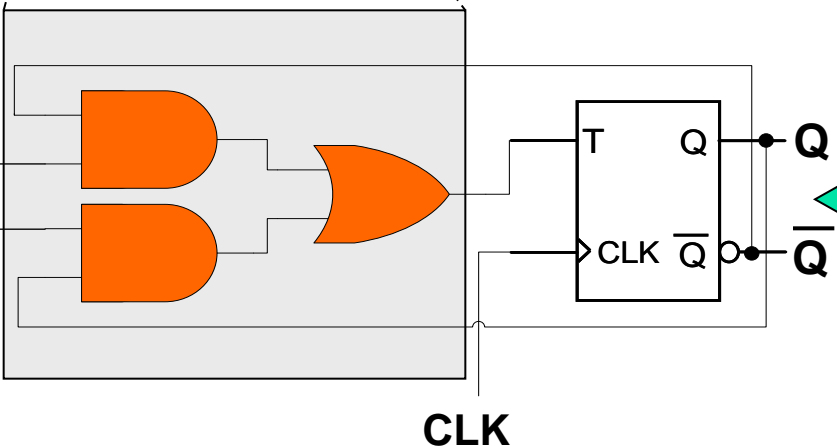

$$T = S(t) \cdot Q(t)' + R(t) \cdot Q(t)$$




# JK Flip-Flop with T Flip-Flop

 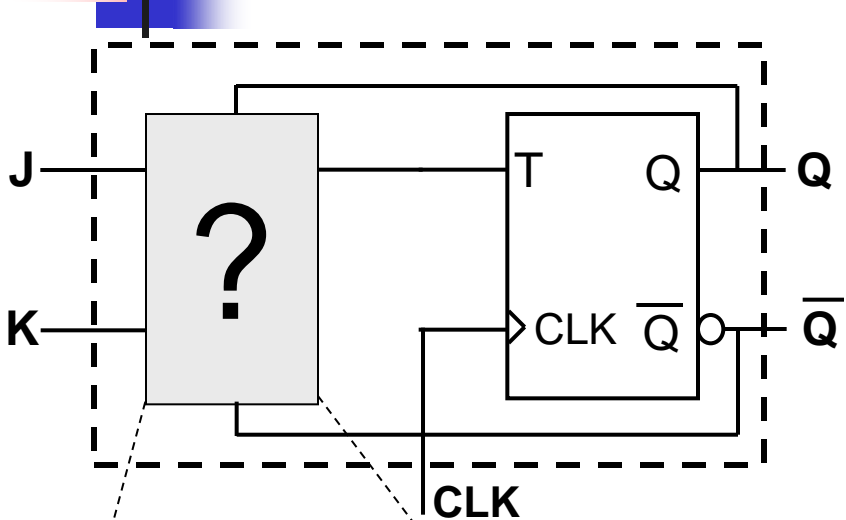

Determine T using the Execution Table for T


Characteristic Table JK

J(t)	K(t)	Q(t)	Q(t+1)	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

 

$$T = J(t) \cdot Q(t)' + K(t) \cdot Q(t)$$



# D Flip-Flop with T Flip-Flop

 

Determine T using the Execution Table for T

Characteristic Table D

D	Q(t)	Q(t+1)	T
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

  

# Implementing Latches & Flip-Flops

- We have seen so far that we can design **any other** Latch/Flip-Flop with a given Latch/Flip-Flop.
- To do this we need **to implement at least one** Latch and one Flip-Flop using **gates** (transistors).
- Historically, first **SR Latch** has been implemented using gates (transistors) – **next slides will show you how!**
- **D Latch** can be implemented using SR Latch (**you already know how to do it!**).
- **D Flip-Flop** can be implemented using SR Latch and D Latch - **next slides will show you how!**
- Given D Latch we can implement JK Latch and T Latch (**you already know how to do it!**).
- Given D Flip-Flop we can implement SR, JK, and T Flip-Flops (**you already know how to do it!**).






# What exactly is storage (memory)?

---

- A memory should have at least three properties.
  1. It should be able to hold a value.
  2. You should be able to *read* the value that was stored.
  3. You should be able to *change* the value that is stored.
- We'll start with the simplest case, a one-bit memory.
  1. It should be able to hold a single bit, 0 or 1.
  2. You should be able to read the bit that was saved.
  3. You should be able to change the value. Since there's only a single bit, there are only two choices:
    - **Set** the bit to 1
    - **Reset**, or **clear**, the bit to 0.
   
# The Basic Idea of a Storage Element


- How can a circuit “remember” anything, when it’s just a bunch of gates that produce outputs according to the inputs?
- The basic idea is **to make a loop**, so the circuit outputs are also inputs.
- Here is one initial attempt:



- Does this satisfy the properties of storage?
  - These circuits “remember” Q, because its value never changes. (Similarly, Q’ never changes either.)
  - We can also “read” Q, by attaching a probe or another circuit.
  - But **we can not change Q!** There are no external inputs here, so we can not control whether Q=1 or Q=0.
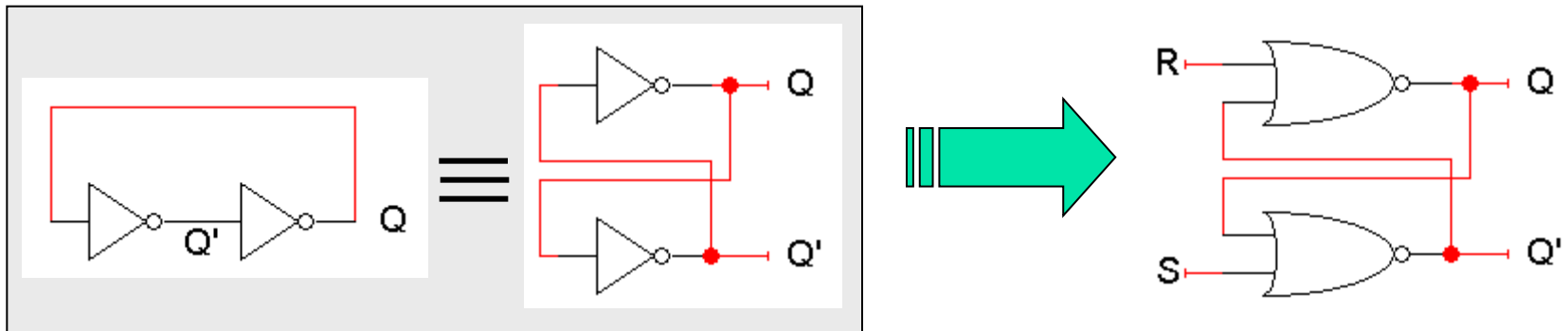
# SR Latch Design using Logic Gates

- Let us use NOR gates instead of inverters.
- The circuit is called **SR latch**. It has two inputs S and R, which will let us control the outputs Q and Q'.



- Here Q and Q' feed back into the circuit. They are not only outputs, they are also inputs!
- To figure out how Q and Q' change, we have to look at not only the inputs S and R, but also the *current* values of Q and Q':

$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$

$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$

- Let's see how different input values for S and R affect this circuit.


# Storing a Value: SR = 00

- What if  $S = 0$  and  $R = 0$ ?
- The equations on the right reduce to:

$$Q_{\text{next}} = (0 + Q'_{\text{current}})' = Q_{\text{current}}$$

$$Q'_{\text{next}} = (0 + Q_{\text{current}})' = Q'_{\text{current}}$$

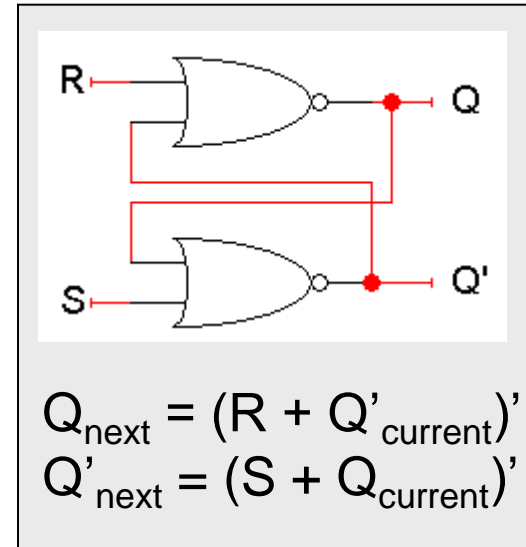- So, when  $SR = 00$ , then  $Q_{\text{next}} = Q_{\text{current}}$ . Whatever value  $Q$  has, it keeps.
- This is exactly what we need to **store** values in the latch.



# Setting The Latch: SR = 10


- What if  $S = 1$  and  $R = 0$ ?
- Since  $S = 1$ ,  $Q'_{\text{next}}$  is 0, *regardless* of  $Q_{\text{current}}$ :

$$Q'_{\text{next}} = (1 + Q_{\text{current}})' = 0$$

- Then, this new value of  $Q'$  goes into the top NOR gate, along with  $R = 0$ .

$$Q_{\text{next}} = (0 + 0)' = 1$$

 - So when  $SR = 10$ , then  $Q'_{\text{next}} = 0$  and  $Q_{\text{next}} = 1$ .
- This is how you set the latch to 1. The  $S$  input stands for “set.”
- Notice that it can take up to two steps (two gate delays) from the time  $S$  becomes 1 to the time  $Q_{\text{next}}$  becomes 1.
- But once  $Q_{\text{next}}$  becomes 1, the outputs will stop changing. This is a stable state.







# Latch Delays

- Timing diagrams are especially useful in understanding how circuits work.
- Here is a diagram which shows an example of how our latch outputs change with inputs  $SR=10$ .

 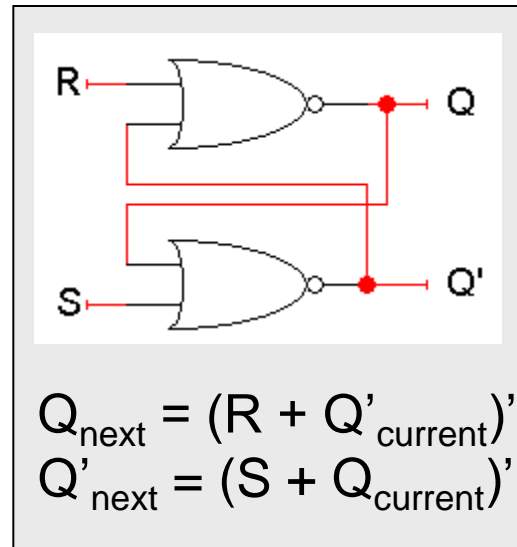0. Suppose that initially,  $Q = 0$  and  $Q' = 1$ .
1. Since  $S=1$ ,  $Q'$  will change from 1 to 0 after one NOR-gate delay (marked by vertical lines in the diagram for clarity).
2. This change in  $Q'$ , along with  $R=0$ , causes  $Q$  to become 1 after another gate delay.
3. The latch then stabilizes until  $S$  or  $R$  change again.



# Resetting The Latch: $SR = 01$


- What if  $S = 0$  and  $R = 1$ ?
- Since  $R = 1$ ,  $Q_{\text{next}}$  is 0, *regardless* of  $Q_{\text{current}}$ :

$$Q_{\text{next}} = (1 + Q'_{\text{current}})' = 0$$

- Then, this new value of  $Q$  goes into the bottom NOR gate, where  $S = 0$ .

$$Q'_{\text{next}} = (0 + 0)' = 1$$

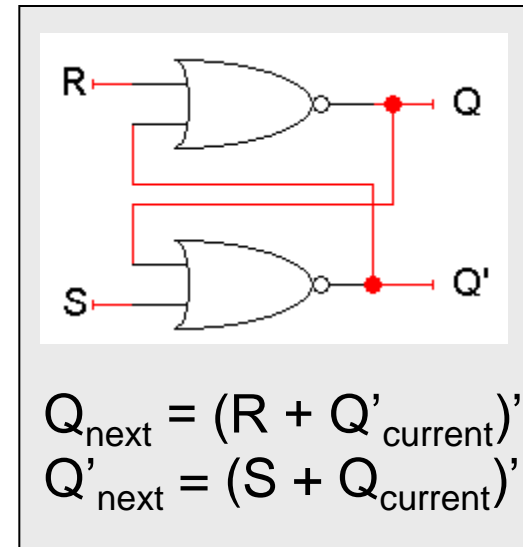- So when  $SR = 01$ , then  $Q_{\text{next}} = 0$  and  $Q'_{\text{next}} = 1$ .
- This is how you reset, or clear, the latch to 0. The  $R$  input stands for “reset.”
- Again, it can take two gate delays before a change in  $R$  propagates to the output  $Q'_{\text{next}}$ .



# What about $SR = 11$ ?

- Both  $Q_{\text{next}}$  and  $Q'_{\text{next}}$  will become 0.
- This contradicts the assumption that  $Q$  and  $Q'$  are always complements.
- Another problem is what happens if we then make  $S = 0$  and  $R = 0$  together.

$$Q_{\text{next}} = (0 + 0)' = 1$$

$$Q'_{\text{next}} = (0 + 0)' = 1$$



- But these new values go back into the NOR gates, and in the next step we get:

$$Q_{\text{next}} = (0 + 1)' = 0$$

$$Q'_{\text{next}} = (0 + 1)' = 0$$

- The circuit enters an infinite loop, where  $Q$  and  $Q'$  cycle between 0 and 1 forever.
- This is actually the worst case, but the moral is do not ever set  $SR=11$ !**
  
$$Q_{\text{next}} = (R + Q'_{\text{current}})'$$
$$Q'_{\text{next}} = (S + Q_{\text{current}})'$$



# SR latch: Summary


- SR latch is indeed 1-bit memory. Why?

- We can store the present value
- We can set it to 1
- We can reset it to 0

S	R	Q
0	0	No change
0	1	0 (reset)
1	0	1 (set)
1	1	Undefined!

- SR latch is a simple **asynchronous** sequential circuit. Why?

 
- It is made of gates with **feed-back loops**



- The output Q represents the data stored in the latch. It is sometimes called the **state** of the latch.
 
# S'R' latch Design using Logic Gates

- There are several varieties of latches.
- You can use NAND instead of NOR gates to get a **S'R' latch**.




S'	R'	Q
1	1	No change
1	0	0 (reset)
0	1	1 (set)
0	0	Undefined!

- This is just like an SR latch, but with inverted inputs, as you can see from the table.
- You can derive this table by writing equations for the outputs in terms of the inputs and the current state, just as we did for the SR latch.
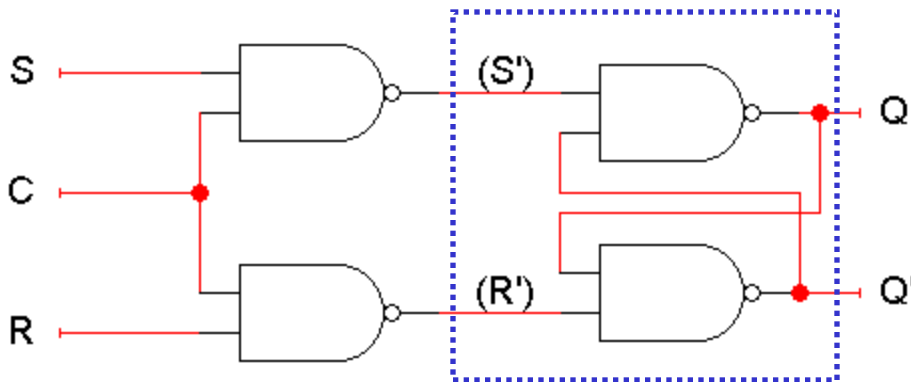
# SR Latch with a Control Input

- Here is SR latch with a control input C. It is based on an S'R' latch. The additional gates generate the S' and R' signals, based on inputs S and R and C ("control").




C	S	R	S'	R'	Q
0	x	x	1	1	No change
1	0	0	1	1	No change
1	0	1	1	0	0 (reset)
1	1	0	0	1	1 (set)
1	1	1	0	0	Undefined

- Notice the hierarchical design!
  - The dotted blue box is the S'R' latch from the previous slide.
  - The additional NAND gates are simply used to generate the correct inputs for the S'R' latch.
- The control input acts just like an enable.
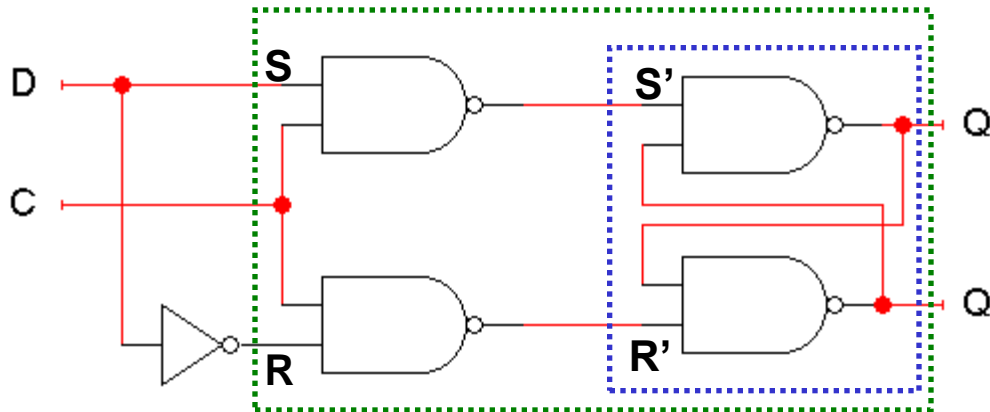
# D Latch Design using Logic Gates

- Finally, a D latch is based on an SR latch. The additional inverter generates the R signal, based on input D (“data”).
  - When  $C = 0$ ,  $S'$  and  $R'$  are both 1, so the state  $Q$  does not change.
  - When  $C = 1$ , the latch output  $Q$  will equal the input  $D$ .
- No more messing with one input for set and another input for reset!



C	D	Q
0	x	No change
1	0	0
1	1	1

- Also, this latch has no “bad” input combinations to avoid. Any of the four possible assignments to  $C$  and  $D$  are valid.



# Latches: Behaviour & Issues


---

- **Level** triggered
- Latches are “**transparent**”, i.e., any change on the inputs is seen at the outputs immediately.
- This causes **synchronization problems!** (not recommended for use in synchronous designs)
- **Solution:** use latches to create **Flip-Flops** that can respond (update) **ONLY** at **SPECIFIC** times (instead of ANY time).
- The specific times are the rising or falling edge of a clock signal.
- Thus, **Flip-Flops** are **Edge** triggered and used in synchronous design.



 
# D Flip-Flop Design using Latches

- Here is the internal structure of a **D flip-flop**.
  - The flip-flop inputs are C and D, and the outputs are Q and Q'.
  - The D latch on the left is the **master**, while the SR latch on the right is called the **slave**.




- Note the layout here (Master-Slave structure).
  - The flip-flop input D is connected directly to the master latch.
  - The master latch output goes to the slave.
  - The flip-flop outputs come directly from the slave latch.

# D Flip-Flop Behavior

 

- The D flip-flop's control input C enables *either* the D latch or the SR latch, but not both.
- When C = 0:
  - The master D latch is enabled. Whenever D changes, the master's output changes too.
  - The slave is disabled, so the D latch output has no effect on it. Thus, the slave just maintains the flip-flop's current state.
- As soon as C becomes 1:
  - The master is disabled. Its output will be the *last* D input value seen just before C became 1.
  - Any subsequent changes to the D input while C = 1 have no effect on the master latch, which is now disabled.
  - The slave latch is enabled. Its state changes to reflect the master's output.

# D Flip-Flop Behavior (cont.)

 

- Based on the behavior described in previous slide we conclude that:
  - The flip-flop output Q changes *only* at the rising edge of C.
  - The change is based on the flip-flop input value that was present right at the rising edge of the clock signal.
- Thus, this is called a **rising edge-triggered** flip-flop.
- How do we get a **falling edge-triggered** flip-flop?