



# Processor Design Basics: Datapath

---




# Overview

---


- Block Diagram of a Generic Processor
- Example of a Simple Processor
- Introduction to Datapath
- Register File
  - Accessing the Register File
  - Register File for Our Simple Processor
- Arithmetic and Logic Unit (ALU)
  - ALU for our Simple Processor
  - ALU Operation
- Initial Datapath for Our Processor
- Refinement of the Initial Datapath
  - To allow access to the RAM Data Memory
  - To allow load/store of Constant Values
- Summary

# Block Diagram of a Generic Processor

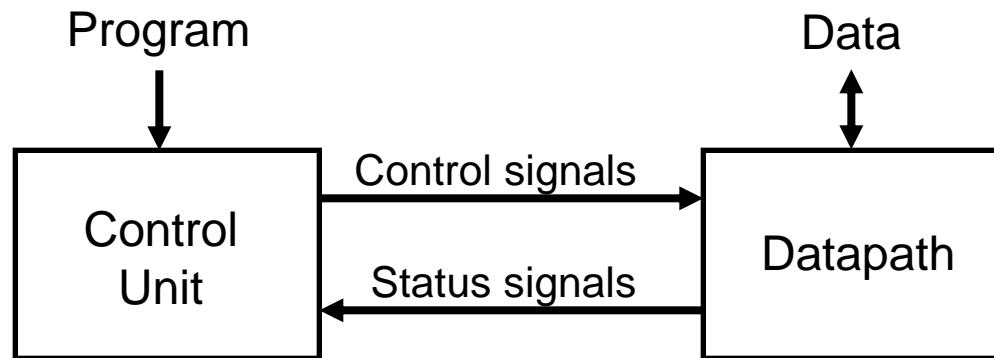


- We can divide the design of a processor into three parts:
  - An **Instruction Set** is the programmer's interface to the processor.
  - The **Datapath** does all of the actual data processing.
  - A **Control unit** uses the programmer's instructions to tell the datapath what to do.
- In this lecture we will discuss the design of a Datapath.

# Example of a Simple Processor

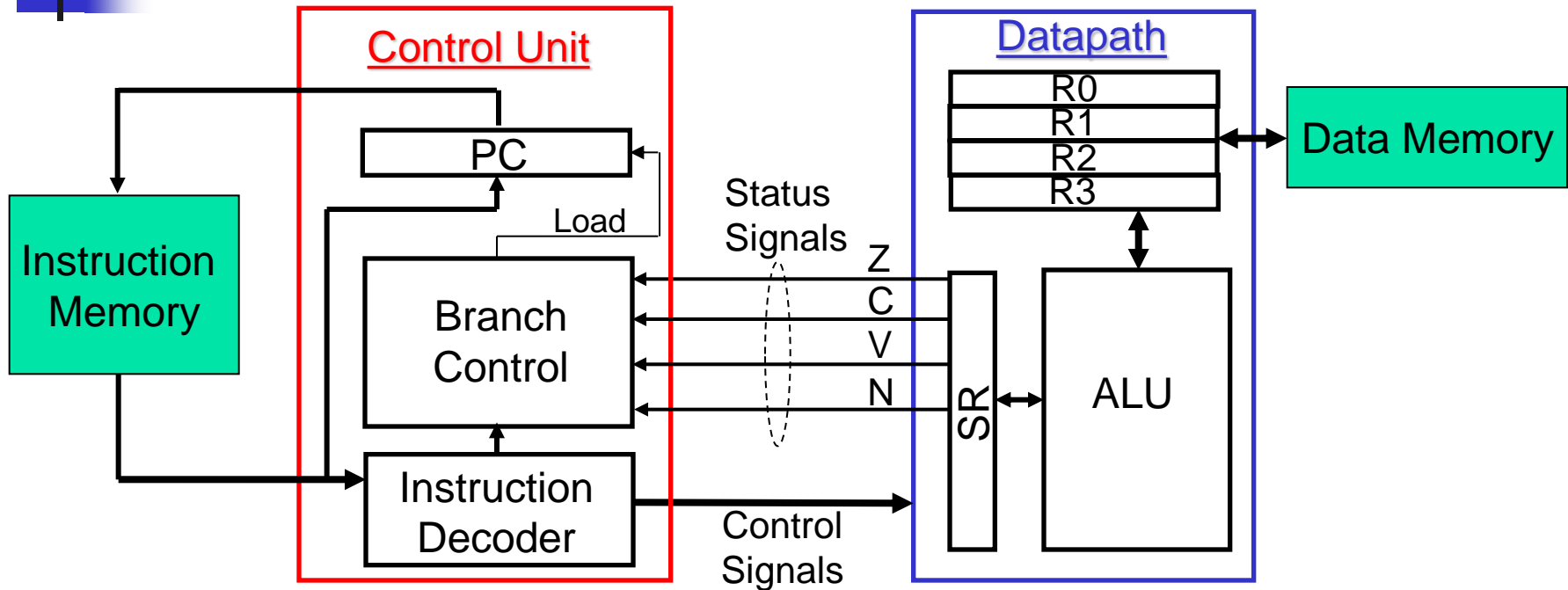

- This processor and its Instruction Set Architecture have been discussed in Lecture 13.
- Here we will look in detail at the processor's datapath, which is responsible for doing all of the “dirty” work.
  - An ALU does arithmetic, logic, and shift operations.
  - A limited set of registers serves as fast temporary storage.
  - A larger, but slower, random-access memory is also available.


# Datapath

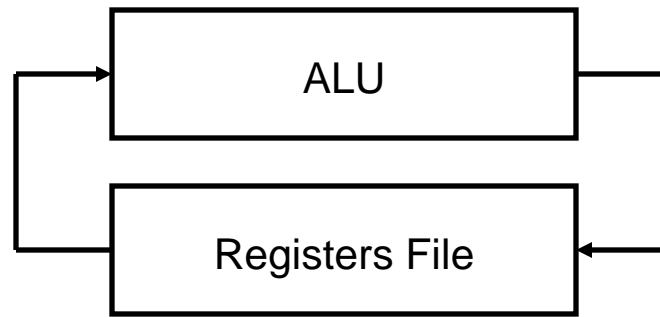

- We can look at the datapath as a **sequential circuit**.
  - Registers are used to store values, which form the state.
  - ALU performs various operations on the data stored in the registers.
- Fundamentally, the processor is just transferring data between the registers using the datapath possibly with some ALU computations.
- ALU is used to perform arithmetic, logic, and shift operations on the data while the data is being transferred.

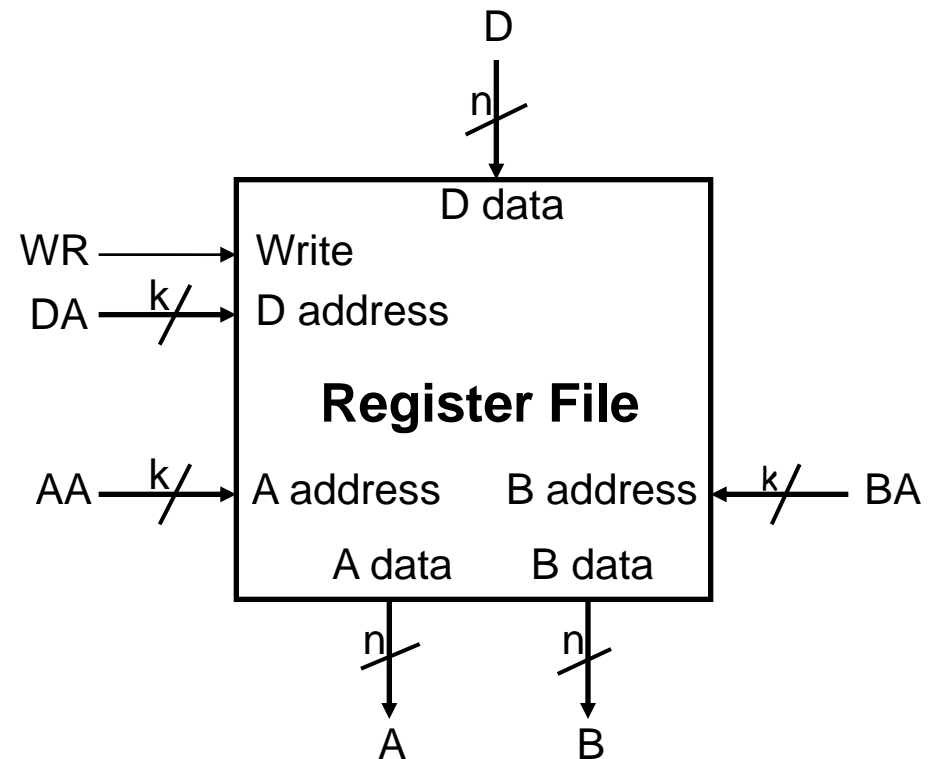
# Register File

- Modern processors have a datapath with a number of registers grouped together in a **register file**.
- Individual registers are identified by an address
  - Much like words stored in a RAM
- Here is a block symbol for a  $2^k \times n$  register file.
  - There are  $2^k$  registers, so register addresses are  $k$  bits long.
  - Each register holds an  $n$ -bit word, so the data inputs and outputs are  $n$  bits wide.



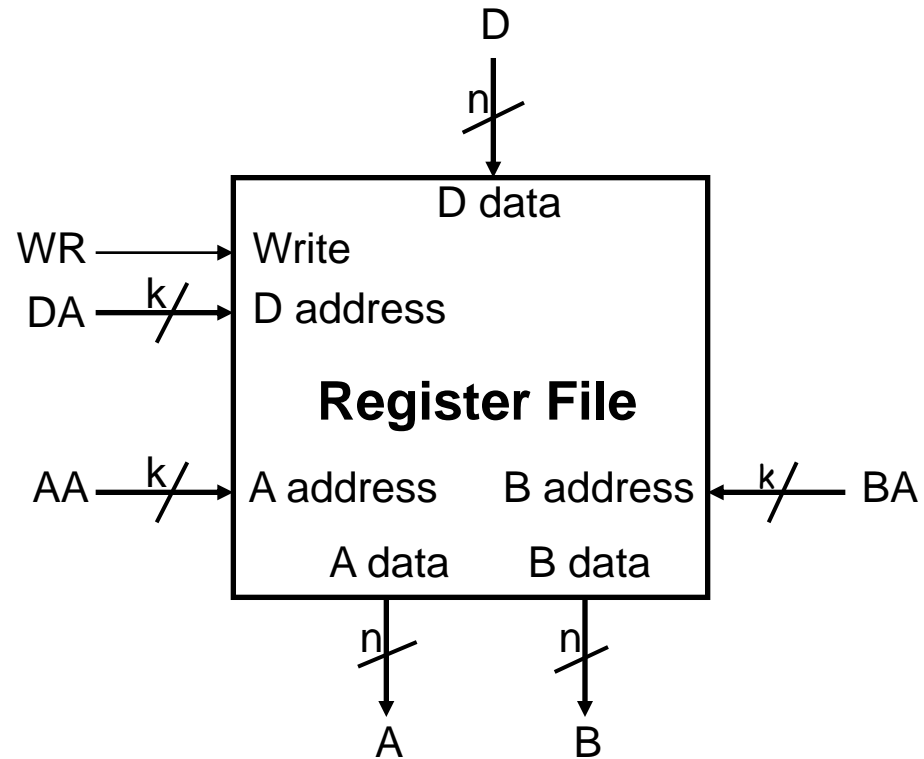
# Accessing the Register File

- You can read *two* registers at once by supplying the **AA** and **BA** inputs. The data appears on the **A** and **B** outputs.
- You can write to a register by using the **DA** and **D** inputs, and setting **WR = 1**.
- These are registers so there must be a **clock** and **reset** signals, even though we usually do not show it in diagrams.
  - We can read from the register file at any time.
  - Data is written only on the positive edge of the clock.


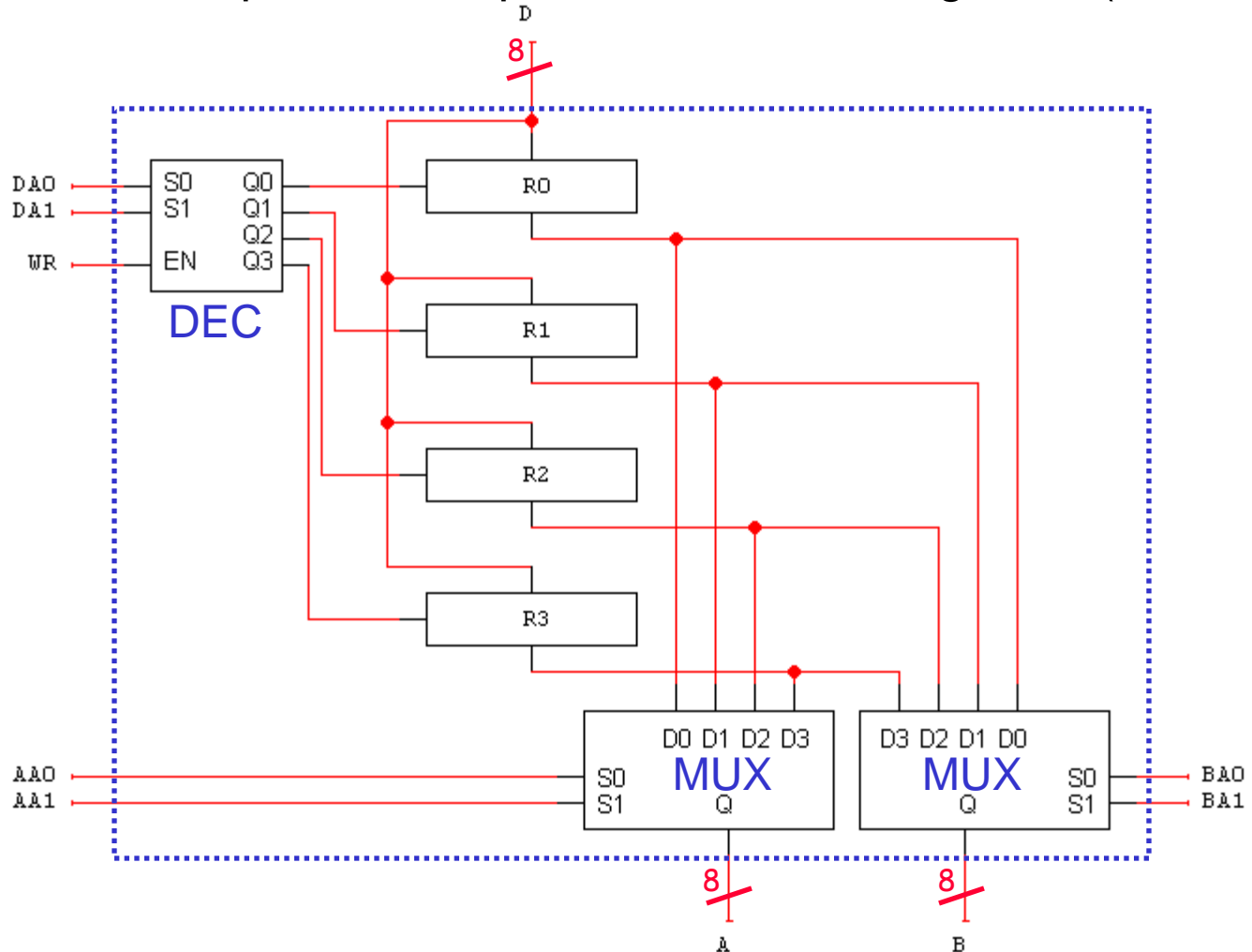
# Register File for our Processor

- We have to design a 4 x 8 register file because the Instruction Set Architecture of our processor specifies four 8-bit registers (R0 to R3).







# Explaining Our Register File

---

- The 2-to-4 decoder **DEC** selects one of the four registers for writing using the inputs DA0 and DA1. If **WR = 1**, the decoder will be enabled and one of the Load signals will be active.
- The 8-bit 4-to-1 multiplexers **MUXs** select two registers from the file and connects them to outputs A and B, based on the inputs AA0,AA1 and BA0,BA1.
- **We need to be able to read two registers at once because most of the instructions of our processor require two registers. See the next slide.**

# Recall the Instructions of Our Processor

Instruction Type	Operation	Mnemonic	Operation	Status Bits	Description
Data Manipulation Instructions	Register-format Arithmetic & Logic Operations	LDR Rj, Ri	$R_j \leftarrow R_i$	Z, N	
		INC Rj, Ri	$R_j \leftarrow R_i + 1$	Z, N	
		DEC Rj, Ri	$R_j \leftarrow R_i - 1$	Z, N	
		ADD Rj, Ri	$R_j \leftarrow R_j + R_i$	C, V, Z, N	
		ADDC Rj, Ri	$R_j \leftarrow R_j + R_i + C$	C, V, Z, N	
		SUB Rj, Ri	$R_j \leftarrow R_j + R_i' + 1$	C, V, Z, N	
		AND Rj, Ri	$R_j \leftarrow R_j \wedge R_i$	Z, N	
		OR Rj, Ri	$R_j \leftarrow R_j \vee R_i$	Z, N	
		XOR Rj, Ri	$R_j \leftarrow R_j \oplus R_i$	Z, N	
	NOT Rj, Ri	$R_j \leftarrow R_i'$	Z, N		
Register-format Shift Operations	SHL Rj, Ri	$R_j \leftarrow R_i \ll 1$	NO effect		
	SHR Rj, Ri	$R_j \leftarrow R_i \gg 1$	NO effect		
Data Movement Instructions	Memory write (from registers)	ST (Rj), Ri	$\text{Mem}[R_0 R_j] \leftarrow R_i$	NO effect	
	Memory read (to registers)	LD Rj, (Ri)	$R_j \leftarrow \text{Mem}[R_0 R_i]$	NO effect	
	Immediate transfer operations	LDI Rj, #const8	$R_j \leftarrow \text{const8}$	NO effect	
		STI (Rj), #const8	$\text{Mem}[R_0 R_j] \leftarrow \text{const8}$	NO effect	
Control Flow Instructions	Branches	BZ #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BNZ #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BC #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BNC #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BV #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BNV #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
		BN #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect	
	BNN #offset11	$\text{PC} \leftarrow \text{PC} + \text{offset11}$	NO effect		
Jump	JMP Rj, Ri	$\text{PC} \leftarrow R_j R_i$	NO effect		

# Arithmetic & Logic Unit (ALU)

- The ALU has to perform all arithmetic, logic, and shift operations specified by the Instruction Set Architecture of a processor.
- To design the ALU of our simple processor we have to **analyze** the relevant part of the **instruction set**.

Instruction Type	Operation	Mnemonic	Operation	Status Bits	Description
Data Manipulation Instructions	Register-format Arithmetic & Logic Operations	LDR Rj, Ri	$R_j \leftarrow R_i$	Z, N	
		INC Rj, Ri	$R_j \leftarrow R_i + 1$	Z, N	
		DEC Rj, Ri	$R_j \leftarrow R_i - 1$	Z, N	
		ADD Rj, Ri	$R_j \leftarrow R_j + R_i$	C, V, Z, N	
		ADDC Rj, Ri	$R_j \leftarrow R_j + R_i + C$	C, V, Z, N	
		SUB Rj, Ri	$R_j \leftarrow R_j + R_i' + 1$	C, V, Z, N	
		AND Rj, Ri	$R_j \leftarrow R_j \wedge R_i$	Z, N	
		OR Rj, Ri	$R_j \leftarrow R_j \vee R_i$	Z, N	
		XOR Rj, Ri	$R_j \leftarrow R_j \oplus R_i$	Z, N	
	NOT Rj, Ri	$R_j \leftarrow R_i'$	Z, N		
	Register-format Shift Operations	SHL Rj, Ri	$R_j \leftarrow R_i \ll 1$	NO effect	
SHR Rj, Ri		$R_j \leftarrow R_i \gg 1$	NO effect		

- Conclusion1: The ALU must perform **12 operations** therefore
  - we need at least **4 control inputs** to select one of the 12 operations.

# Arithmetic & Logic Unit (ALU)

Instruction Type	Operation	Mnemonic	Operation	Status Bits	Description
Data Manipulation Instructions	Register-format Arithmetic & Logic Operations	LDR Rj, Ri	$R_j \leftarrow R_i$	Z, N	
		INC Rj, Ri	$R_j \leftarrow R_i + 1$	Z, N	
		DEC Rj, Ri	$R_j \leftarrow R_i - 1$	Z, N	
		ADD Rj, Ri	$R_j \leftarrow R_j + R_i$	C, V, Z, N	
		ADDC Rj, Ri	$R_j \leftarrow R_j + R_i + C$	C, V, Z, N	
		SUB Rj, Ri	$R_j \leftarrow R_j + R_i' + 1$	C, V, Z, N	
		AND Rj, Ri	$R_j \leftarrow R_j \wedge R_i$	Z, N	
		OR Rj, Ri	$R_j \leftarrow R_j \vee R_i$	Z, N	
		XOR Rj, Ri	$R_j \leftarrow R_j \oplus R_i$	Z, N	
	NOT Rj, Ri	$R_j \leftarrow R_i'$	Z, N		
	Register-format Shift Operations	SHL Rj, Ri	$R_j \leftarrow R_i \ll 1$	NO effect	
SHR Rj, Ri		$R_j \leftarrow R_i \gg 1$	NO effect		

- Conclusion2: The operations require 1 or 2 operands therefore
  - The ALU must have 2 data inputs.
  - The operands are 8-bit binary numbers.

# Arithmetic & Logic Unit (ALU)

Instruction Type	Operation	Mnemonic	Operation	Status Bits	Description
Data Manipulation Instructions	Register-format Arithmetic & Logic Operations	LDR Rj, Ri	$R_j \leftarrow R_i$	Z, N	
		INC Rj, Ri	$R_j \leftarrow R_i + 1$	Z, N	
		DEC Rj, Ri	$R_j \leftarrow R_i - 1$	Z, N	
		ADD Rj, Ri	$R_j \leftarrow R_j + R_i$	C, V, Z, N	
		ADDC Rj, Ri	$R_j \leftarrow R_j + R_i + C$	C, V, Z, N	
		SUB Rj, Ri	$R_j \leftarrow R_j + R_i' + 1$	C, V, Z, N	
		AND Rj, Ri	$R_j \leftarrow R_j \wedge R_i$	Z, N	
		OR Rj, Ri	$R_j \leftarrow R_j \vee R_i$	Z, N	
		XOR Rj, Ri	$R_j \leftarrow R_j \oplus R_i$	Z, N	
	NOT Rj, Ri	$R_j \leftarrow R_i'$	Z, N		
	Register-format Shift Operations	SHL Rj, Ri	$R_j \leftarrow R_i \ll 1$	NO effect	
SHR Rj, Ri		$R_j \leftarrow R_i \gg 1$	NO effect		

- Conclusion3: Each operation returns **1 result**, therefore
  - The ALU must have **1 data output**.
  - The result is 8-bit binary number.


# Arithmetic & Logic Unit (ALU)

Instruction Type	Operation	Mnemonic	Operation	Status Bits	Description
Data Manipulation Instructions	Register-format Arithmetic & Logic Operations	LDR Rj, Ri	$R_j \leftarrow R_i$	Z, N	
		INC Rj, Ri	$R_j \leftarrow R_i + 1$	Z, N	
		DEC Rj, Ri	$R_j \leftarrow R_i - 1$	Z, N	
		ADD Rj, Ri	$R_j \leftarrow R_j + R_i$	C, V, Z, N	
		ADDC Rj, Ri	$R_j \leftarrow R_j + R_i + C$	C, V, Z, N	
		SUB Rj, Ri	$R_j \leftarrow R_j + R_i' + 1$	C, V, Z, N	
		AND Rj, Ri	$R_j \leftarrow R_j \wedge R_i$	Z, N	
		OR Rj, Ri	$R_j \leftarrow R_j \vee R_i$	Z, N	
		XOR Rj, Ri	$R_j \leftarrow R_j \oplus R_i$	Z, N	
	NOT Rj, Ri	$R_j \leftarrow R_i'$	Z, N		
	Register-format Shift Operations	SHL Rj, Ri	$R_j \leftarrow R_i \ll 1$	NO effect	
SHR Rj, Ri		$R_j \leftarrow R_i \gg 1$	NO effect		

- Conclusion4: Some of the operations must **modify status bits** therefore
  - The ALU must have **4 status outputs** to indicate
    - if **C**arry and/or **oV**erflow has occurred
    - if the result of an operation is **Z**ero or **N**egative
 
# The ALU for Our Processor

- We will use the following block symbol for the ALU.
  - **A** and **B** are two 8-bit data inputs for operands.
  - **FS** is a 5-bit control input to select an operation.
  - The 8-bit result is called **F**.
  - Several **status bits** provide more information about the output **F**:
    - **V** = 1 in case of signed overflow.
    - **C** is the carry out.
    - **N** = 1 if the result is negative.
    - **Z** = 1 if the result is 0.
  - **Carry-in** input is needed for instruction ADDC (ADD with carry-in).
- This block should look familiar to you from your design project!



# ALU Operations (Functions)


- Each ALU operation is **uniquely encoded** – see the **function selection code FS** in the table.
- The function select code FS is 5 bits long, but there are only 12 different operations here. Why?
- The FS code has a structure:
  - FS(5) = '0' indicates **data manipulation**
  - FS(4:3) =
    - "00" indicates **arithmetic** operations
    - "01" indicates **propagate** or **shift** operations (except  $F = B - 1$ )
    - "10" indicates **logic** operations
- Structuring the FS code helps to design simpler decoder structure for the ALU.

INSTR	FS	Operation
INC	00000	$F = B + 1$
ADD	00001	$F = A + B$
ADDC	00010	$F = A + B + \text{Carry-in}$
SUB	00011	$F = A + B' + 1$
DEC	00100	$F = B - 1$
LDR	00101	$F = B$
SHR	00110	$F = \text{sr } B$ (shift right)
SHL	00111	$F = \text{sl } B$ (shift left)
AND	01000	$F = A \wedge B$ (AND)
OR	01001	$F = A \vee B$ (OR)
XOR	01010	$F = A \oplus B$
NOT	01011	$F = B'$


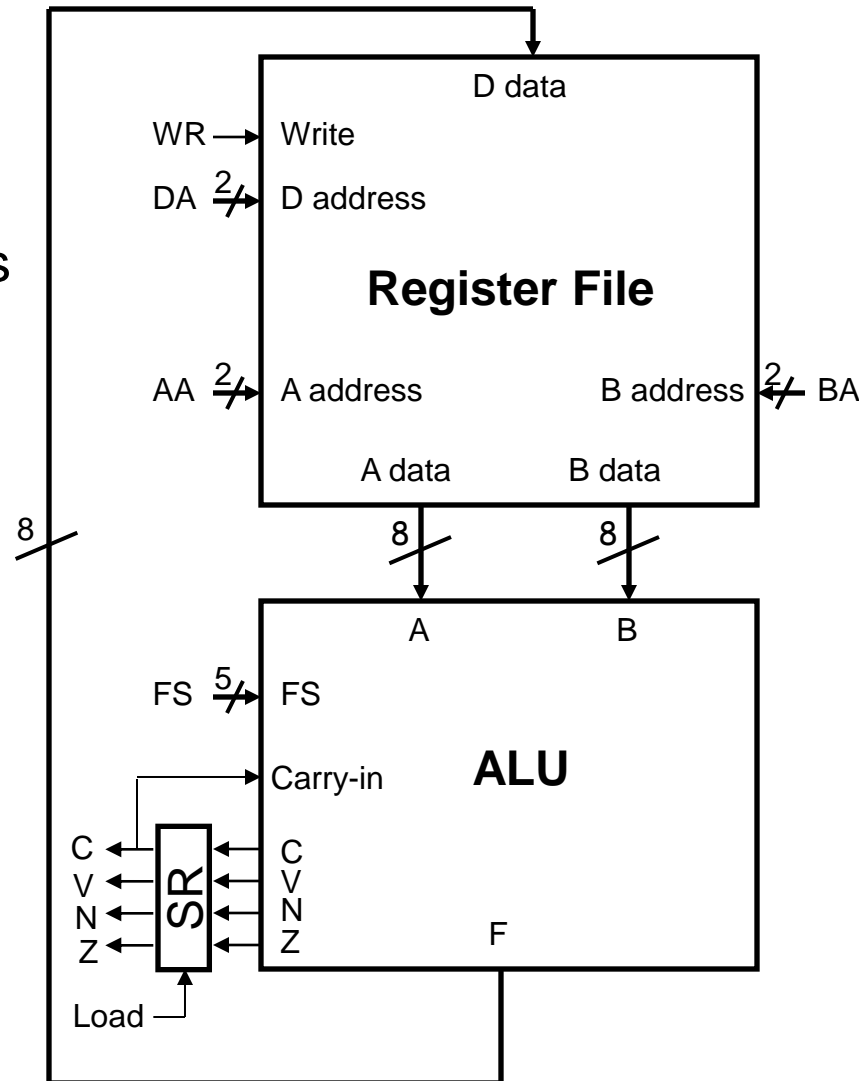
# Initial Datapath for Our Processor

- Here is the most basic datapath.
  - The ALU's two data inputs come from the register file.
  - The ALU computes a result, which is saved back to the registers.
  - The status bits are stored in the status register SR.
- **WR**, **DA**, **AA**, **BA**, **FS** and **Load** are **control signals**.
  - Their values determine the exact actions taken by the datapath,
  - That is, which registers are used and for what operation.




# An Example Computation

- Let us look at the proper control signals for executing the processor instruction below:

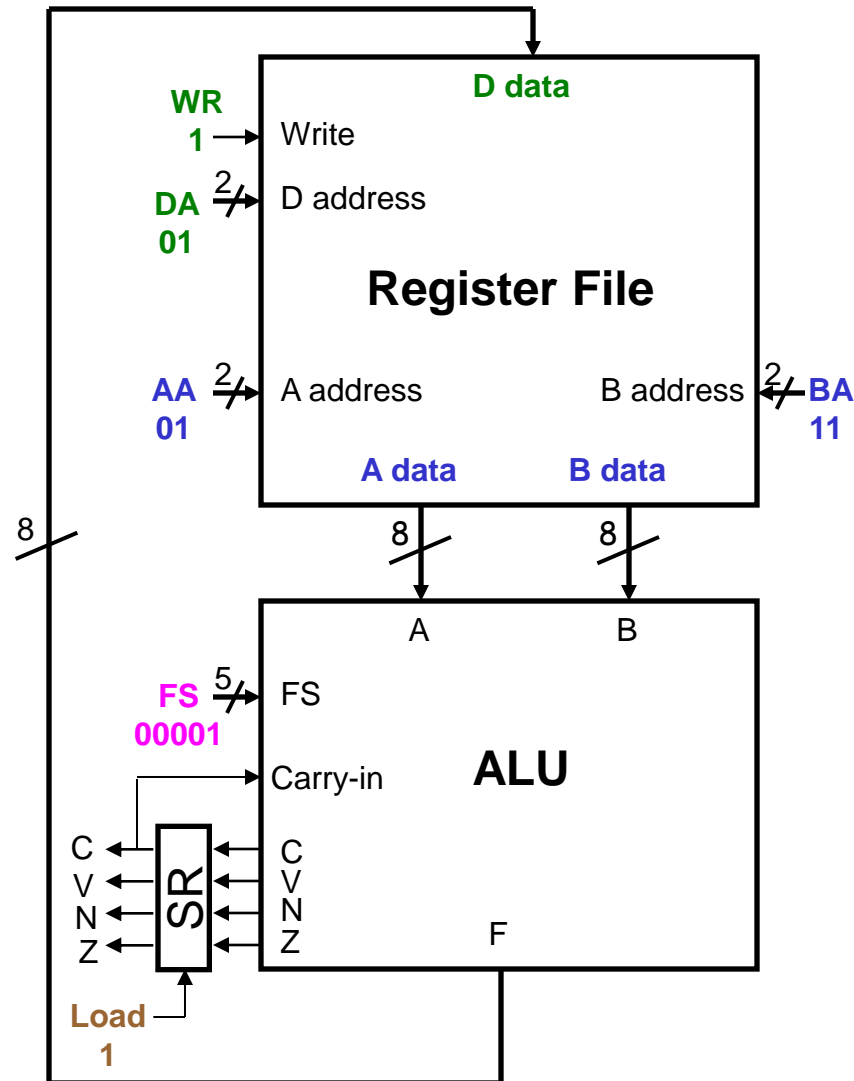
**ADD R1, R3       $R1 \leftarrow R1 + R3$**

- Set all control signals **simultaneously** as explained below.
- Set **AA = 01** and **BA = 11**. This causes the contents of R1 to appear at **A data**, and the contents of R3 to appear at **B data**.
- Set the ALU's function select input **FS = 00001** (A + B).
- Set **DA = 01** and **WR = 1**. On the next positive clock edge, the ALU result ( $R1 + R3$ ) will be stored in R1.
- Set **Load = 1**. On the next positive clock edge, the ALU status bits (C, V, N, Z) will be stored in SR.




# Two Issues with this Datapath

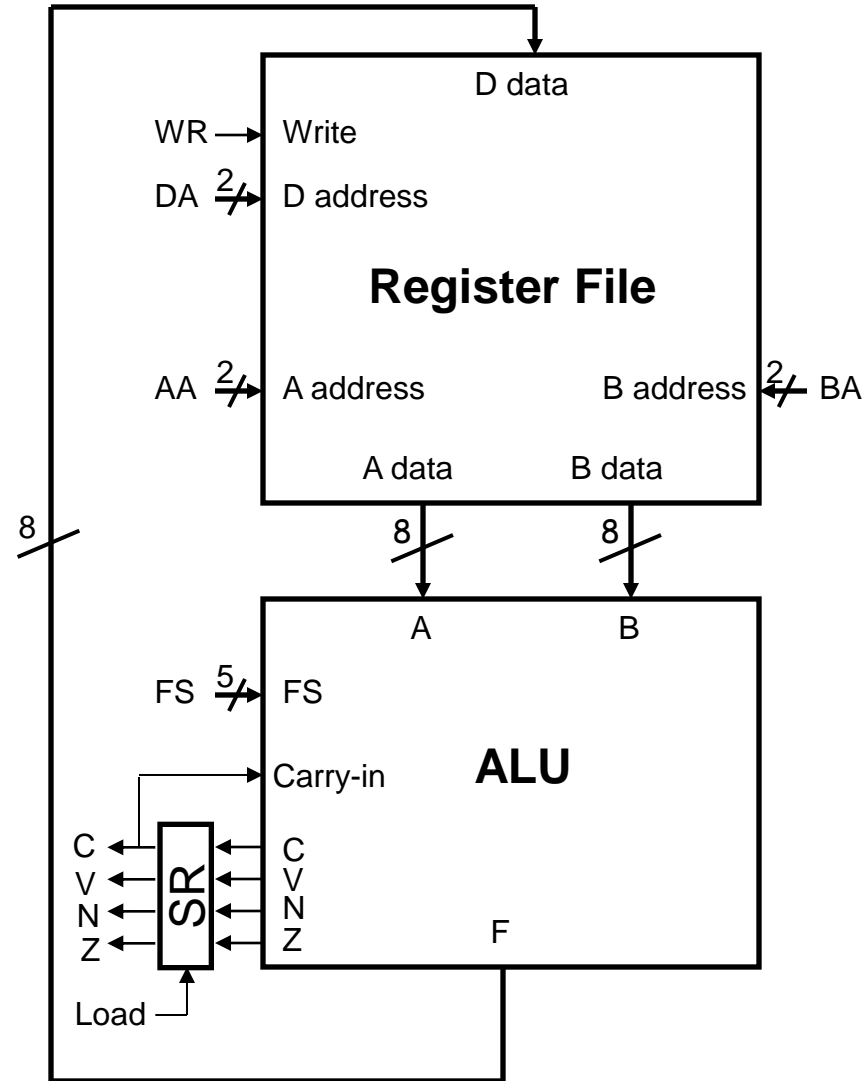- **Q1:** Four registers is not a lot. What if we need more storage?
- **A1:** Our processor has a **Data RAM Memory** and supports **data movement** between RAM and registers with instructions **ST** and **LD**.
- **Q2:** What if we have to do operations with constants?
- **A2:** Our processor has two instructions: **LDI** (**load an 8-bit constant in a register**), **STI** (**storing an 8-bit constant in a memory location**)
- **Problem!** Our initial datapath on the right does not support the answers A1 and A2. Why?
- **Solution:** We have to refine our initial datapath. See next slides!



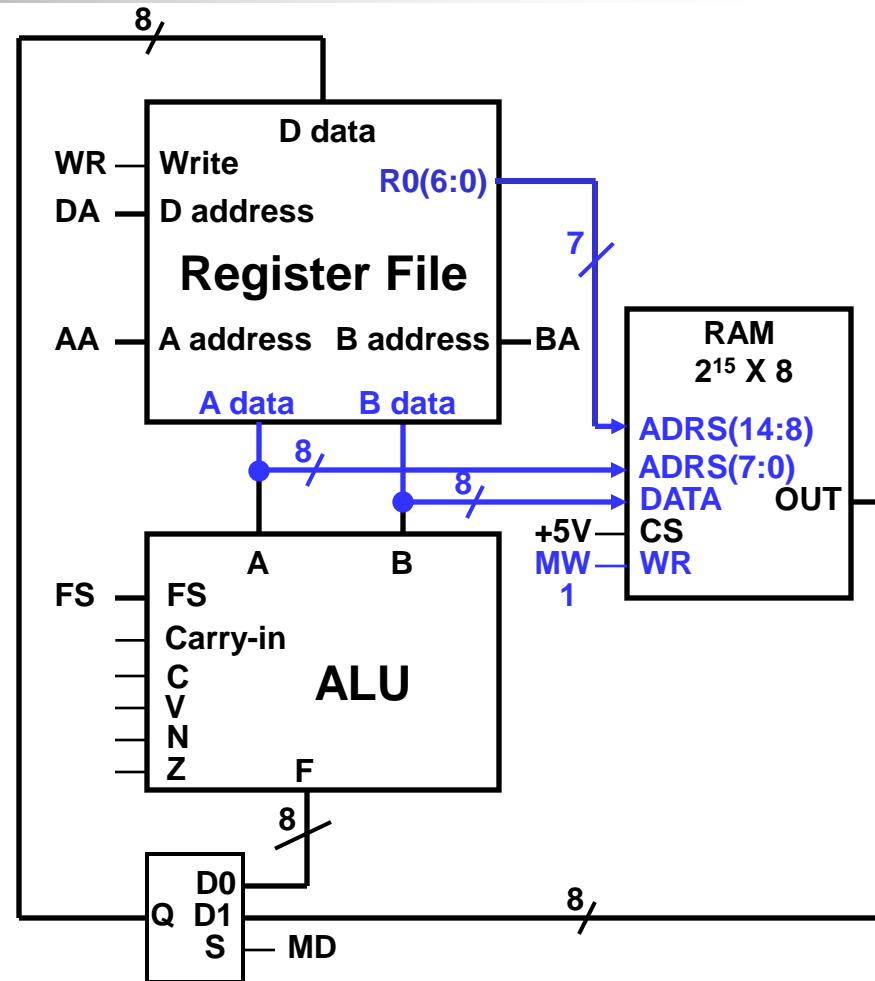
# Writing to RAM

- Here is a way to connect RAM into our existing datapath.
- To *write* to RAM, we must give an address and a data value.
- These will come from the registers. We connect **A data** and **Register R0** to the memory's **ADRS** input, and **B data** to the memory's **DATA** input.
- Set **MW = 1** to write to the RAM. (It's called MW to distinguish it from the WR write signal on the register file.)



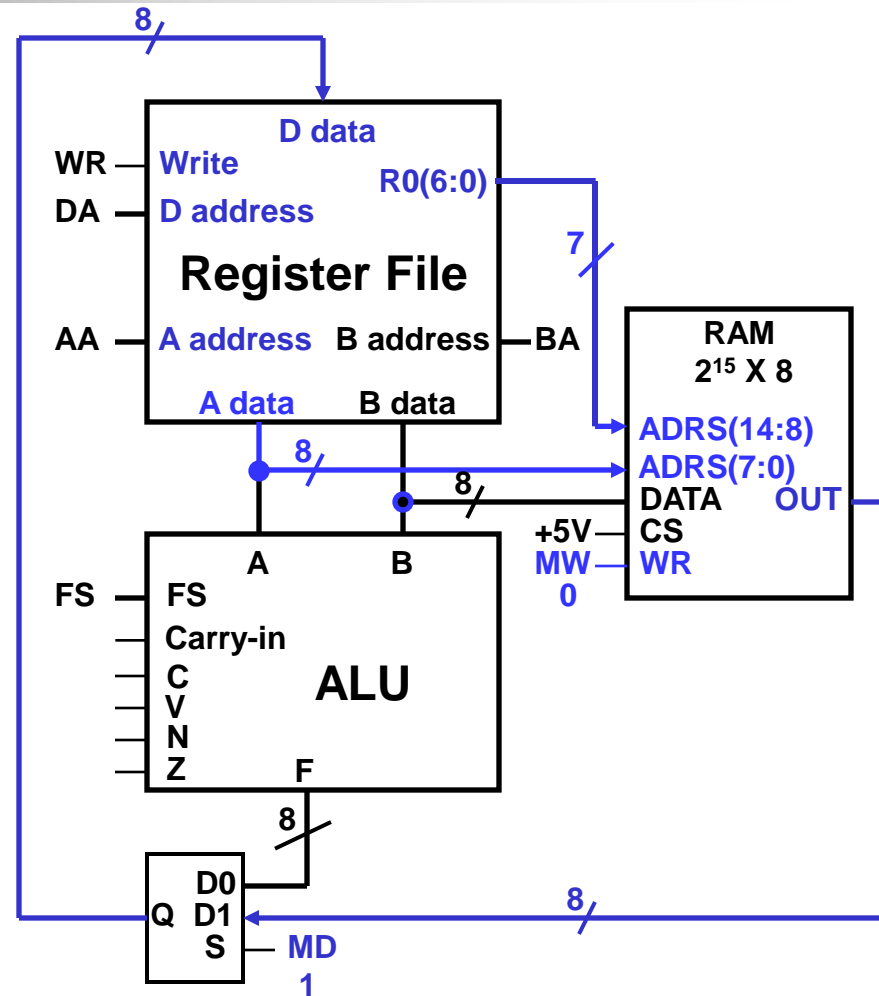
# Reading from RAM

- To *read* from RAM, *A* data and register R0 must supply the address.
- Set  $MW = 0$  for reading.
- The incoming data will be sent to the register file for storage.
- This means that the register file's *D data* input could come from either the ALU output or the RAM.
- A MUX *MD* selects the source for the register file.
  - When  $MD = 0$ , the ALU output can be stored in the register file.
  - When  $MD = 1$ , the RAM output is sent to the register file instead.


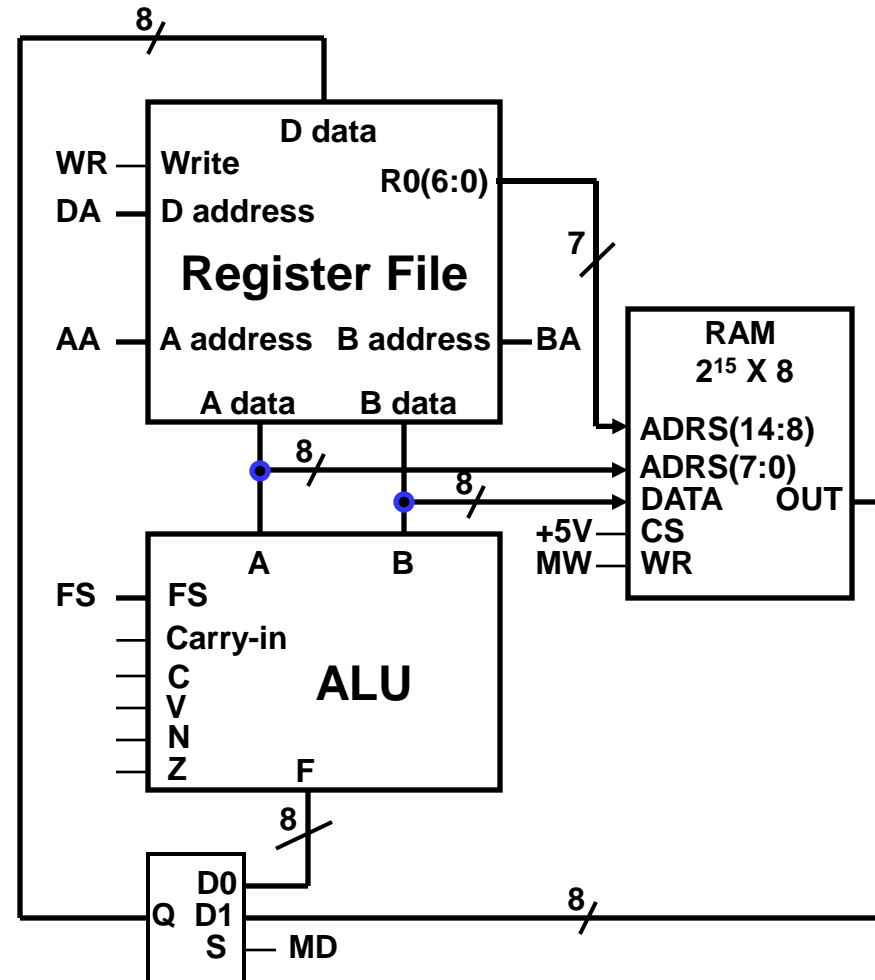
# Notes About This Setup

- We now have a way to copy data between our register file and the RAM.
- Notice that there is **no** way for the ALU to **directly access** the memory - RAM contents **must** go through the register file first.
- Here the size of the memory is **limited** by the size of the registers:
  - With 8-bit registers, we use a  $2^{15} \times 8$  RAM.
  - Address bits **14 down to 8** are **always** taken from register **R0**.
  - Address bits **7 down to 0** can be taken from **any** register.
- For simplicity we assume the RAM is at least as fast as the processor clock. (**This is definitely not the case in real processors these days!**)



# Example Sequence of Instructions


- The RAM memory access in our processor is supported by two instructions:
  - **LD R<sub>j</sub>, (R<sub>i</sub>)** -- load register R<sub>j</sub> with the content of a RAM memory cell at address given by register R<sub>i</sub>;
  - **ST (R<sub>j</sub>), R<sub>i</sub>** -- store the content of register R<sub>i</sub> in a RAM memory cell at address given by register R<sub>j</sub>;
- Here is a simple series of memory/register transfer instructions:

<b>LD R3, (R2)</b>	$R3 \leftarrow \text{Mem}[R0 R2]$
<b>DEC R3, R3</b>	$R3 \leftarrow R3 - 1$
<b>ST (R2), R3</b>	$\text{Mem}[R0 R2] \leftarrow R3$

- This just decrements the content of RAM memory cell at address R0|R2 .
  - Again, our ALU only operates on registers, so the RAM contents must first be loaded into a register, and then saved back to RAM.
  - We will assume that R0 and R2 contain a valid memory address.
- How would these instructions execute in our datapath?

# “LD R3, (R2)” is $R3 \leftarrow \text{Mem}[R0|R2]$


- AA should be set to 10, to read register R2.
- The value in R2 will be sent to the RAM address inputs, so  $\text{Mem}[R0|R2]$  appears as the RAM output OUT.
- MD must be 1, so the RAM output goes to the register file.
- To store something into R3, we will need to set  $DA = 11$  and  $WR = 1$ .
- MW should be 0, so nothing is accidentally changed in RAM.
- We do not use the ALU, thus FS value can be arbitrary)
- We do not use the second register file output, thus BA also can be arbitrary.

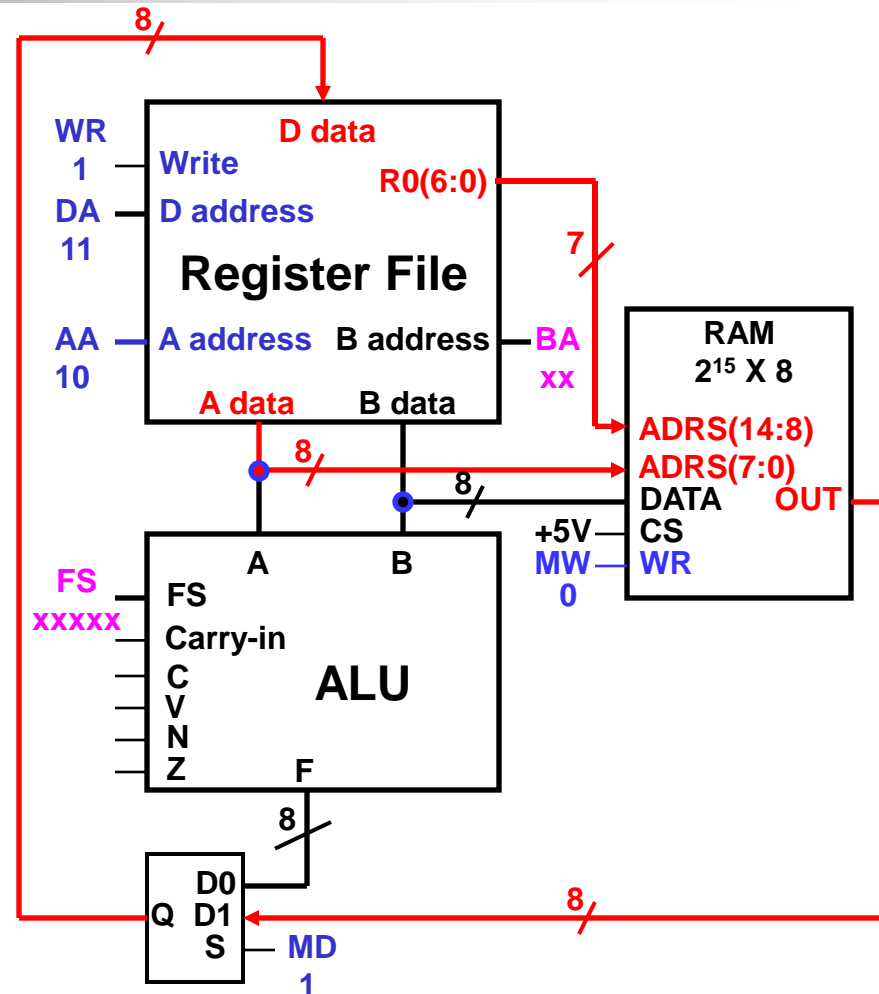



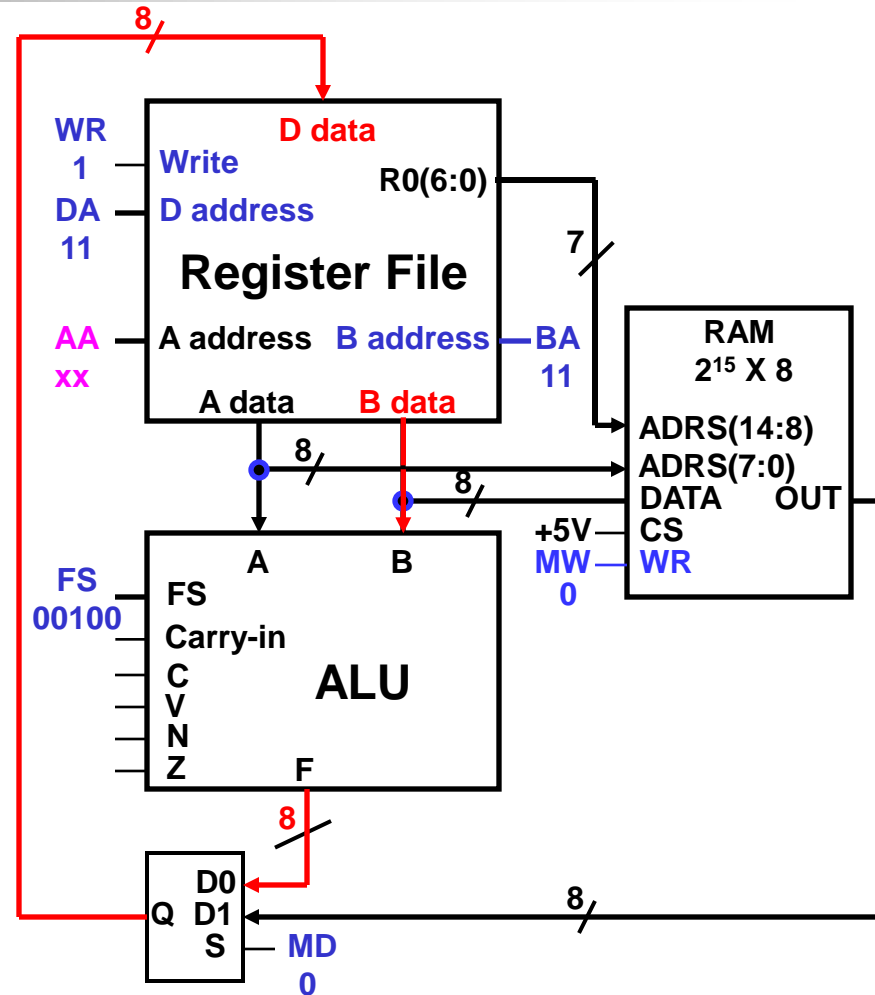
# “DEC R3, R3” is $R3 \leftarrow R3 - 1$

- $BA = 11$ , so R3 is read from the register file and sent to the ALU's B input.
- $FS$  needs to be  $00100$  for the operation B - 1. Then,  $R3 - 1$  appears as the ALU output F.
- If  $MD$  is set to 0, this output will go back to the register file.
- To write to R3, we need to make  $DA = 11$  and  $WR = 1$ .
- Again,  $MW$  should be 0 so the RAM is not changed.
- We do not use  $AA$ .




# “ST (R2), R3” is Mem[R0|R2] ← R3

- Finally, we want to store the contents of R3 into RAM address R0|R2.
- Remember the RAM address comes from “A data,” and the contents come from “B data.”
- So, we have to set  $AA = 10$  and  $BA = 11$ . This sends R2 to  $ADRS(7:0)$ , and R3 to DATA.
- $MW$  must be 1 to write to memory.
- No register updates are needed, so  $WR$  should be 0, and MD and DA are unused.
- We also do not use the ALU, so FS was ignored.

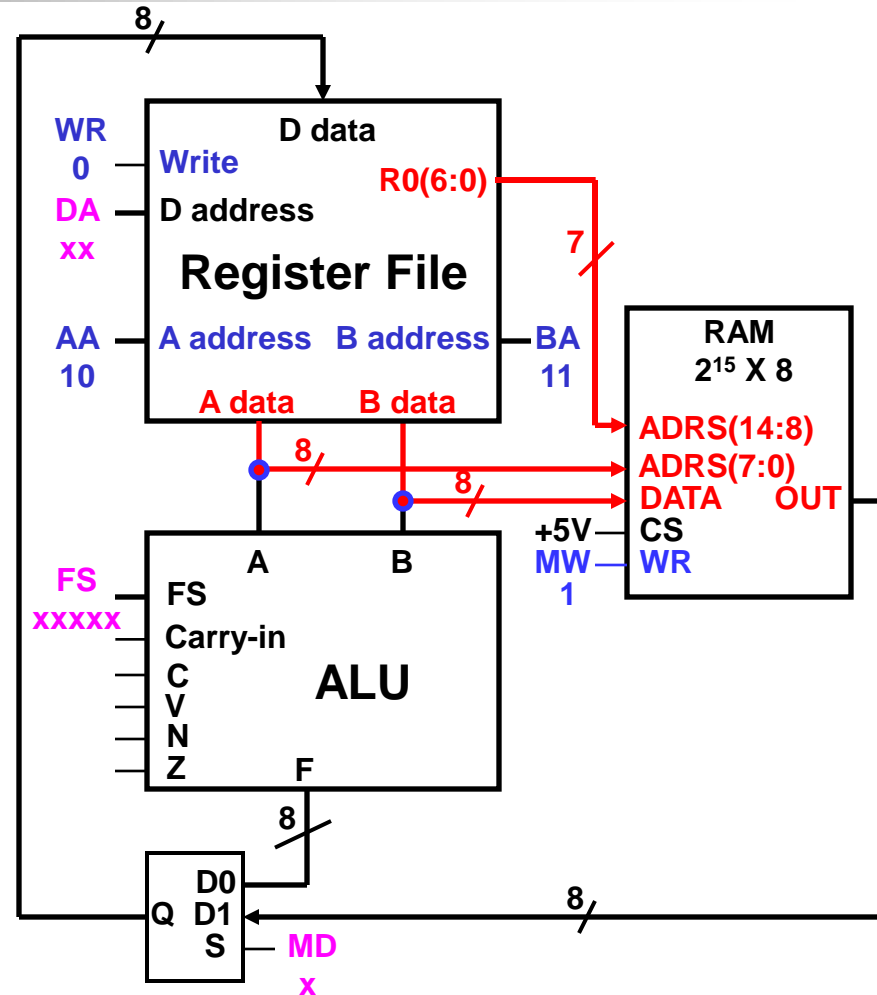
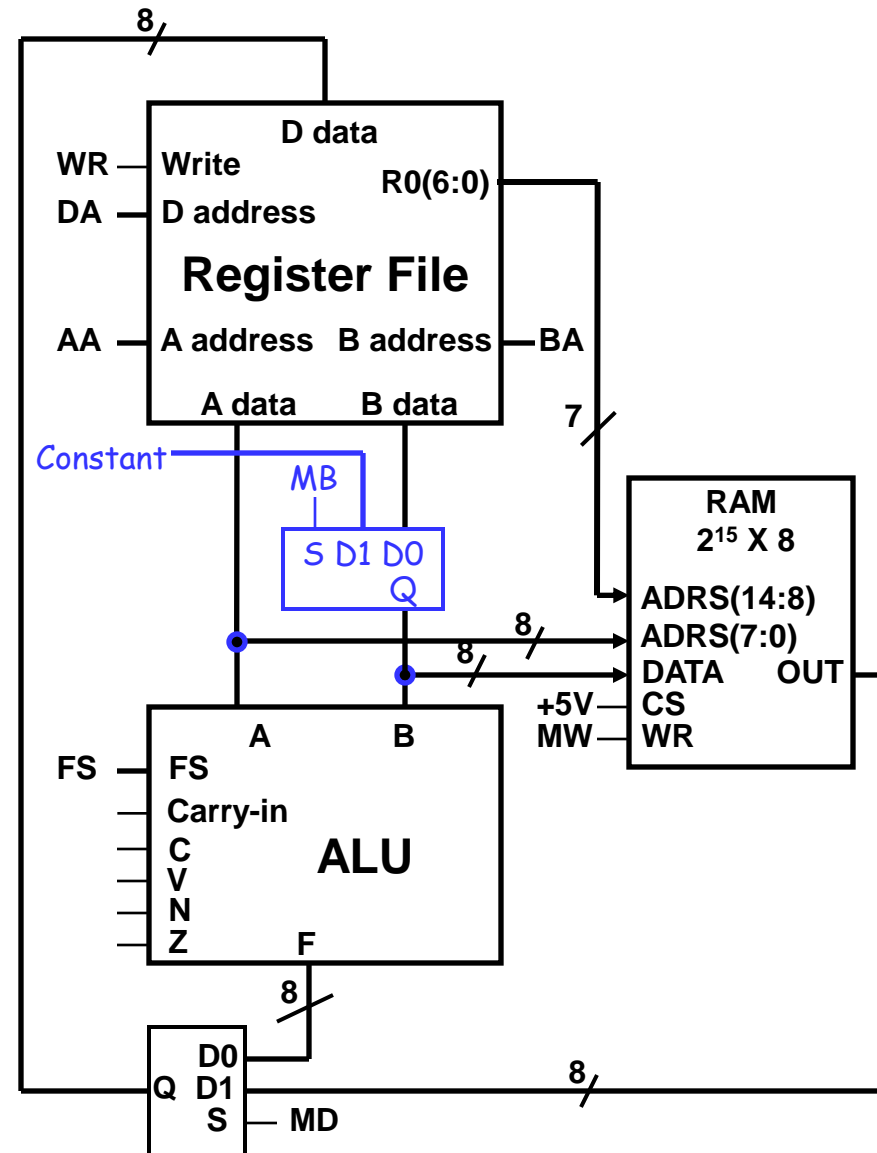
# Constant In

- One last refinement is the addition of a **Constant** input.
- The modified datapath is shown on the right,
  - One extra MUX is added.
  - With one extra control signal **MB**.
- Intuitively, it provides an easy way to initialize a register or memory location with some arbitrary number (8-bit constant).
- The constant comes from the instructions **LDI** and **STI** (see instruction format 2!).
- **At home try to set the control signals of the datapath on the right for the following instructions:**
  - **LDI R2, #0xc8**
  - **STI (R1), #0x3f**





# Who is Configuring the Datapath?

---

- The datapath on the previous slide is a complete datapath for our simple processor, i.e.,
  - the datapath supports all Data Manipulation instructions
  - the datapath supports all Data Movement instructions
- Different actions are performed when we provide different values for the datapath control signals
  - See the instruction examples on previous slides
- In processors, the datapath actions are determined by the **program** that is loaded and running
- The **Control Unit** is responsible for generating the correct control signals for a datapath, based on the program code
- We will talk about the control unit next week.



# Summary

---

- The datapath is the part of a processor where computation is done
  - The basic components are an ALU, a register file and some RAM
  - The ALU does all of the computations
  - The register file and RAM provide storage for the ALU's operands and results.
- Various control signals in the datapath govern its behavior.
- Next week, we will see
  - how programmers can give commands to the processor
  - how these commands are translated in control signals for the datapath.